
Unit 1.5. Electronic circuits and logic families

Digital Electronic Circuits
E.T.S.I. Informática
Universidad de Sevilla

Jorge Juan-Chico <jjchico@dte.us.es> 2010-2024

You are free to copy, distribute and communicate this work publicly and make derivative work provided you cite the source and respect the conditions of the Attribution-Share alike license from Creative Commons.


You can read the complete license at:

<http://creativecommons.org/licenses/by-sa/4.0>

Contenidos

- Electronic circuits
 - Charge and conductors
 - Electronic devices
 - Electric circuits
 - Semiconductors
 - Technology: discrete and integrated devices
- Logic families
 - Digital circuits
 - Gates and logic operators
 - Logic families
 - Electrical and switching parameters

Conductors and charge carriers

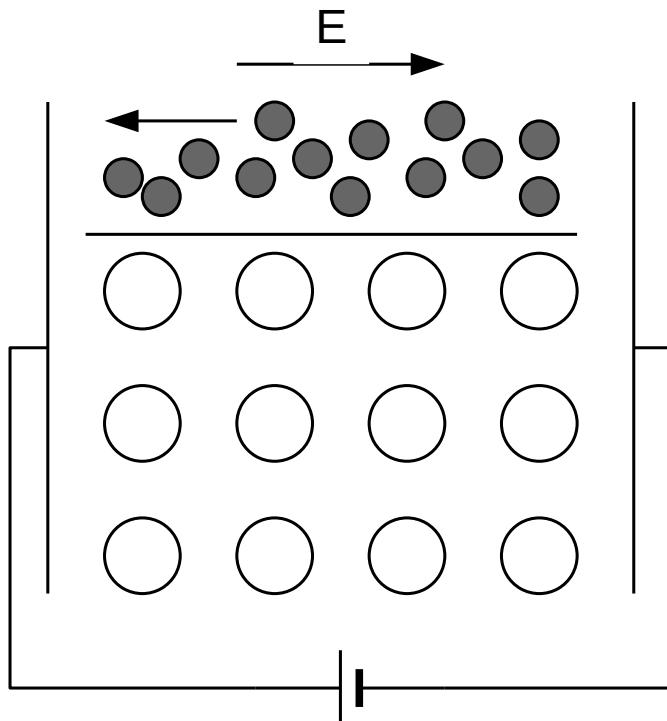


- Conductors charge carriers can be positive (+) or negative (-)
- Most typical charge carriers are “free” electrons (-) in metals.
- When an electric field (E) is applied, electrons move accordingly.
- Electric fields exist whenever an electric potential difference (voltage) is applied.

○ Metal atoms

● Free electrons

Basic conductor properties

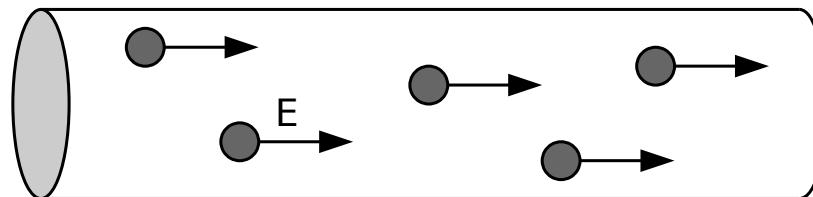
- Conductors in electrical circuits
 - Typically wire-shaped.
 - Charge (and electric field) is confined inside the conductors.
- Charge does not accumulate inside conductors: conductors remain neutral.



Electrical magnitudes


- Voltage: potential energy difference between two points in the circuit by unit of charge (Volts [V]).
 - Electric field (electric force) points from high to low voltage areas.
 - Positive charges move to lower voltage, negative charges to higher voltage (lower energy in both cases).
 - Absolute voltage values do not exist. An arbitrary point is selected as zero voltage (ground node or GND).
- Current: charge per unit time crossing the conductor's section (Amperes [A]).
 - Same current in all sections of a conductor. Why?

$$I = \frac{dQ}{dt}$$

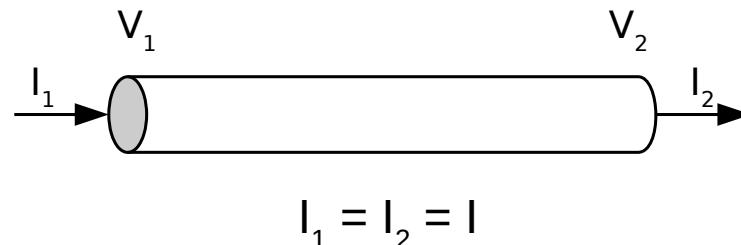

Ohm's Law

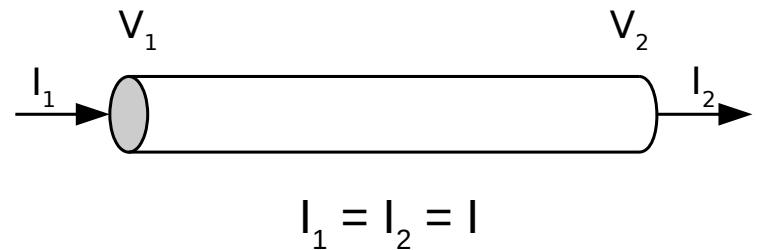
- Ohms law
 - Resistance: relation between the voltage and current across the conductor.
 - Unit: Ohms $[\Omega]=[V]/[A]$
- Ideal conductors ($R=0$)
 - Wires: metals used for connection in electronic circuits can be considered ideal conductors most of the time.
 - Consequence: same voltage across wires.



$$R = \frac{V_1 - V_2}{I}$$

$$R = 0 \Rightarrow V_1 = V_2$$


Electronic devices

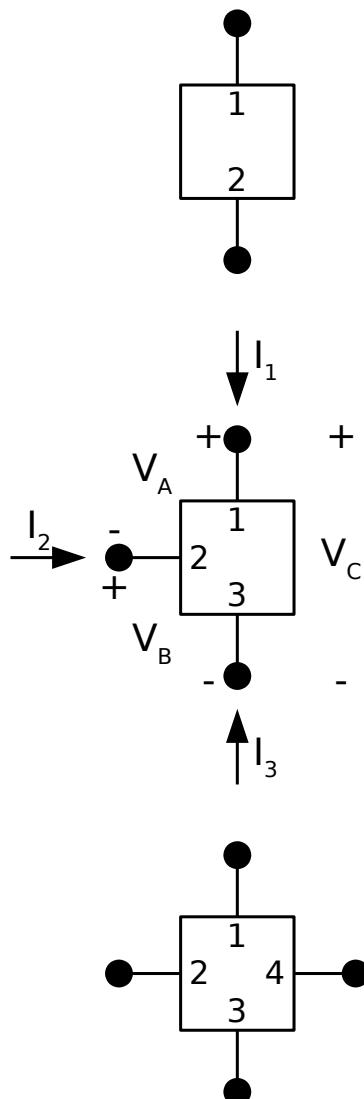

- Electronic elements with two or more terminals (connection points).
- Impose a relationship between the current and voltage across the terminals.
- All currents and voltages are signed numbers.
 - Current: arrow indicates positive current direction (going into the device by convention).
 - Voltage: when the voltage is positive, (+) voltage is higher than (-) voltage, and the other way around.
- Net charge is not accumulated inside the devices:
 - $I_1 + I_2 + I_3 + \dots = 0$


Basic electronic devices

Resistor
Ohm [Ω]

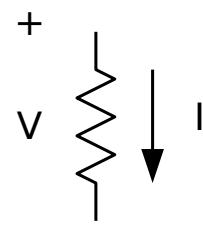


$$V = IR$$

Capacitor
Farad [F]

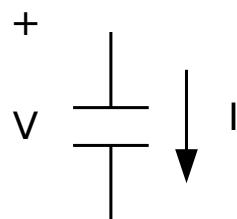

$$I = C \frac{dV}{dt}$$

Inductor
Henry [H]

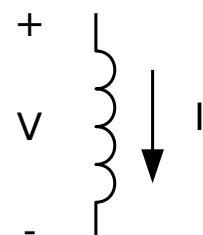


$$V = -L \frac{dI}{dt}$$


Basic electronic devices

Ideal sources

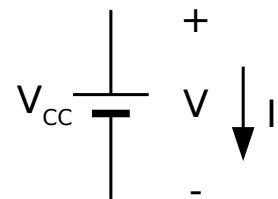
Constant voltage source
(power supply)
(battery)




$$V = V_{CC}$$

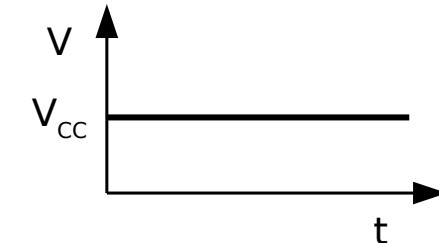


Variable voltage source

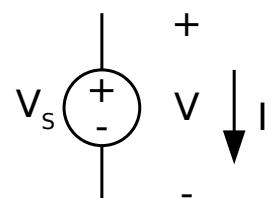


$$V = V_S(t)$$

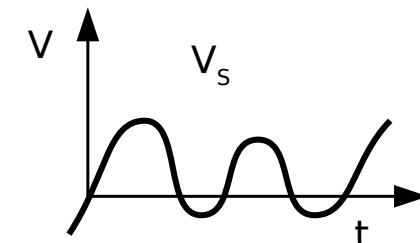

Variable current source

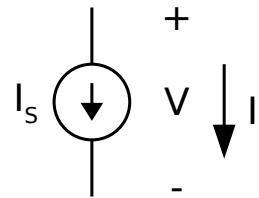


$$I = I_S(t)$$

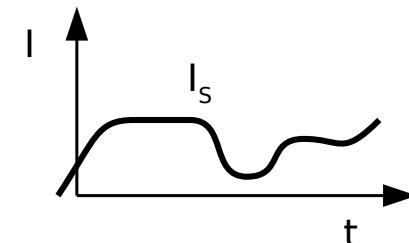


Electric circuits

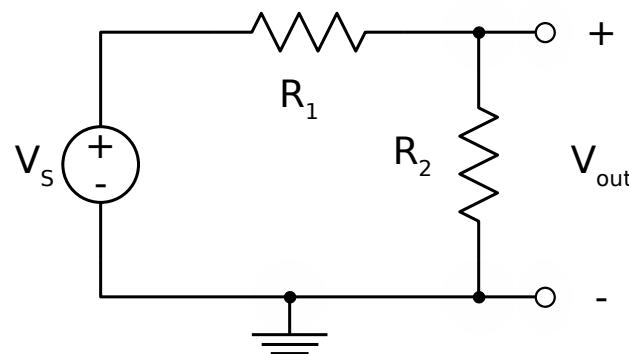- Connection of devices with wires to achieve some properties or functionality.
- Node: connection between two or more devices.
 - Same voltage alongside a single node (ideal wire)



Voltage divider

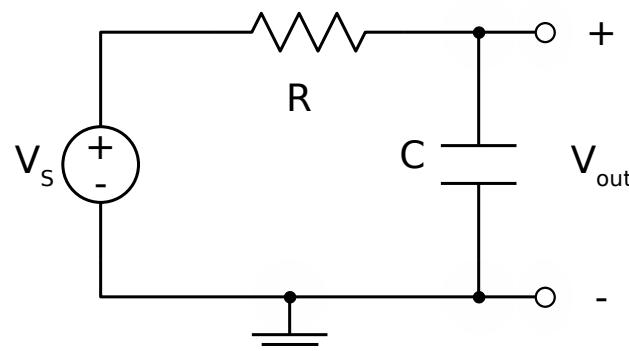

Low-pass filter


Circuit analysis

- Circuit analysis is based on:
 - Device equations
 - Topological Equations (Kirchhoff laws)
- Kirchhoff laws
 - Current: the sum of the currents entering a circuit node is zero (charge does not accumulate in circuit nodes)
 - The sum of voltage drops along any close path is zero.

Types of circuit analysis



- Static analysis (DC):
 - All magnitudes and sources are constant.
 - The solution is derived from algebraic equations.
- Transient analysis
 - Considers variable sources and the evolution of circuit's magnitudes with time.
 - In general, the solution implies resolving differential equations :)
- Frequency analysis (AC)
 - Solves the circuit for sinusoidal signals.
 - Simplified resolution thanks to the use of specific mathematical tools (Laplace's Transform).
 - Obtains the circuit response as a function of the signal's frequency.

Circuit analysis. Example

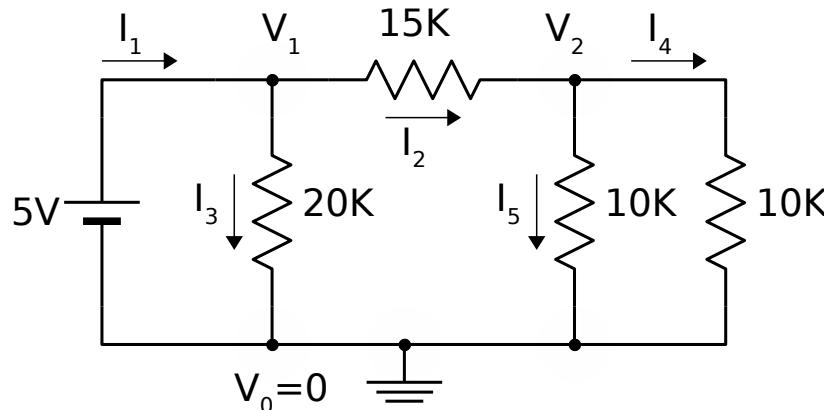

Static analysis (DC)

Simulation

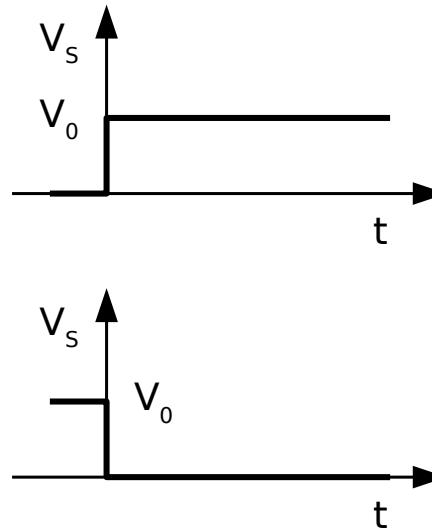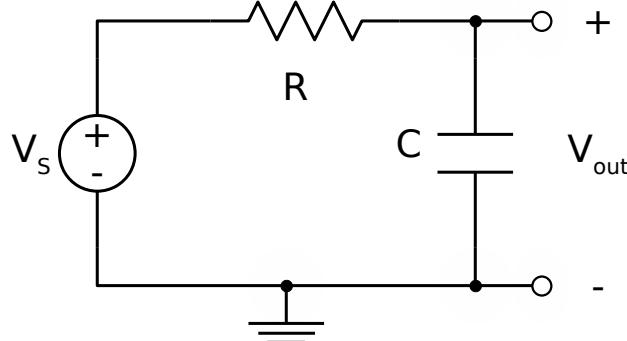


Transient analysis

Simulation

Power


- Consumed energy per unit time.
- Power is a major concern in current electronics.
 - Portable devices (battery duration).
 - Dissipation (put a big fan!).
 - Environment (climate change).
- Power is consumed (dissipated) every time some current goes from a higher to a lower potential.
- Power can be negative
 - In this case, the device is "producing" power to be consumed in the circuit (e.g. a power supply)

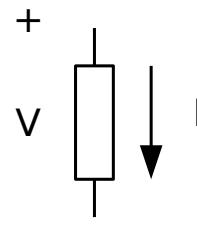


$$P = VI$$

Semiconductor devices (intrinsic)

T=0

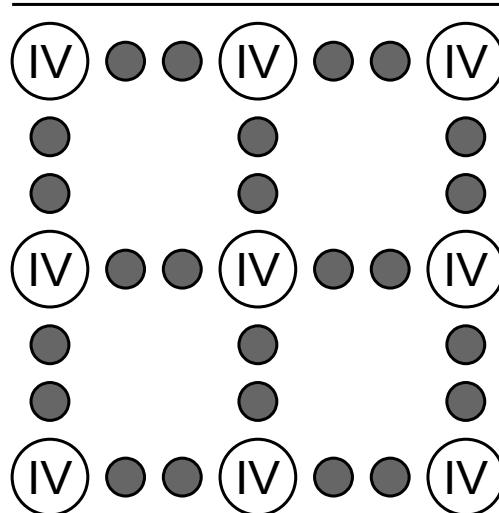

T>0

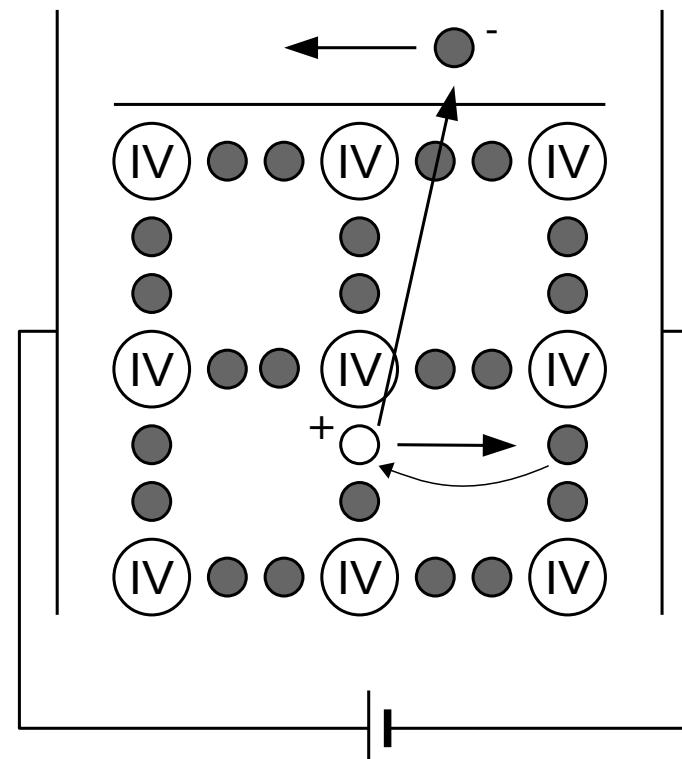

Group IV atom (Si)



Electron (-)




Hole (+) (left by the electron)

bad conductor

Semiconductor devices (doped) ($T=0$)

n-type

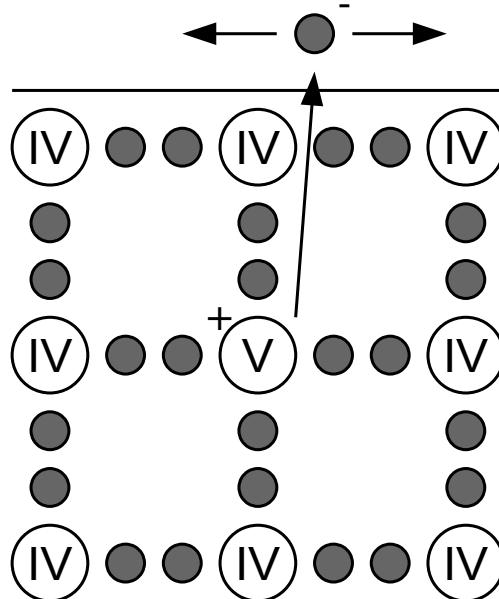


good conductor

● Electron (-)

○ Hole (+) (left by the electron)

p-type

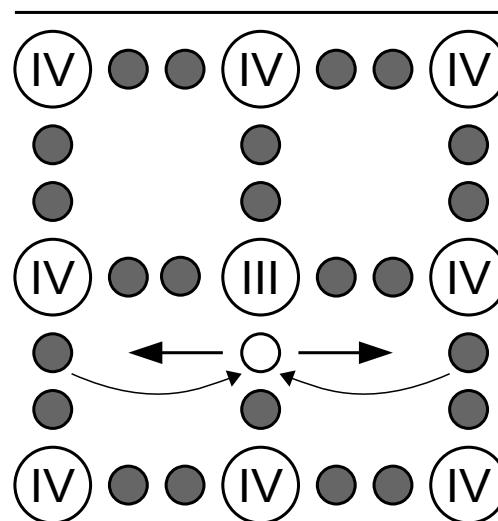

good conductor

● IV Group IV atom (Si)










○ V Group V atom (P, As)

● III Group III atom (B, Ga)








Semiconductors nice properties

- Conductance depends on temperature, light, etc.
 - Temperature sensors
 - Light sensors
 - Solar cells
 - ...
- Conductance can be controlled by doping.
- Type of carrier (+ or -) can be controlled by doping (P or N).
- Nice devices can be created by combining different types of semiconductors (P+N).
 - Electrical: selective conductivity.
 - Optical: light emission.

Diodes and Light-Emitting Diodes (LED's)

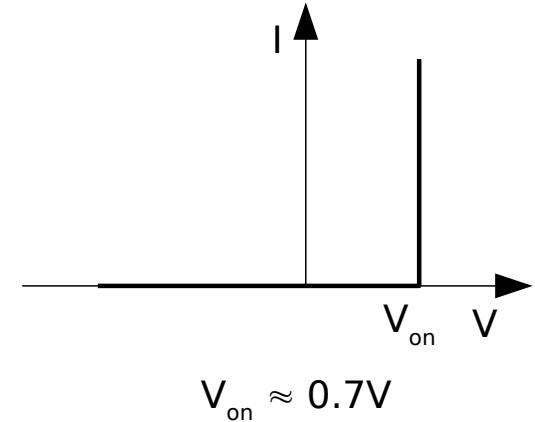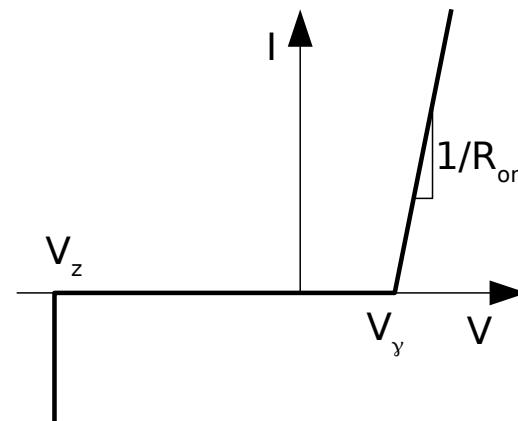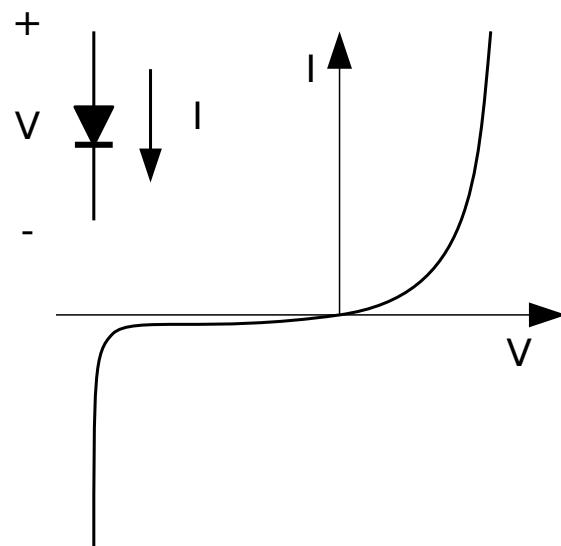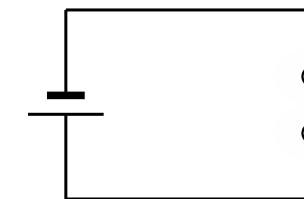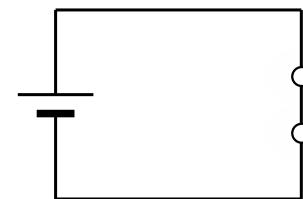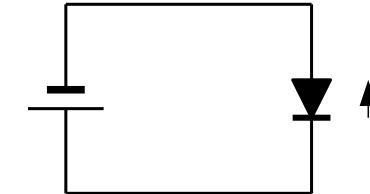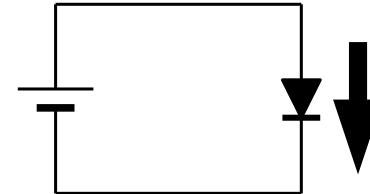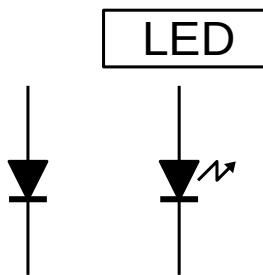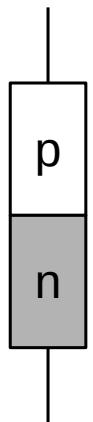


Bipolar transistor

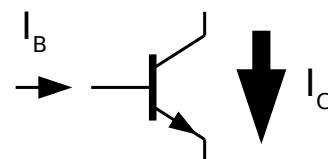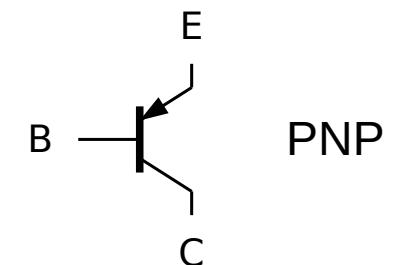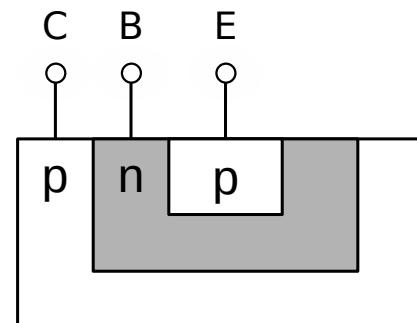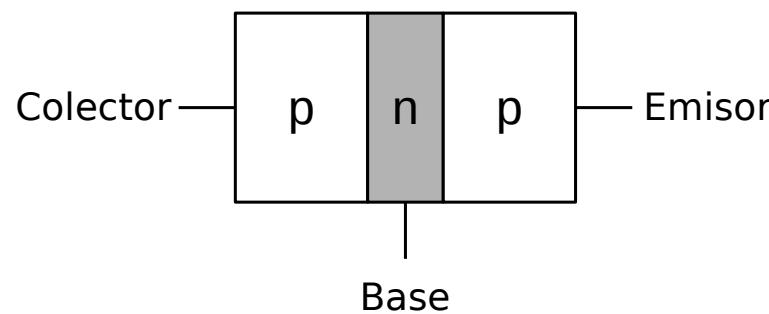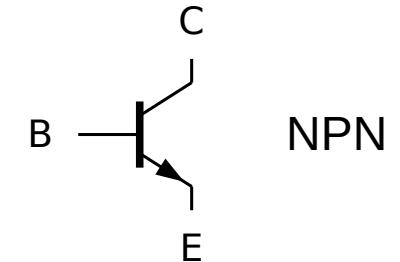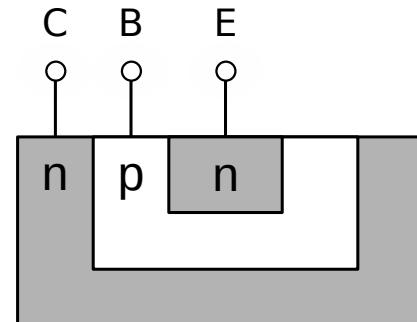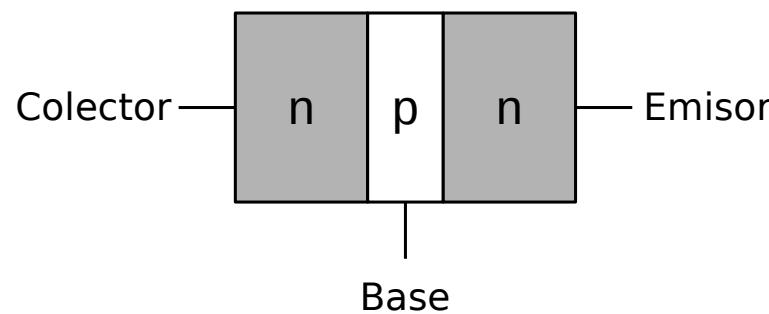

$$I_C = \beta I_B$$
$$\beta \approx 100$$


A small current through B-E allows a big current to flow through C-E.
Direct use: amplifier.

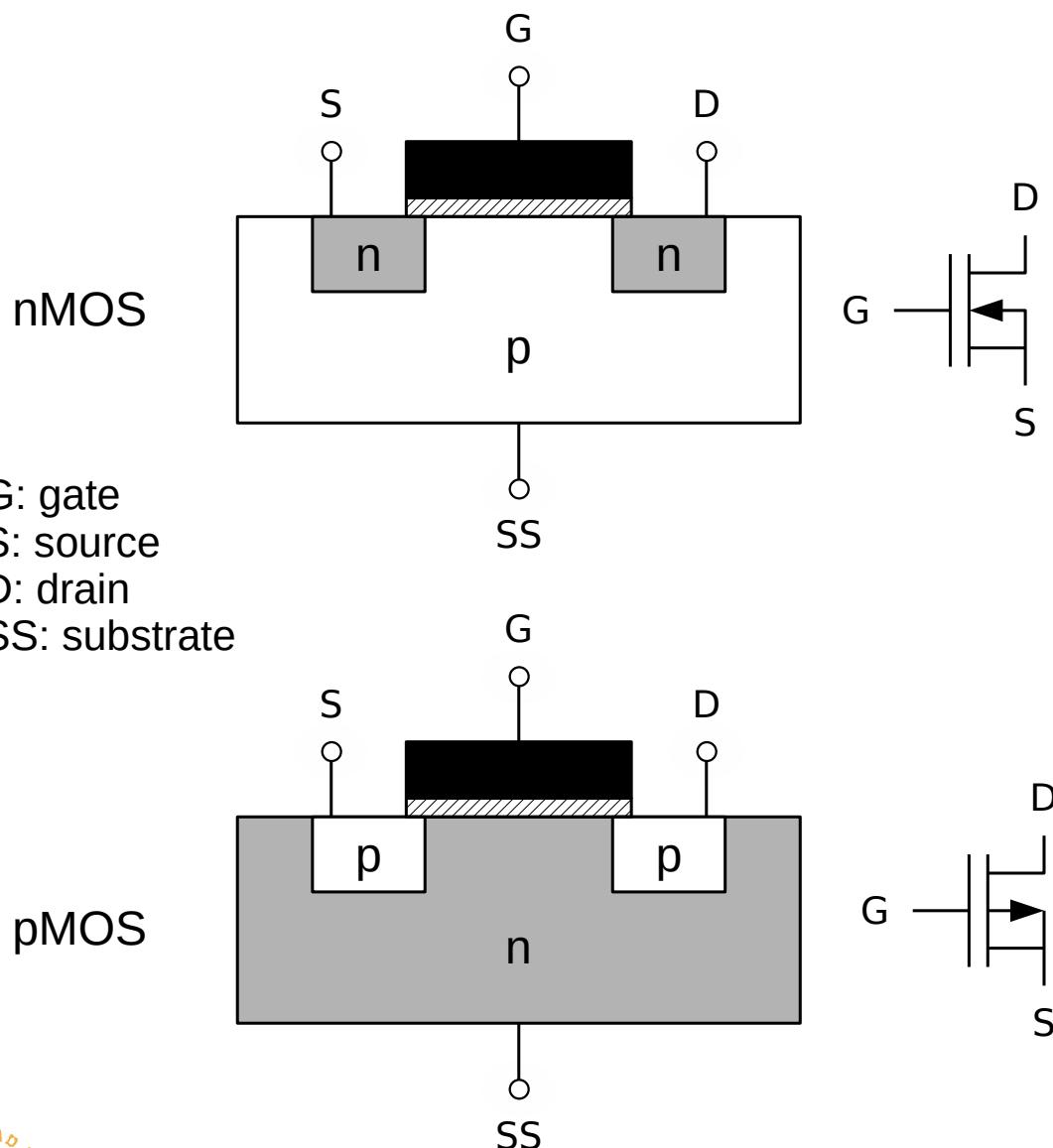Field Effect Transistors (E.g.: MOSFET's)



G: gate
S: source
D: drain
SS: substrate

Conductor (Poly-Si)
Dielectric (SiO_2)



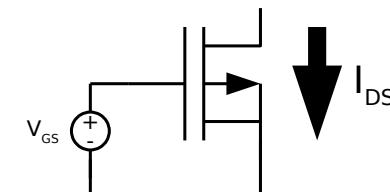


A small voltage between G and S allows a big current to flow from D to S.
Applications: amplifier, sensors, power control, etc.

Transistors demo

$$V = IR \quad I = \frac{V}{R}$$
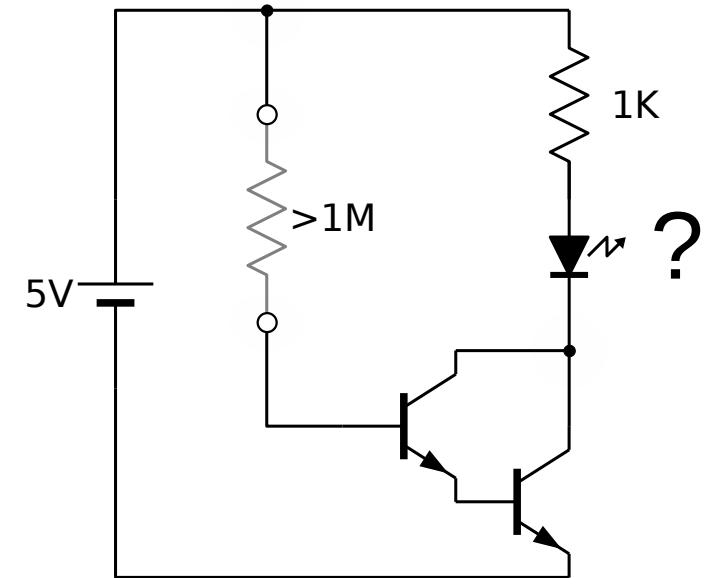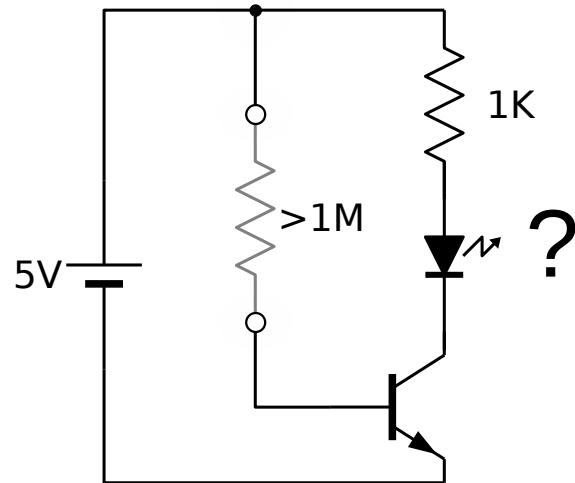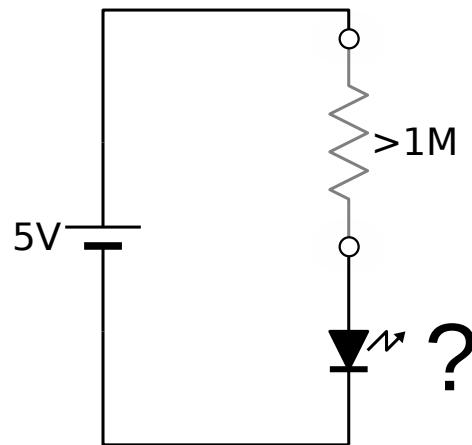
$$I_C = \beta I_B \quad \beta \approx 100$$



$$I_D = I_R \approx 0$$


$$I_D = I_C \approx 100 I_R$$

$$I_D \approx 10000 I_R$$

Electronic technology

- Discrete components
 - Devices are fabricated one by one
 - Normally, they are soldered in printed circuit boards (PCB's)
- Integrated circuits (chips, IC's)
 - Several devices (mostly transistors) are fabricated at the same time over a common substrate.
 - Really big numbers: 10-500 million! devices in the same chip.
 - Most of today's electronics is done as IC's
- Types of IC's
 - Application specific (ASIC)
 - Programmable (E.g. FPGA)




Electronic devices

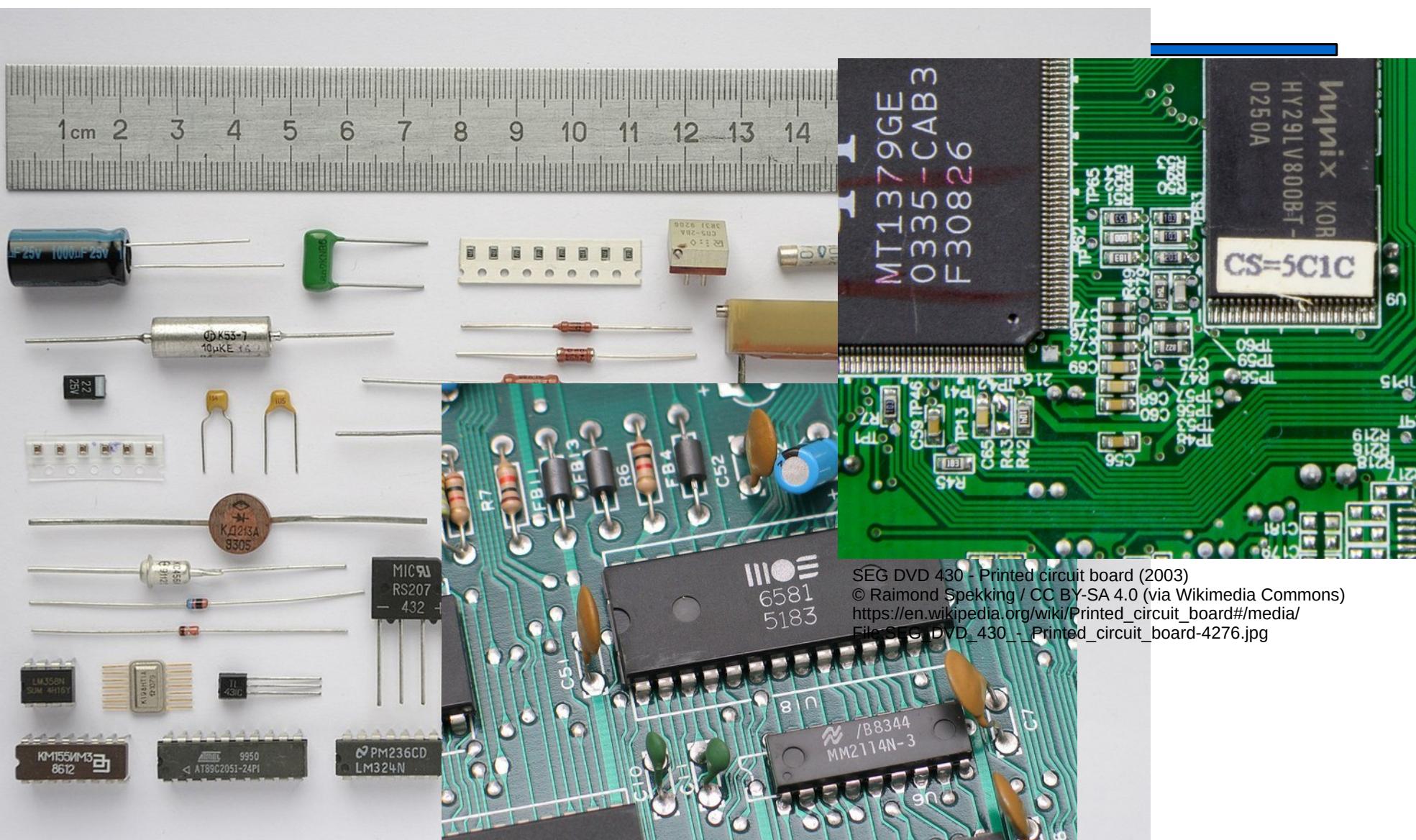

By Kae - Own work, Public Domain
<https://commons.wikimedia.org/w/index.php?curid=655329>

Commodore 64 PCB (1980)
By Christian Taube - Own work, CC BY-SA 2.5,
<https://commons.wikimedia.org/w/index.php?curid=1503038>


Integrated circuits

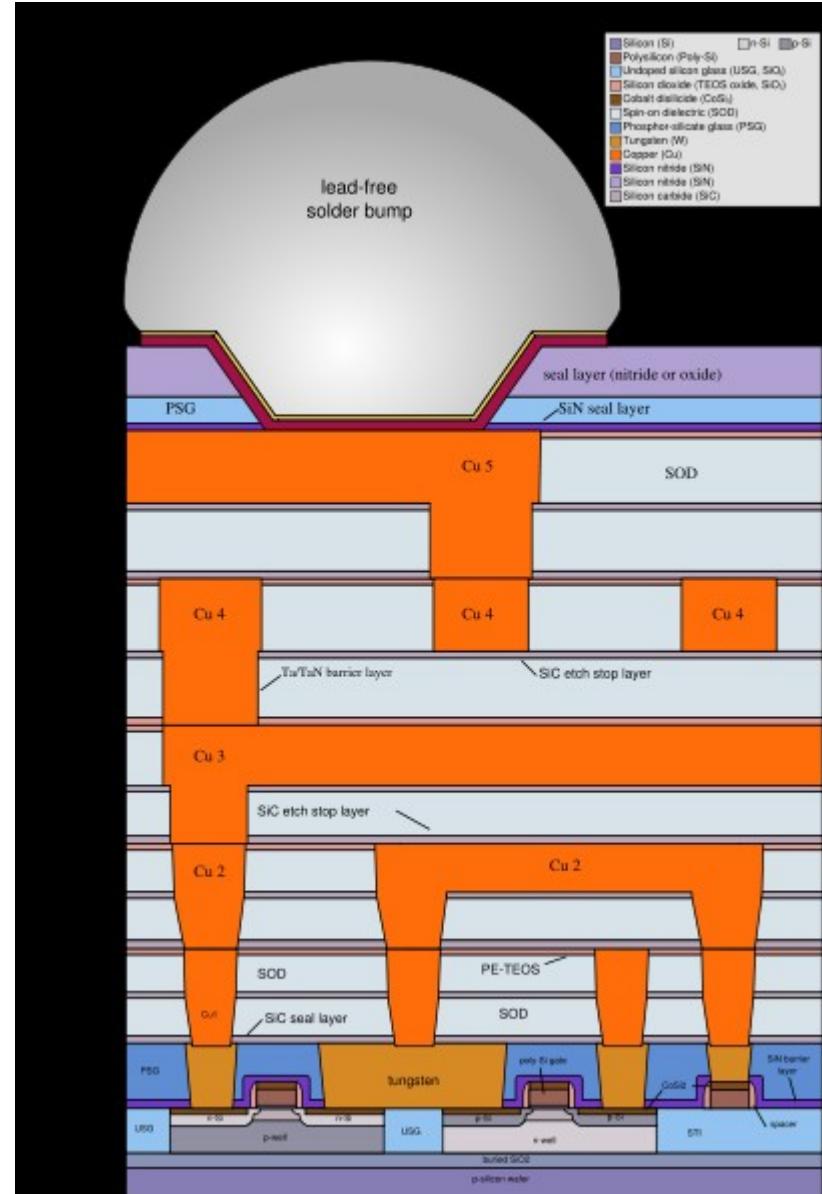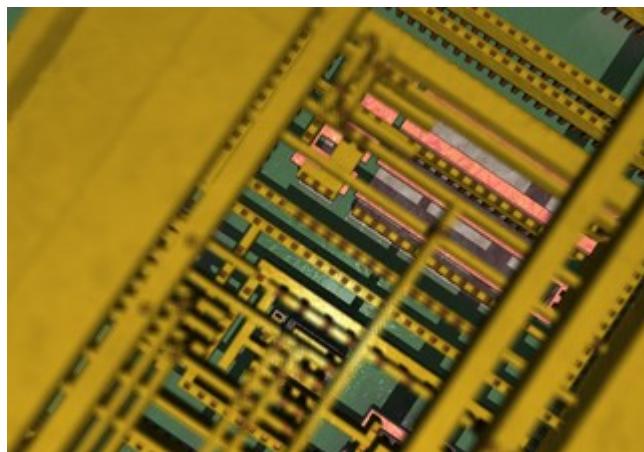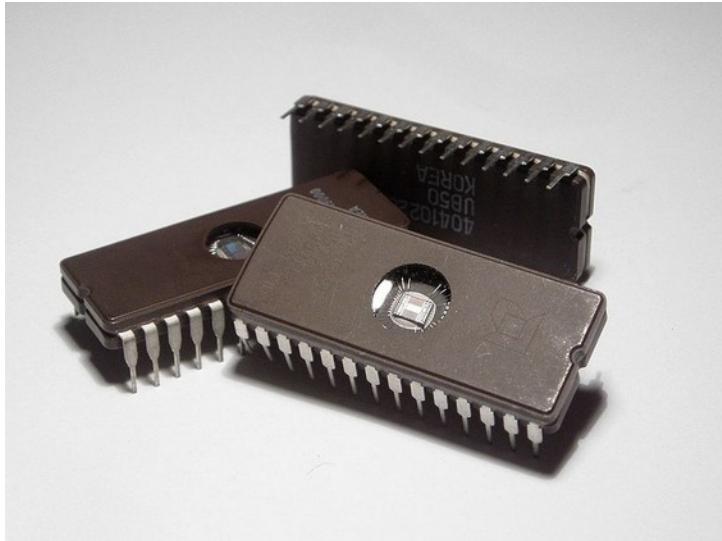

http://en.wikipedia.org/wiki/Integrated_circuit

Integrated circuits. Types



Application Specific IC (ASIC)

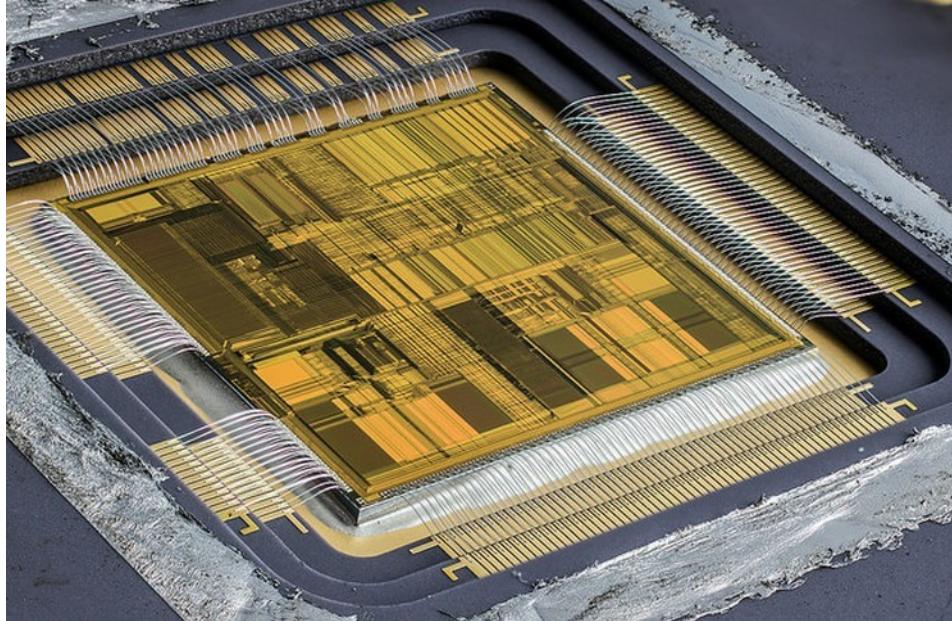

Public domain.
<https://www.flickr.com/photos/130561288@N04/16637740870>

Programmable (ej. FPGA)

Xilinx XC4010-6

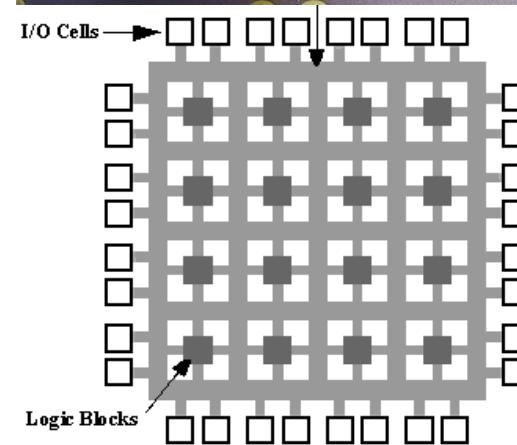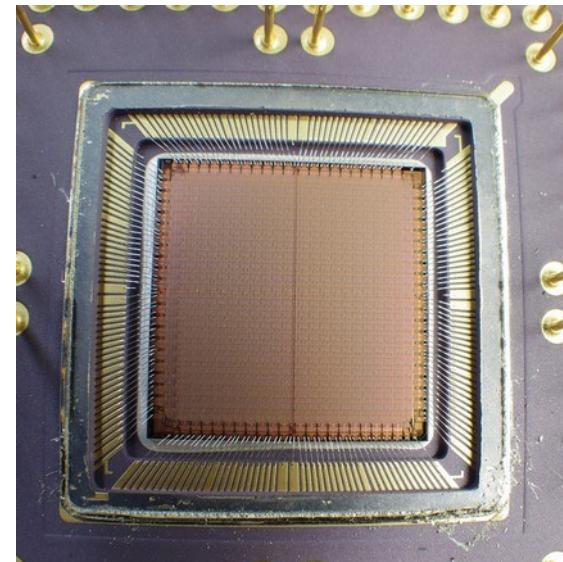

<http://commons.wikimedia.org/wiki/File:Fpga1a.gif>

Xilinx XC4010-6. Public domain.
<https://www.flickr.com/photos/34923408@N07/22054207552/>

Integrated Circuits. Generations

Name	Meaning	Year	No. of	Comment
SSI	Small-scale integration	1964	1 a 10	Military and space applications
MSI	Medium-scale integration	1968	10 a 500	Consumer electronics
LSI	Large-scale integration	1971	500 a 20000	Microprocessors and integrated memories
VLSI	Very large-scale integration	1980	20000 a 1M	Advances microprocessors and memories. Need Design Automation (DA)
ULSI	Ultra-large-scale integration	1984	> 1M	System on Chip (SoC)


Evolution

Vacuum tube



By Kguirnela - Own work, CC BY 3.0
<https://commons.wikimedia.org/w/index.php?curid=3820451>

ENIAC (1946)

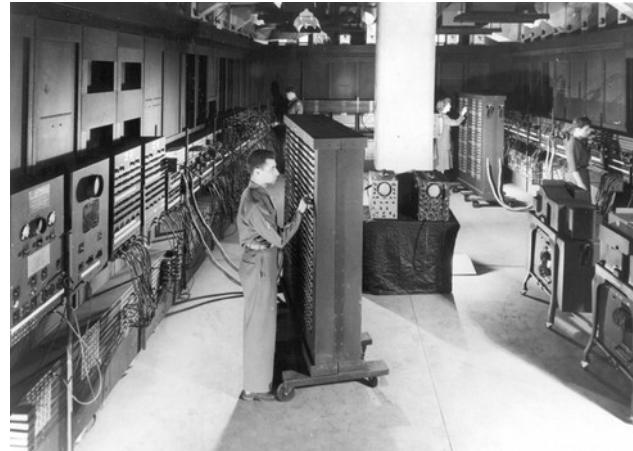

By Unidentified U.S. Army photographer, Public Domain
<https://commons.wikimedia.org/w/index.php?curid=978770>

Transistors



Integrated Circuit
Intel Pentium IV (~50Mtt)



IBM 360 Model 20 (1966)



By Ben Franske - DM IBM S360.jpg on en.wiki, CC BY 2.5
<https://commons.wikimedia.org/w/index.php?curid=1189162>

Laptop (2018)




By Vostrouser - Own work, CC0
<https://commons.wikimedia.org/w/index.php?curid=47766991>

Moore's Law: The number of transistors on microchips doubles every two years

Our World
in Data

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.

Transistor count

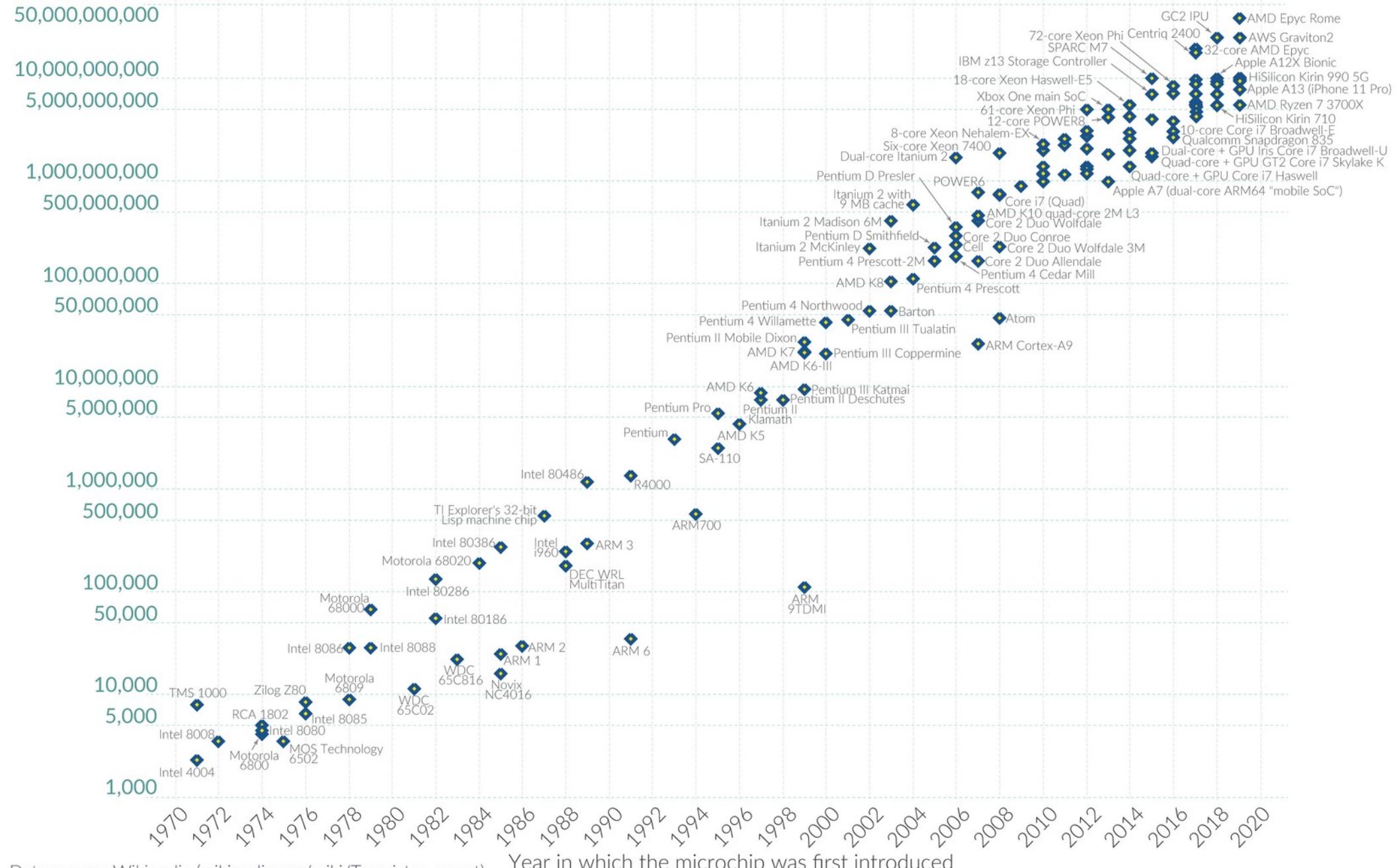

Data source: Wikipedia ([wikipedia.org/wiki/Transistor_count](https://en.wikipedia.org/wiki/Transistor_count))


OurWorldInData.org - Research and data to make progress against the world's largest problems.

Licensed under CC-BY by the authors Hannah Ritchie and Max Roser.


Digital circuits and logic families

- Digital circuits
- Logic gates and logic operators
- Logic families
- Electrical parameters
- Switching parameters

Digital circuits

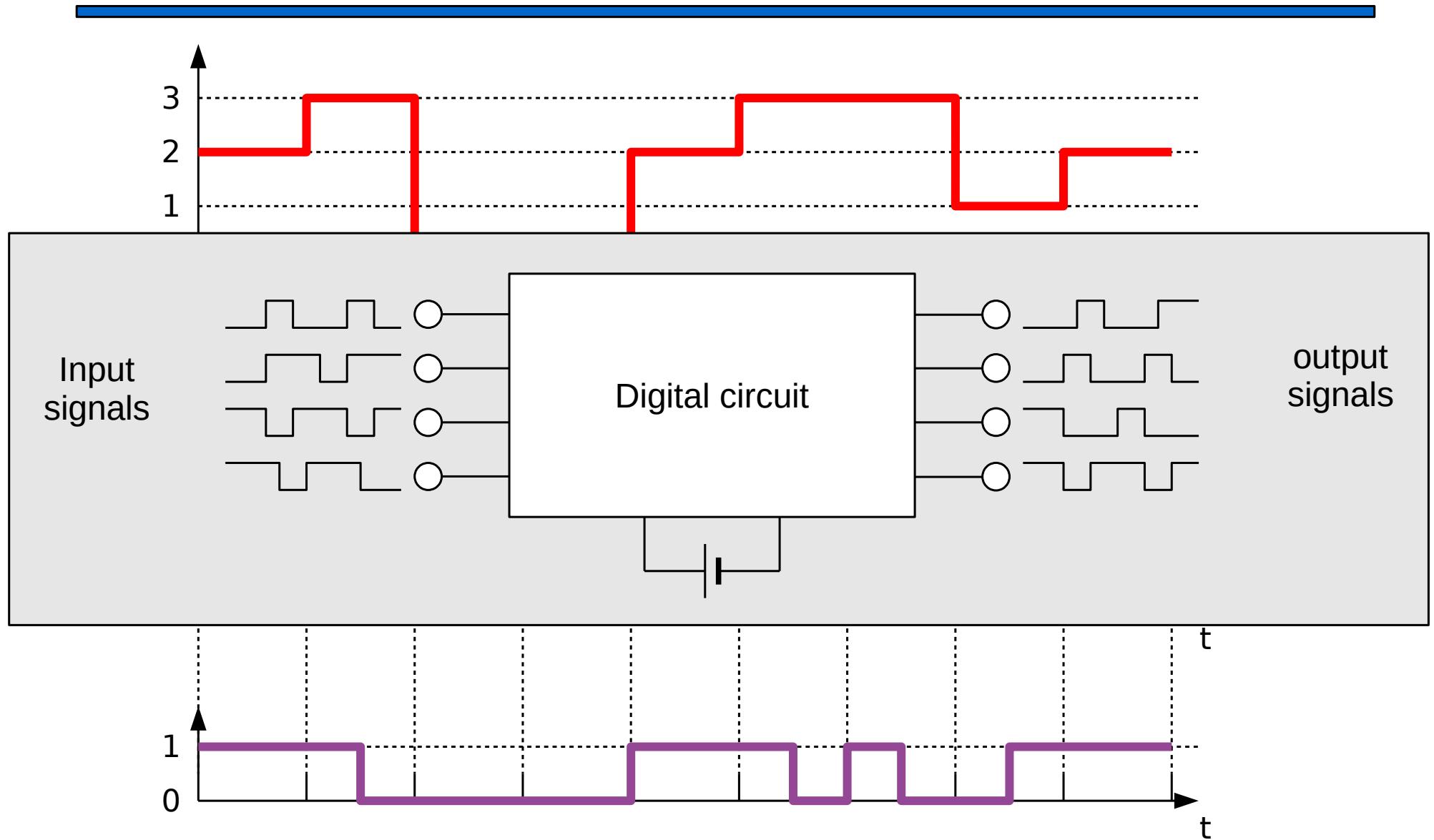


Digital circuits. Logic levels


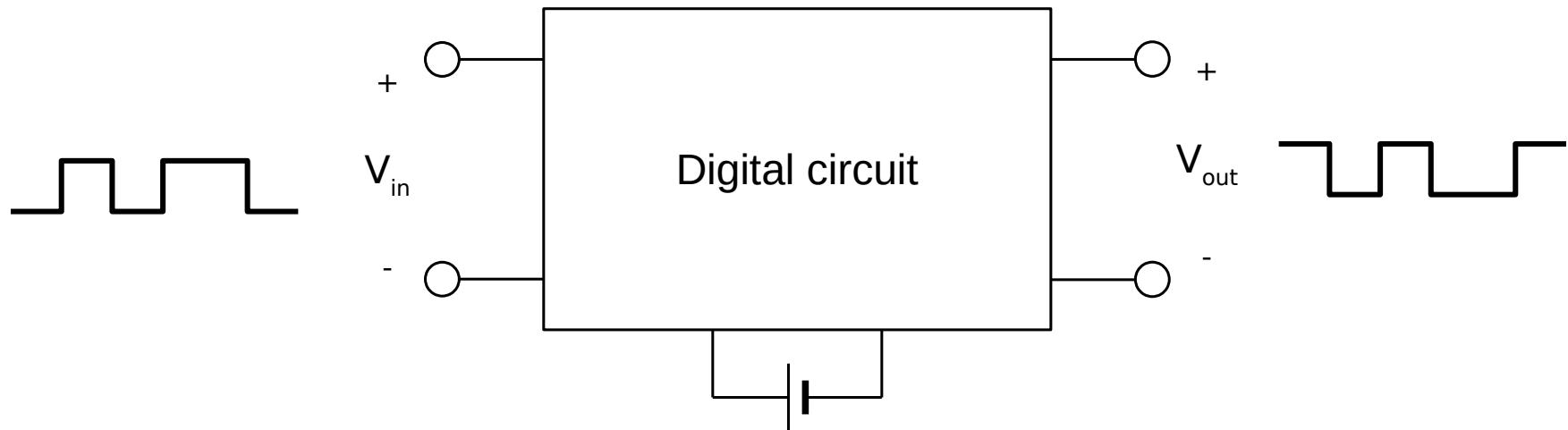


Electric value (V_x) vs. logic value (X)
Ejemplo: 3,3V

V_x	X
~0V	0
~3,3V	1

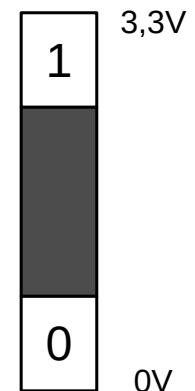


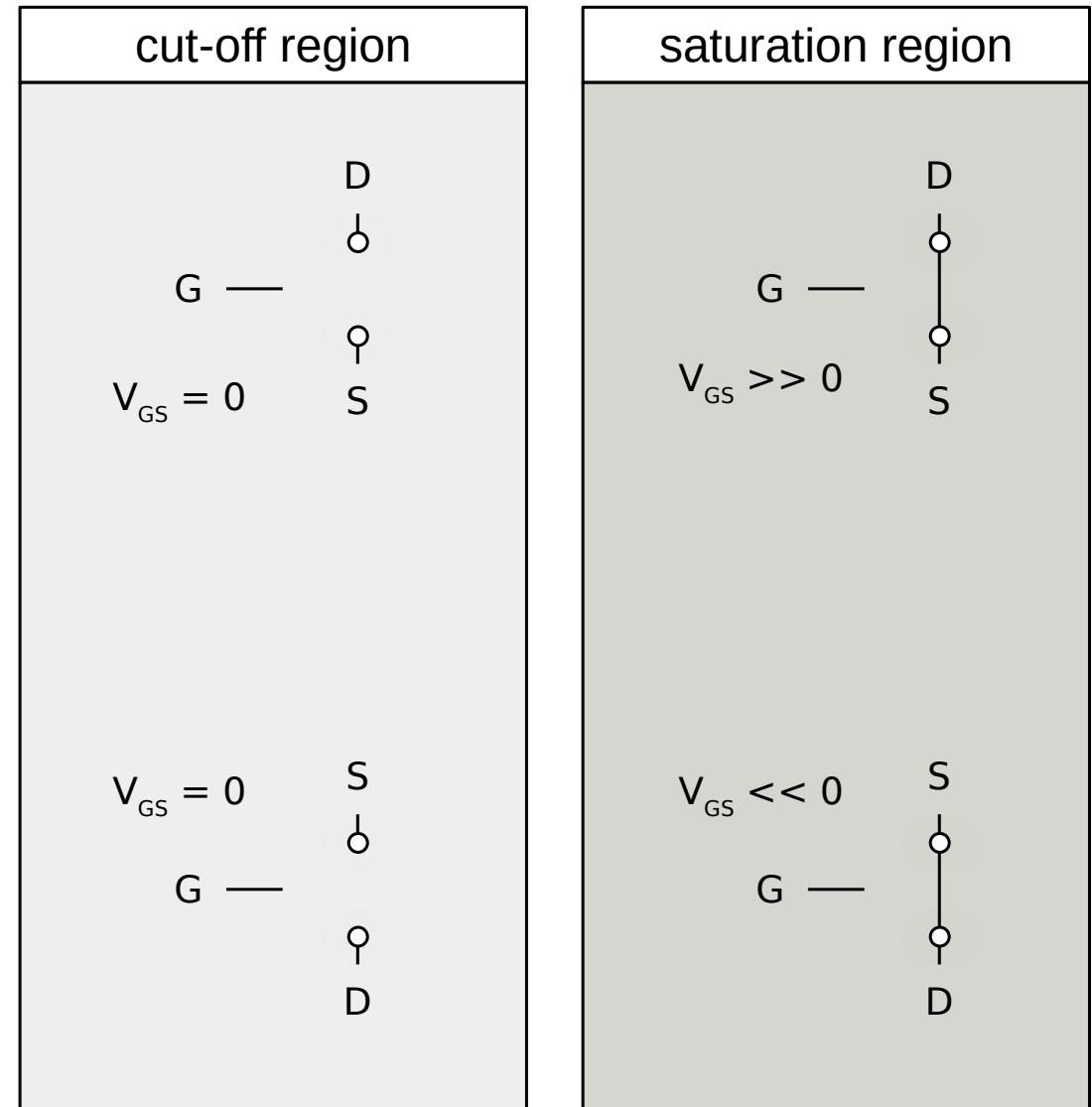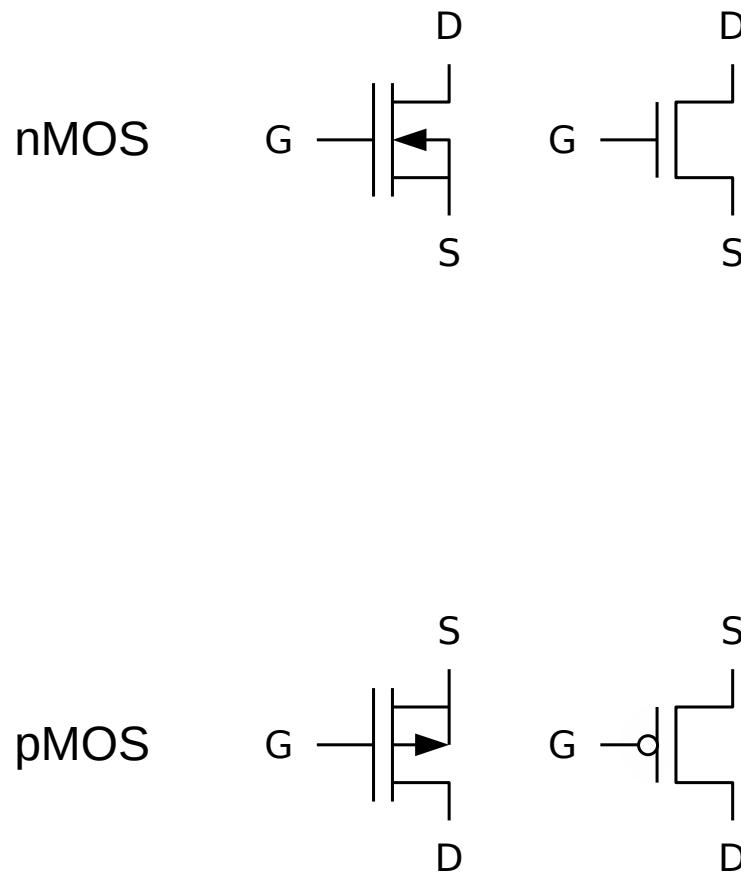Transistors in switching mode (MOS example)




Logic gates. CMOS Inverter


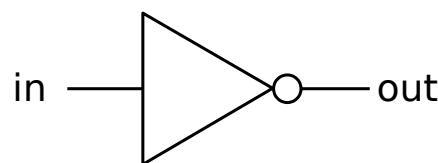
- Logic gates perform simple operations on digital data.
- The simplest (non identical) operation is “inversion”, implemented by the inverter gate.



in	out
0	1
1	0

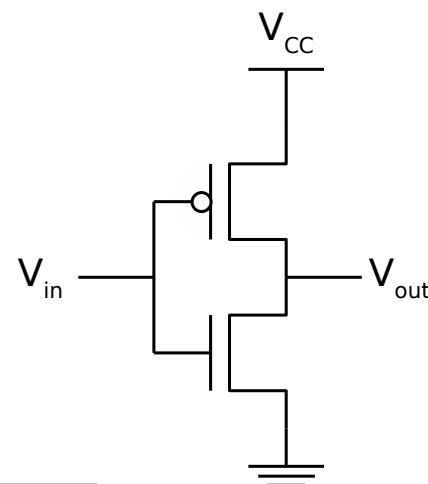


Simulación

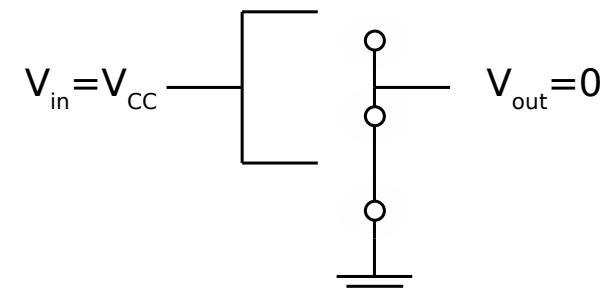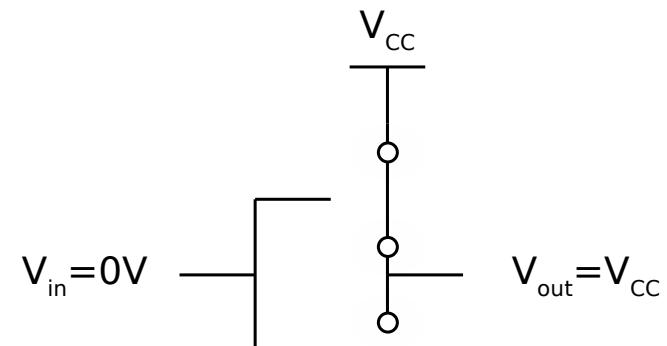


Logic gates and logic operators

AND

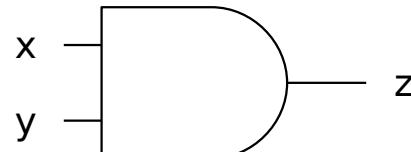


x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

NAND

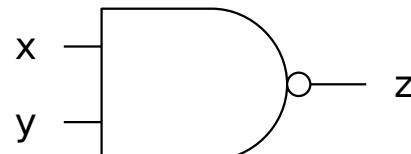


x	y	z
0	0	1
0	1	1
1	0	1
1	1	0

OR

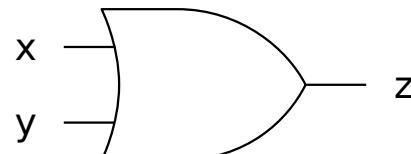

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1


NOR

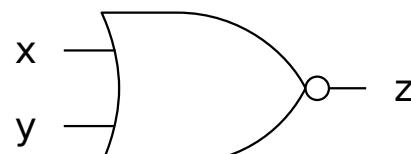

x	y	z
0	0	1
0	1	0
1	0	0
1	1	0


Logic gates and logic operators

XOR

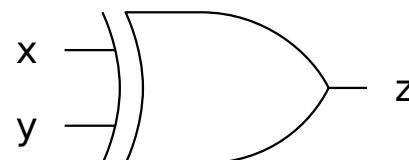

x	y	z
0	0	0
0	1	1
1	0	1
1	1	0



XNOR

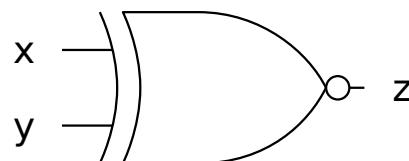

x	y	z
0	0	1
0	1	0
1	0	0
1	1	1



CMOS gates are “naturally inverting”
(INV, NAND, NOR, ...)

Logic gates. CMOS NAND

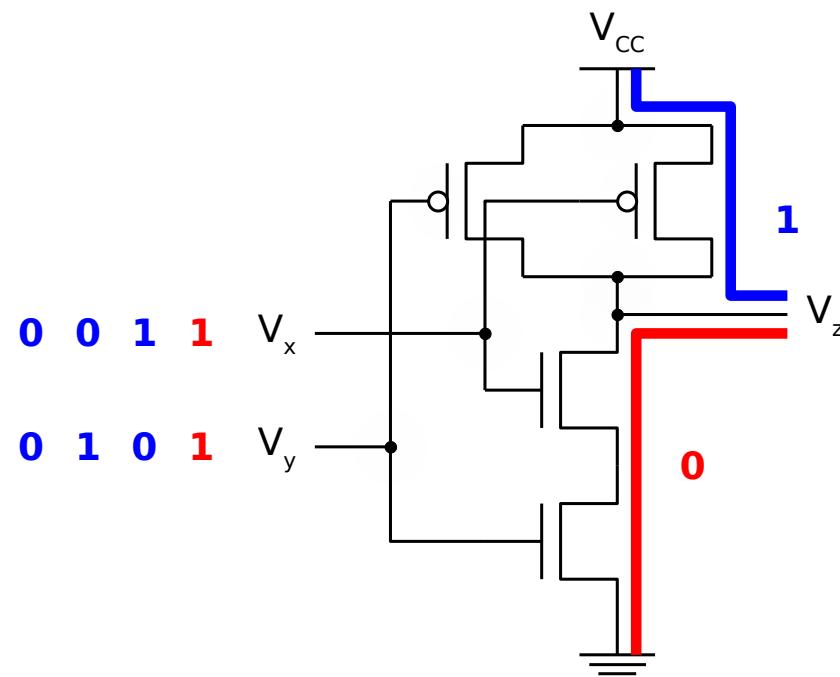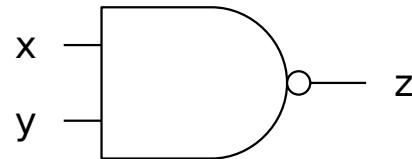

Simulation

Logic Gates. CMOS NOR

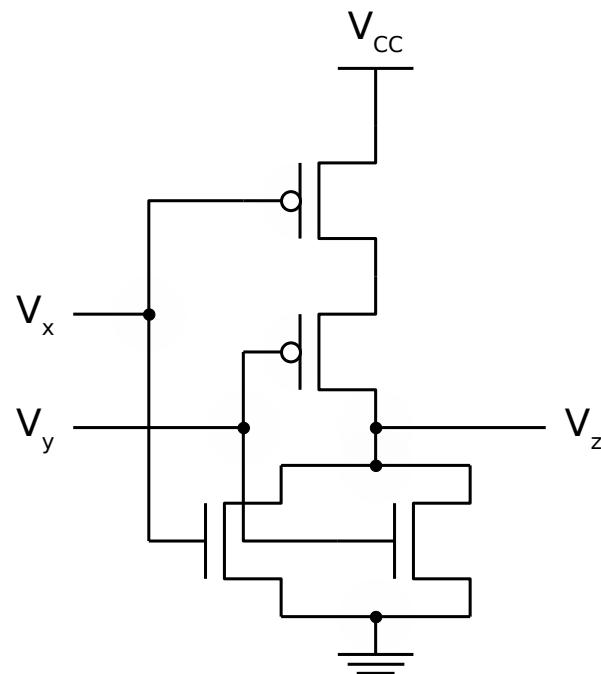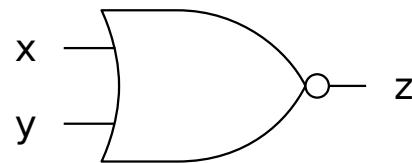


Simulation

Examples: digital interface

- Simple digital signal generation
 - Switch
 - Push button
 - Variable resistance sensor:
 - light, temperature, humidity, etc.
 - Sensor sensitivity adjustment
- Simple digital signal perception
 - LED + resistor
 - Buzzer
 - Etc.

Switch with pull-down resistor

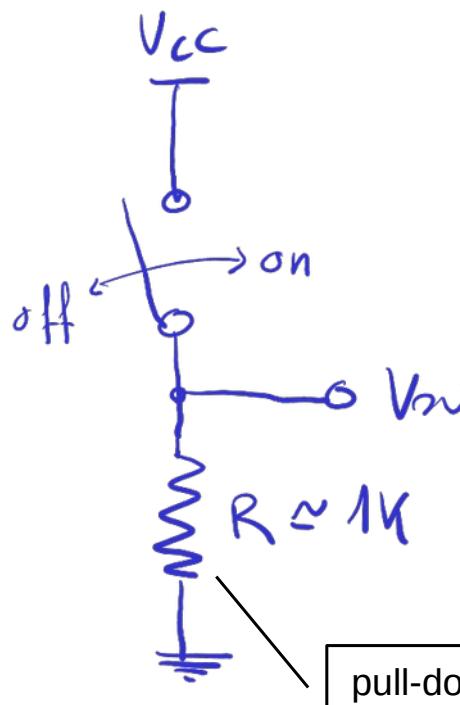


on: $V_{out} = V_{CC}$ (logic 1)
off: $V_{out} = 0V$ (logic 0)

- Pull-down resistor:

- Forces V_{out} low when the switch is off.
- Prevents V_{out} node from being disconnected (floating).
- The voltage in floating nodes may change without control: interferences, radiation, etc.

Simulation

Push button with pull-up resistor

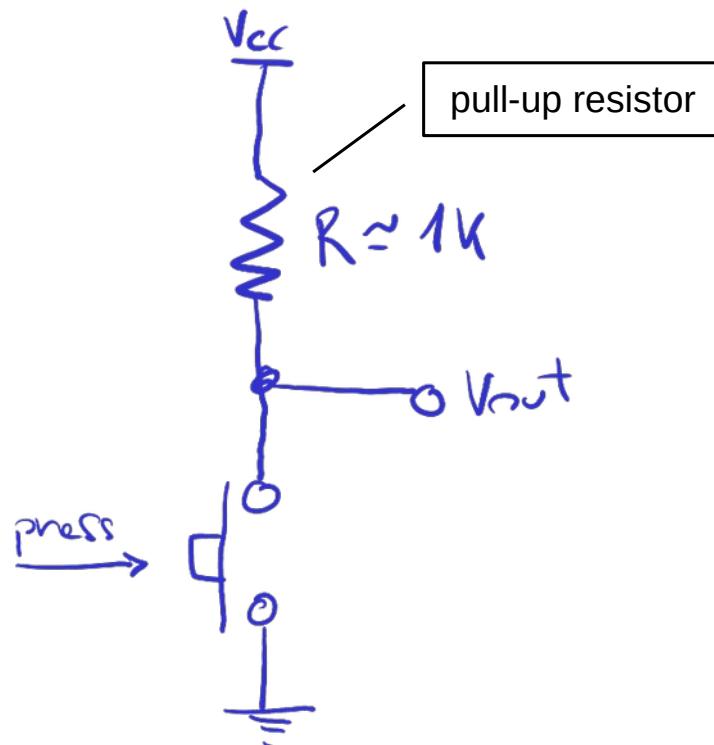


press: $V_{out} = 0V$ (logic 0)
release: $V_{out} = V_{CC}$ (logic 1)

- Pull-up resistor:

- Forces V_{out} high when the button is not pressed.
- Prevents V_{out} node from being disconnected (floating).

Simulation

SPDT switch with RC dumping circuit

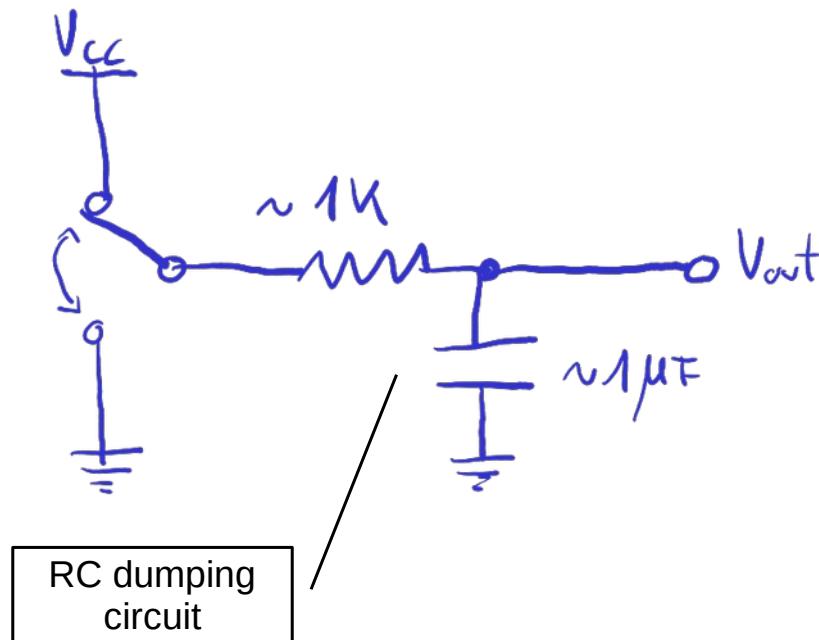

- Dumping circuit
 - Keeps the output voltage while the switch is changing.
 - Dump switch “bounces”.


up: $V_{out} = V_{CC}$ (logic 1)
down: $V_{out} = 0V$ (logic 0)

Simulation

Example

- Simple alarm system with a NAND gate
 - On/off switch
 - Contact sensor
 - Alarm indicator (LED, etc.)
- Modifications
 - Alarm when sensor is off
 - Activate something bigger
 - Relay
 - Light
 - Engine
 - ...

x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

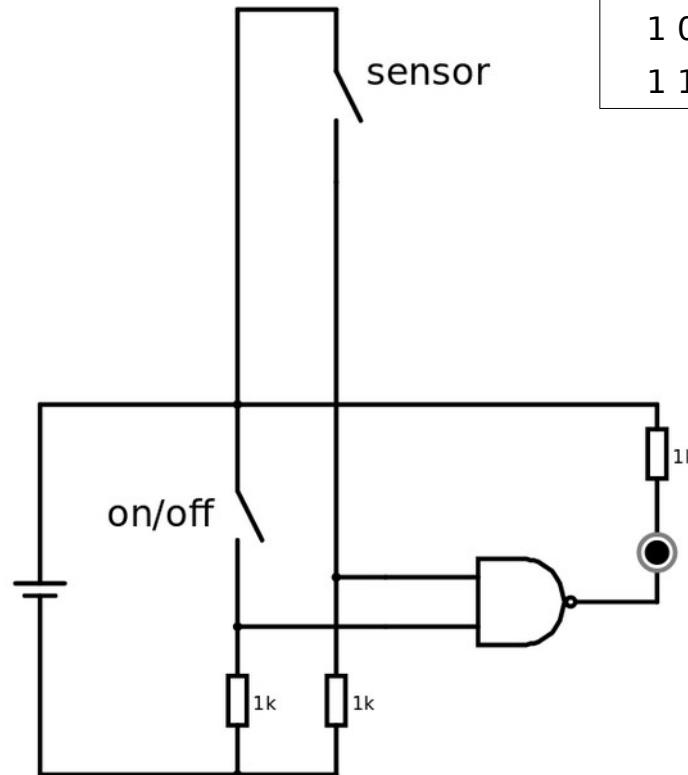

Simulation

Logic families





- Logic gates are fabricated using different technologies (Bipolar, CMOS, ...) and different techniques.
- Logic family: set of gates sharing the same technology and similar design techniques
 - Gates in a family are compatible: will operate correctly when connected to each other.
 - Share similar electrical and dynamic parameters.
- Some logic families are compatible with others.
- Specially relevant when working with SSI and MSI devices (7400 series)

Logic families

- Bipolar
 - ECL (Emitter-coupled-logic, 1962): first logic family available in integrated circuits.
 - DTL (Diode-Transistor-Logic, 1962).
 - RTL (Resistor-Transistor-Logic, 1963): used in the Apollo guidance computer (first CPU built from IC's).
 - TTL (Transistor-transistor logic): very popular. Many improvements since 1963. E.g. 74 series.
 - LS TTL: very popular low-power variant.
- CMOS
 - E.g. HC logic. Compatible with TTL. E.g. 74HC series.
 - Most extended technology nowadays in IC's.
 - Better noise margins, lower static consumption, cheaper, but slower.
- BiCMOS
 - Combines CMOS inputs with TTL drivers.
 - Includes various logic families.

Logic families

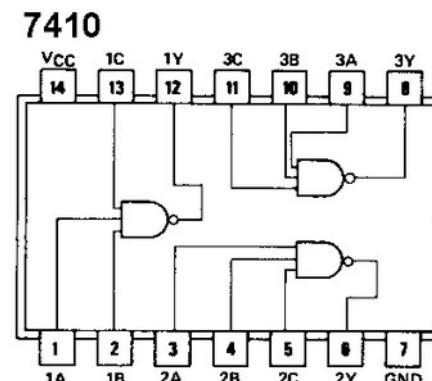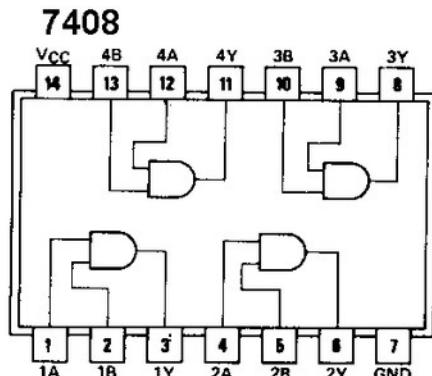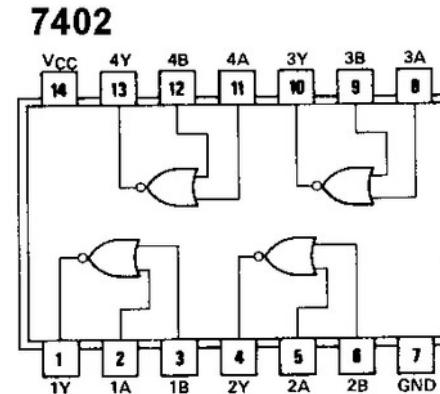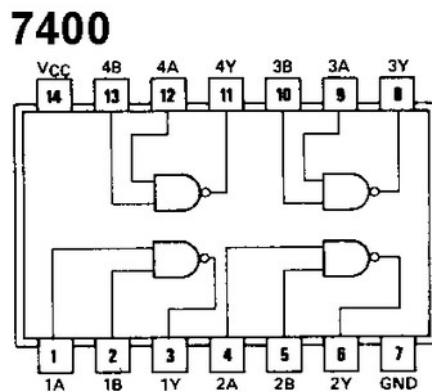- 7400 series
 - Very popular as SSI and MSI devices in education
 - Initially a TTL family, there exist various compatible logic families in various technologies.



Electrical parameters

- Supply voltage (V_{CC})
- Logic levels
 - High and low
 - Input and output
 - Allow noise margin calculations
- Maximum current
 - Input (I_{IL}, I_{IH}). Lower is better.
 - Output (I_{OL}, I_{OH}). Higher is better.
 - Allow *fan-out* calculations.
- Power consumption
 - Static: when signals do not change.
 - Dynamic: when signals change.

Electrical parameters

recommended operating conditions

		SN54AS04			SN74AS04			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
V _{CC}	Supply voltage	4.5	5	5.5	4.5	5	5.5	V
V _{IH}	High-level input voltage	2			2			V
V _{IL}	Low-level input voltage			0.8			0.8	V
I _{OH}	High-level output current			-2			-2	mA
I _{OL}	Low-level output current			20			20	mA
T _A	Operating free-air temperature	-55		125	0		70	°C

electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST CONDITIONS	SN54AS04			SN74AS04			UNIT
		MIN	TYP [§]	MAX	MIN	TYP [§]	MAX	
V _{IK}	V _{CC} = 4.5 V, I _I = -18 mA			-1.2			-1.2	V
V _{OH}	V _{CC} = 4.5 V to 5.5 V, I _{OH} = -2 mA	V _{CC} - 2			V _{CC} - 2			V
V _{OL}	V _{CC} = 4.5 V, I _{OL} = 20 mA		0.35	0.5		0.35	0.5	V
I _I	V _{CC} = 5.5 V, V _I = 7 V			0.1			0.1	mA
I _{IH}	V _{CC} = 5.5 V, V _I = 2.7 V			20			20	µA
I _{IL}	V _{CC} = 5.5 V, V _I = 0.4 V			-0.5			-0.5	mA
I _{O†}	V _{CC} = 5.5 V, V _O = 2.25 V	-30	-112	-30	-112			mA
I _{CCH}	V _{CC} = 5.5 V, V _I = 0		3	4.8		3	4.8	mA
I _{CCL}	V _{CC} = 5.5 V, V _I = 4.5 V		14	26.3		14	26.3	mA

§ All typical values are at V_{CC} = 5 V, T_A = 25°C.

† The output conditions have been chosen to produce a current that closely approximates one half of the true short-circuit output current, I_{OS}.

Electrical parameters

recommended operating conditions (see Note 4)

		SN54LS00			SN74LS00			UNIT
		MIN	NOM	MAX	MIN	NOM	MAX	
V_{CC}	Supply voltage	4.5	5	5.5	4.75	5	5.25	V
V_{IH}	High-level input voltage	2			2			V
V_{IL}	Low-level input voltage			0.7			0.8	V
I_{OH}	High-level output current			-0.4			-0.4	mA
I_{OL}	Low-level output current			4			8	mA
T_A	Operating free-air temperature	-55	125	0	0	70	°C	

NOTE 4: All unused inputs of the device must be held at V_{CC} or GND to ensure proper device operation. Refer to the TI application report, *Implications of Slow or Floating CMOS Inputs*, literature number SCBA004.

electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)




PARAMETER	TEST CONDITIONS [†]	SN54LS00			SN74LS00			UNIT
		MIN	TYP [‡]	MAX	MIN	TYP [‡]	MAX	
V_{IK}	$V_{CC} = \text{MIN}$, $I_I = -18 \text{ mA}$			-1.5			-1.5	V
V_{OH}	$V_{CC} = \text{MIN}$, $V_{IL} = \text{MAX}$, $I_{OH} = -0.4 \text{ mA}$	2.5	3.4		2.7	3.4		V
V_{OL}	$V_{CC} = \text{MIN}$, $V_{IH} = 2 \text{ V}$	$I_{OL} = 4 \text{ mA}$	0.25	0.4	0.25	0.4		V
		$I_{OL} = 8 \text{ mA}$			0.35	0.5		
I_I	$V_{CC} = \text{MAX}$, $V_I = 7 \text{ V}$			0.1			0.1	mA
I_{IH}	$V_{CC} = \text{MAX}$, $V_I = 2.7 \text{ V}$			20			20	µA
I_{IL}	$V_{CC} = \text{MAX}$, $V_I = 0.4 \text{ V}$			-0.4			-0.4	mA
$I_{OS\$}$	$V_{CC} = \text{MAX}$	-20	-100		-20	-100		mA
I_{CCH}	$V_{CC} = \text{MAX}$, $V_I = 0 \text{ V}$	0.8	1.6		0.8	1.6		mA
I_{CCL}	$V_{CC} = \text{MAX}$, $V_I = 4.5 \text{ V}$	2.4	4.4		2.4	4.4		mA

[†] For conditions shown as MIN or MAX, use the appropriate value specified under recommended operating conditions.


[‡] All typical values are at $V_{CC} = 5 \text{ V}$, $T_A = 25^\circ\text{C}$.

[§] Not more than one output should be shorted at a time.

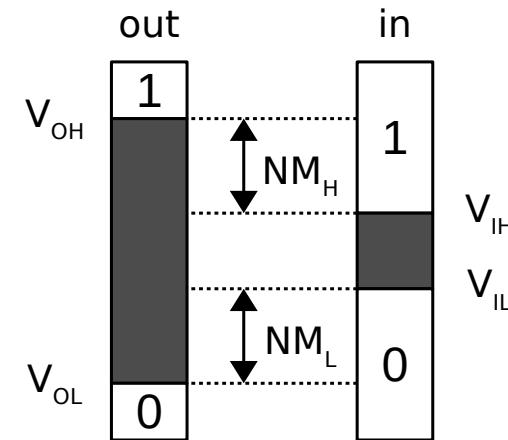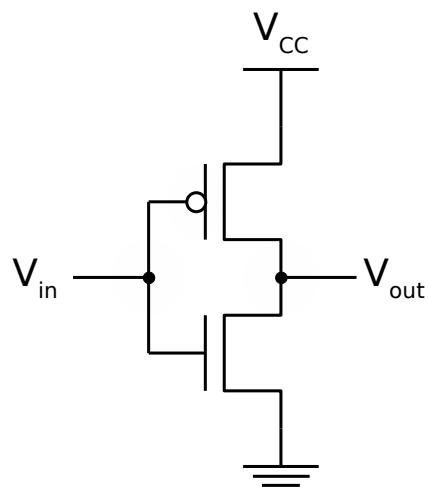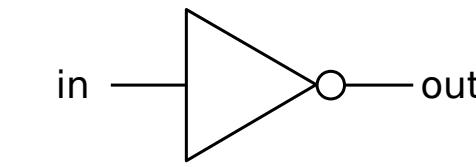Electrical parameters Logic levels and noise margins



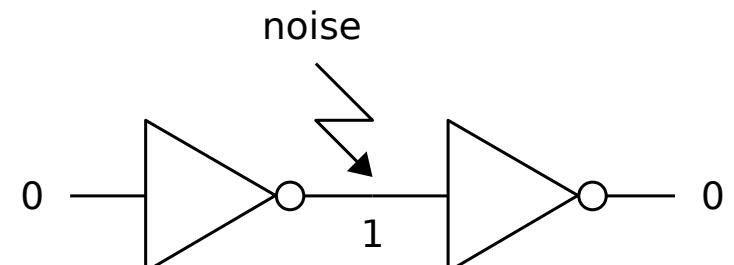
$$NM_L = V_{IL} - V_{OL}$$
$$NM_H = V_{OH} - V_{IH}$$
$$NM = \min(NM_L, NM_H)$$



Simulation

Electrical parameters


Fan-out

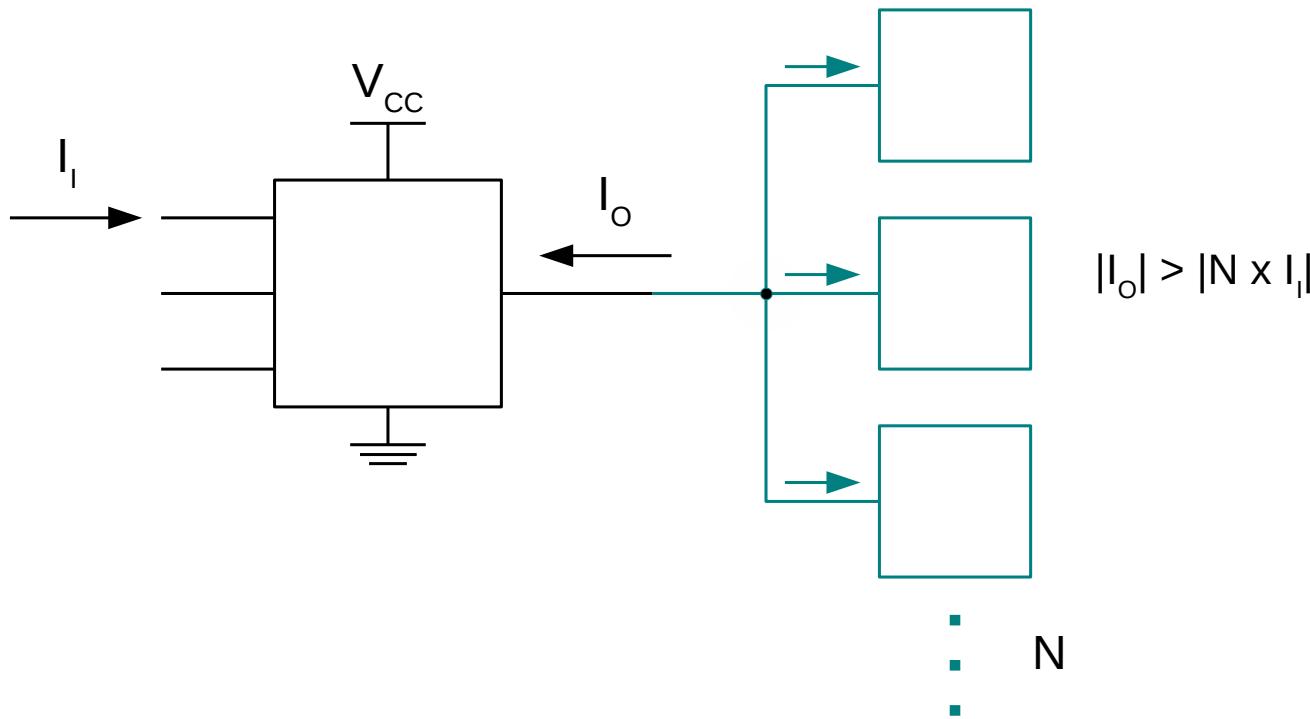

FAN-OUT


Maximum value of N so that $|I_o| > |N \times I_i|$ in both cases (high and low output levels)

The buffer

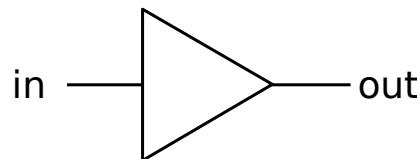

in	out
0	0
1	1

Sample implementation

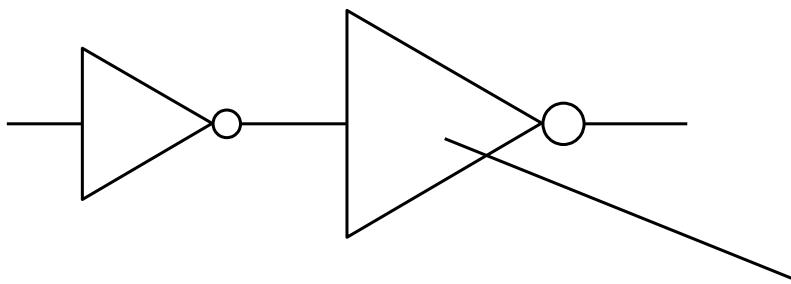

- Implements the “identity” logic operation.
- Used to generate an identical “logic” signal with better “electrical” characteristics:
 - Restoring logic levels.
 - Incrementing output current (and fan-out thereafter).
 - Filtering voltage picks (input buffer).
 - Amplifying voltage and providing more power (output buffer).



An inverter using bigger transistors

Electrical parameters

Power consumption

- Static
- Dynamic
 - Depends on the frequency

$$P = VI$$

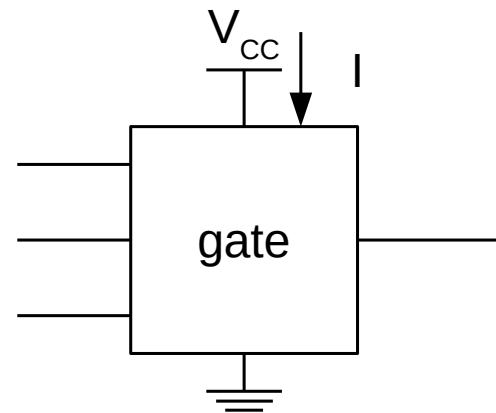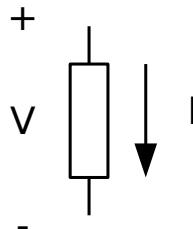

$$P = V_{CC} I$$



Switching parameters

- Transition time: time for a transition to change from:
 - 10% V_{CC} to 90% V_{CC} (rising transition): t_{LH}
 - 90% V_{CC} to 10% V_{CC} (falling transition): t_{HL}
 - Depends on many factors, specially gate's strength and load.
- Propagation delay: time elapsed from the input transition to the output transition.
 - Two types: low-to-high (t_{pLH}) and high-to-low (t_{pHL}).
 - 50% V_{CC} as the reference for transitions.
 - Depends on many factors: gate design, output load (linear), etc.

switching characteristics, $V_{CC} = 5$ V, $T_A = 25^\circ\text{C}$ (see Figure 1)

PARAMETER	FROM (INPUT)	TO (OUTPUT)	TEST CONDITIONS	SN54LS00 SN74LS00			UNIT
				MIN	TYP	MAX	
t_{PLH}	A or B	Y	$R_L = 2\text{ k}\Omega$, $C_L = 15\text{ pF}$	9	15	15	ns
t_{PHL}				10	15	15	

Switching parameters

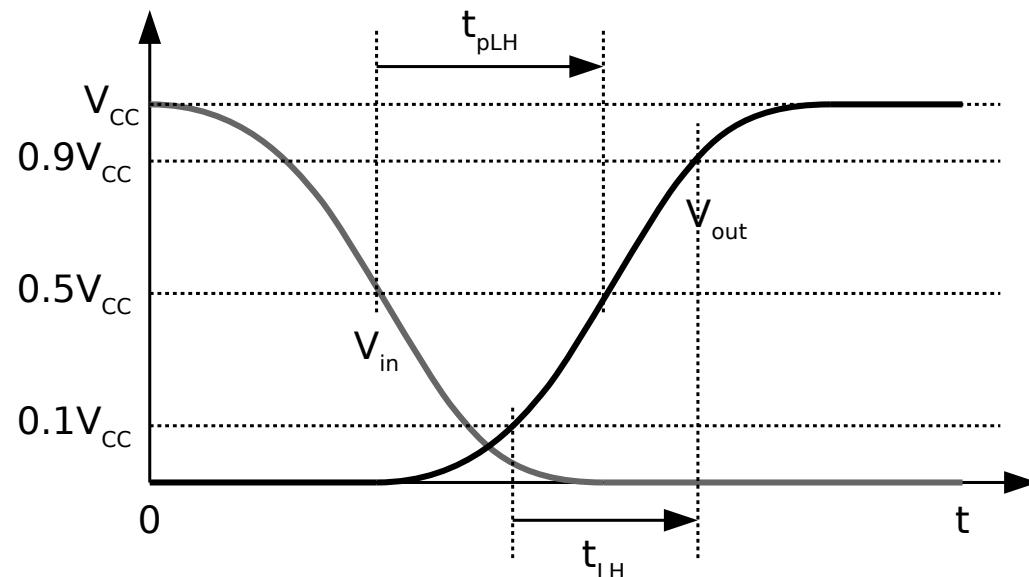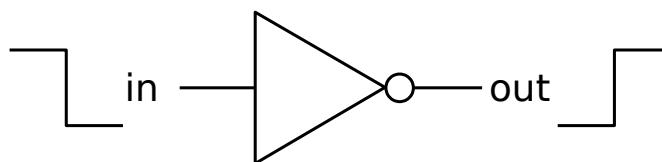

Simulation

Larger propagation delays make digital systems (computers) to run slower (smaller clock frequency)