

Assignment 3

Exercise 1. Obtain the following functions in sum-of-minterms and product-of-maxterms form:

- a) $f_1 + f_2$ b) $f_1 \cdot f_2$ c) $f_1 \oplus f_2$ d) $f_1 \odot f_2$

where $f_1 = \prod(1, 2, 3, 5, 6, 7, 13, 14, 15)$ and $f_2 = \sum(0, 4, 8, 9, 10, 14, 15)$

Exercise 2. Using Karnaugh maps, obtain the minimum sum-of-products and product-of-sums expressions for the following functions:

- a) $f(a, b, c, d) = \sum(0, 4, 6, 7, 10, 12, 13, 14)$
 b) $f(a, b, c, d) = \prod(3, 5, 7, 11, 13, 15)$
 c) $f(a, b, c, d) = \sum(1, 2, 5, 6, 9) + d(10, 11, 12, 13, 14, 15)$
 d) $f(a, b, c, d) = (a\bar{b} + c)(\bar{c}d) + (b + \bar{d})$

Exercise 3. Draw an optimal two-level combinational circuit (plus inverters) corresponding to the functions in sections b and c of the previous exercise. "Optimal" means using the minimum number of gates.


Exercise 4. We need to design a circuit that can compares two 2-bit numbers A (a_1, a_0) and B (b_1, b_0). The circuit should have three binary outputs G, E, L so that:

- $G=1$ if and only if $A > B$
- $E=1$ if and only if $A = B$
- $L=1$ if and only if $A < B$

Design the required circuit using only NAND gates.

Exercise 5. A water tank has a sensor system that provides the water level in the tank with a number from 0 to 12. This number is given as a 4 bit digital signal in natural binary code (x_3, x_2, x_1, x_0). Design a combinational circuit that takes (x_3, x_2, x_1, x_0) as inputs and generates an output signal 'z' which is '1' when the tank level is equal or less than 5 and is '0' otherwise. Make an optimum design using only NOR gates.

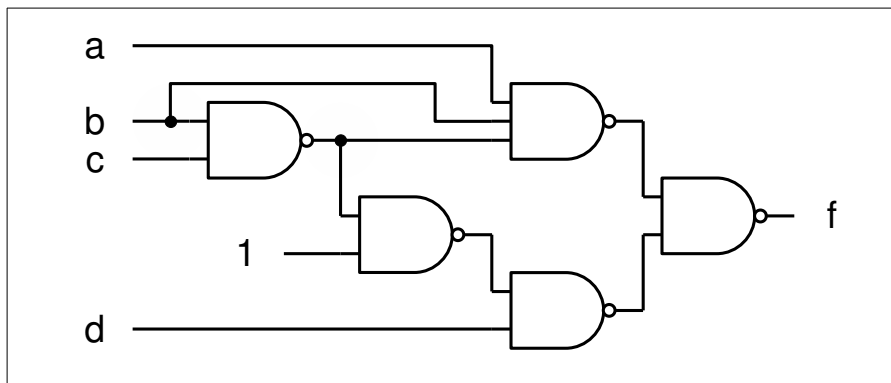Exercise 6. In the circuit depicted below all the gates have the same delay Δ .



- a) Obtain a minimum sum-of-products expression for function f .
 b) Obtain the truth table of f . ¿Can you figure out a possible application for f ?
 c) Determine the waveform of f when $b=d=1$ and a and c change as depicted below. Comment the results.

