
Unit 4. Design of a (Yet Another) Simple Academic Computer

Computer Structure
E.T.S.I. Informática
Universidad de Sevilla

Jorge Juan-Chico <jjchico@dte.us.es> 2021-24

This work is licensed under the Creative Commons Attribution-ShareAlike 4.0 International License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-sa/4.0/> or send a letter to Creative Commons, PO Box 1866, Mountain View, CA 94042, USA.

Some images and other objects are used here according to their license. Follow the reference to the original work for details. Images not referenced are either original work of the author or are in the public domain.

Contents

- Computers: the “What”, “Why” and “How”.
- Basic concepts
- The Yet Another Simple Academic Computer (YASAC)
- YASAC stage 1
- YASAC stage 2
- YASAC stage 3
- YASAC stage 4
- YASAC stage 5
- What's next?

Computers: What, Why and How


- What is a computer?
 - A machine that can do tasks according to a “program”.
 - An algorithm can be expressed in a “program”.
 - They are backed up by strong theoretical results thanks to **Alan Turing** and other people.
 - Useful computers are **Turing-complete**.
- Why are computers so useful?
 - Many problems can be solved by executing an algorithm.
 - The program in modern computers can be easily changed.
 - The computer has become the universal machine.
- How are computers designed and built
 - You will see a simple example in this unit!

Computer architecture design basics

- Instruction Set Architecture
 - Programmers view
 - Links software and hardware (contract)
 - Finality of the computer
 - Human vs compiler friendly
 - Support high-level languages
- Microarchitecture
 - What elements you need to implement the ISA?
 - How to connect them?
- System design
 - Digital system designers wanted!


Stored program computers

Harvard vs Von Neumann architectures

 

Von Neumann

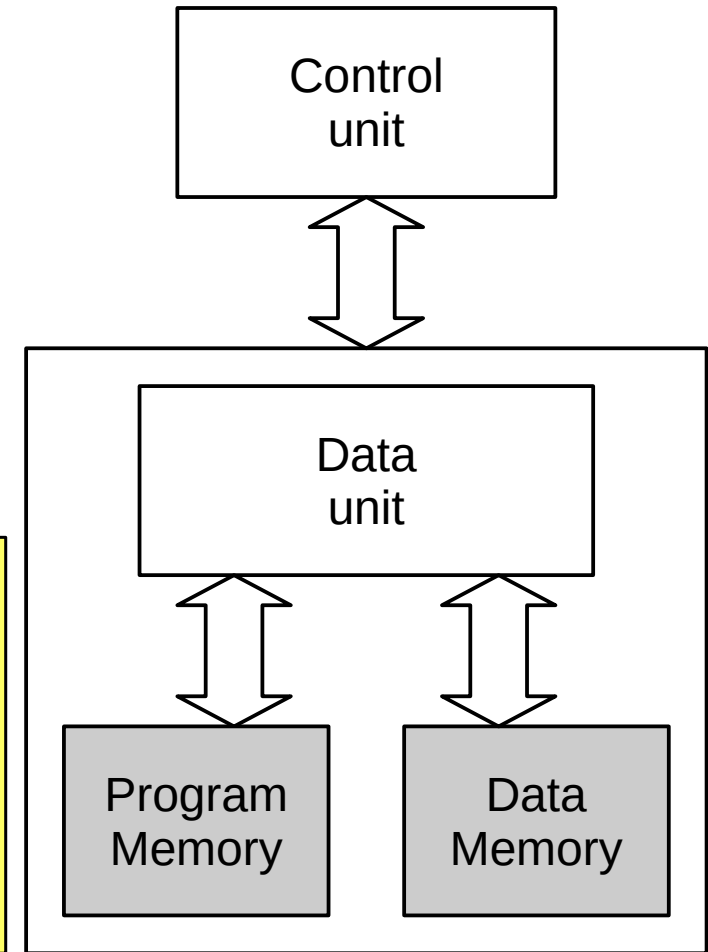- Simpler design.
- Von Neumann's bottleneck.
- Used in most standard computers.



Harvard

- No Von Neumann bottleneck.
- Better program memory protection (can be read-only).
- Used in embedded systems and microcontrollers.

RISC vs CISC

- **Complex Instruction Set Computer (CISC)**
 - Powerful complex instructions that may take many cycles to execute.
 - Saves access to memory to fetch new instructions (good).
 - Difficult to execute various instructions in parallel (bad).
 - Complex system design and resource intensive (bad).
- **Reduced Instruction Set Computer (RISC)**
 - Simple instructions that may execute very quickly (one clock cycle most of the time).
 - Needs more instructions to perform the same task (bad).
 - More instructions consumes more memory (bad).
 - Easy to execute many instructions in parallel through **instruction pipelining** (good).
 - Simpler system design (good).

YASAC

Yet Another Simple Academic Computer

- Academic computer with some realistic characteristics.
- Simple enough to be understood by first-year students.
- Powerful enough to introduce all main computer fundamentals.
- Expandable: it is not a complete and full-featured design.
- Microcontroller-like functionality.
 - ISA inspired by Atmel's AVR family of microcontrollers (the core of the Arduino UNO board and others).
- Easy to model in Verilog.
- Easy to implement in FPGA chips.
- Harvard architecture.
- RISC.

The YASAC is a slightly re-designed version of the CS2010 and CS simple computers used in various courses of the Electronics Technology Department (Universidad de Sevilla), developed by professors and students of the Department along the years.

YASAC development overview

- Stage by stage development.
- Each stage has:
 - A specification: instructions and functionality to implement.
 - Design documentation: drawings, micro-operations, ASM charts, etc.
 - A Verilog model and test bench.
 - An FPGA implementation.
- Each stage builds on the previous one.

YASAC development overview. Stages

- Stage 1
 - Minimal computer. Only program memory. Basic I/O.
- Stage 2
 - Data memory and memory addressing. Memory-mapped I/O.
- Stage 3
 - Jumping and branching instructions.
- Stage 4
 - Logic and status register instructions
- Stage 5
 - Stack and subroutines.
- Stage 6
 - Interrupts.
- Stage 7
 - Writable program memory and boot loader.


We will cover stages 1 to 5.

Improvements can be done at every stage (assignments).


Every stage can be implemented in an FPGA board (labs).

YASAC Stage 1. General specification

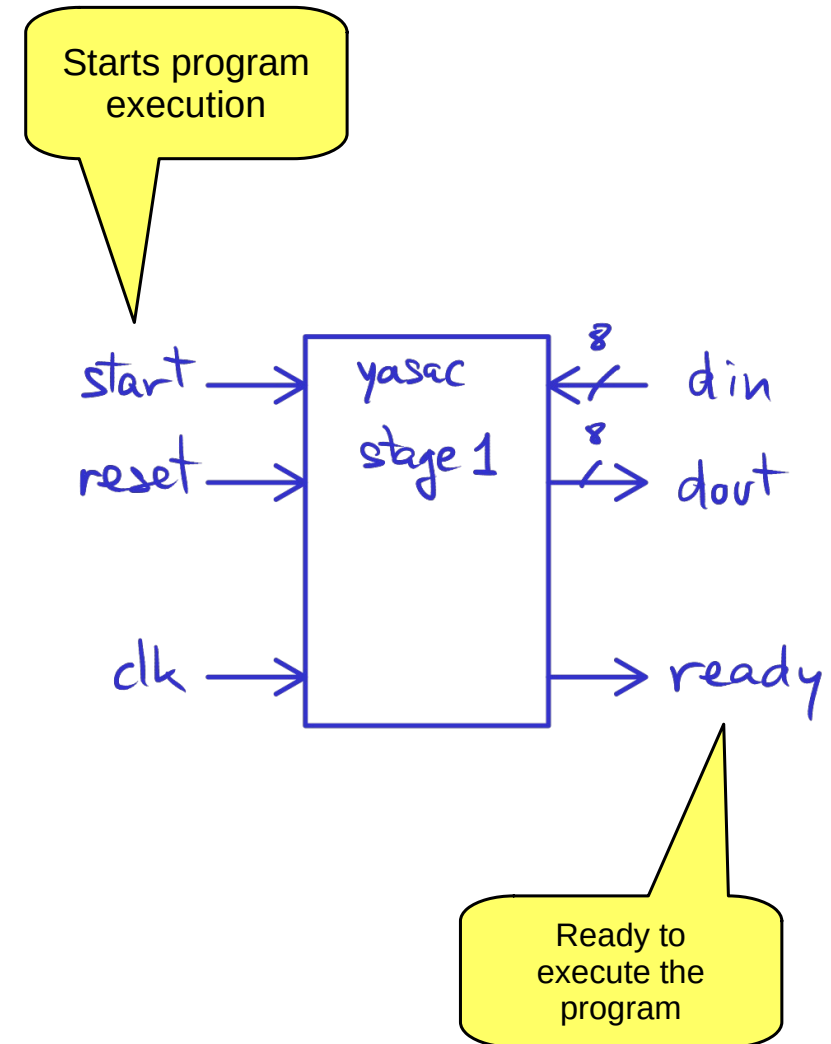- 8-bit data unit and registers
- 8 general purpose registers
 - R0 to R7
- One 8-bit input port and one 8-bit output port
 - din: input port (mapped to R7)
 - dout: output port (mapped to R6)
- Program memory: 256x16
 - ROM memory defined at design time.
- 16-bit instructions




YASAC Stage 1 Board implementation

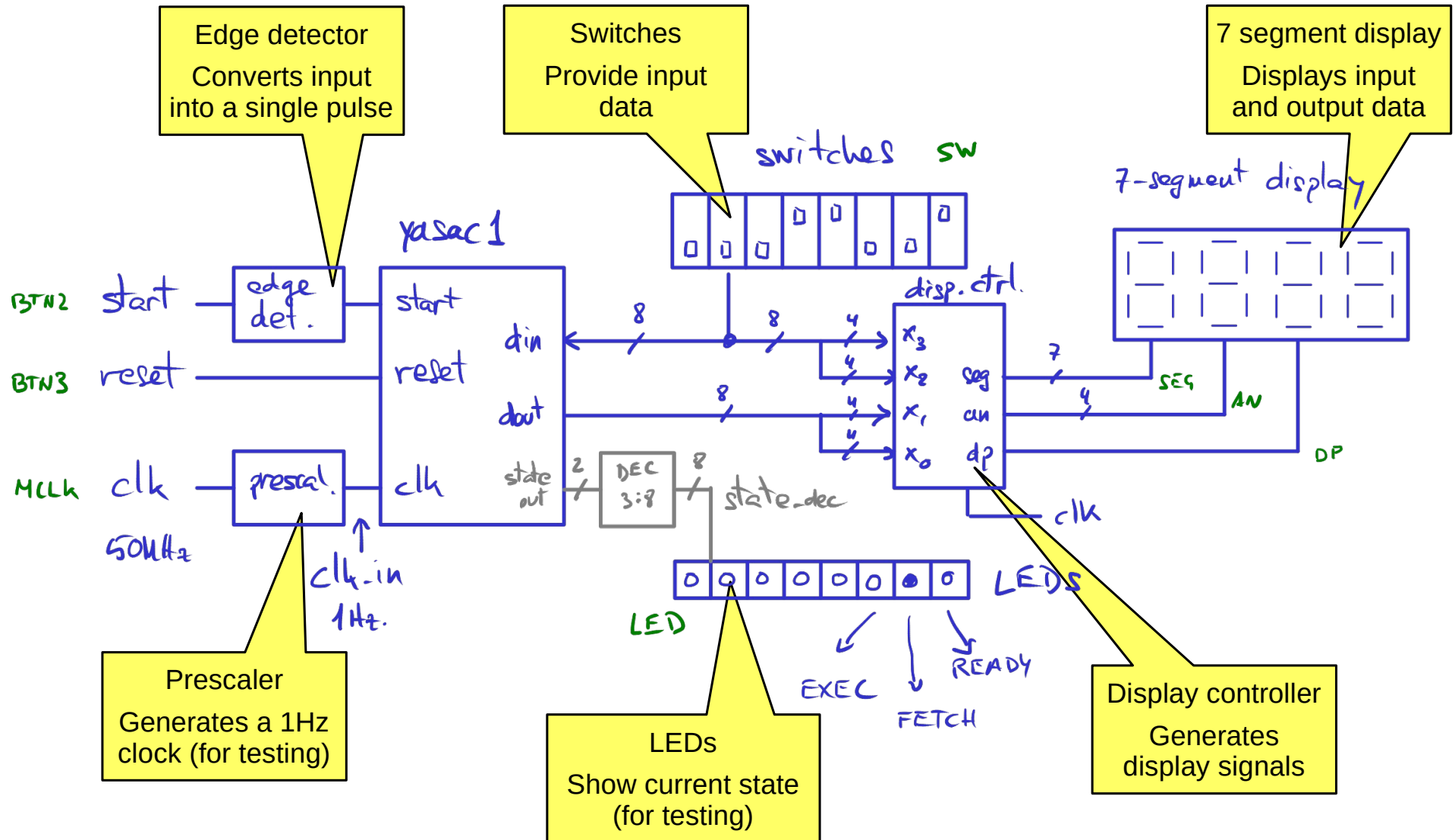


YASAC Stage 1

Instruction Set Architecture

Registers

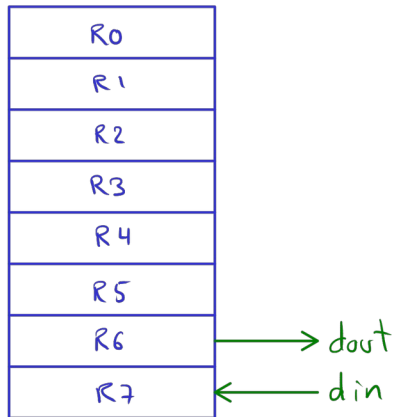

Instruction format

 

Mnemonic code


LDI	0001	(1)
MOV	0010	(2)
ADD	0011	(3)
SUB	0100	(4)
STOP	0101	(5)

Instructions

LDI Ra, k	; Ra ← k
MOV Ra, Rb	; Ra ← Rb
ADD Ra, Rb	; Ra ← Ra + Rb
SUB Ra, Rb	; Ra ← Ra - Rb
STOP	


YASAC Stage 1

Sample program

 

Mnemonic	code
LDI	00001 (1)
MOV	00010 (2)
ADD	00011 (3)
SUB	00100 (4)
STOP	00101 (5)

Instruction format

 

Assembly code

```
MOV R1, R7
MOV R0, R1
ADD R0, R1
LDI R2, 5
SUB R0, R2
MOV R6, R0
STOP
```

Machine code

```
00010 001 00000111
00010 000 00000001
00011 000 00000001
00001 010 00000101
00100 000 00000010
00010 110 00000000
00101 000 00000000
```


RTL

```
R1 ← din
R0 ← R1
R0 ← R0 + R1
R2 ← 5
R0 ← R0 - R2
R6 ← R0
(none)
```

What is the value in dout at the end of the program if din=6?

YASAC Stage 1


Data unit

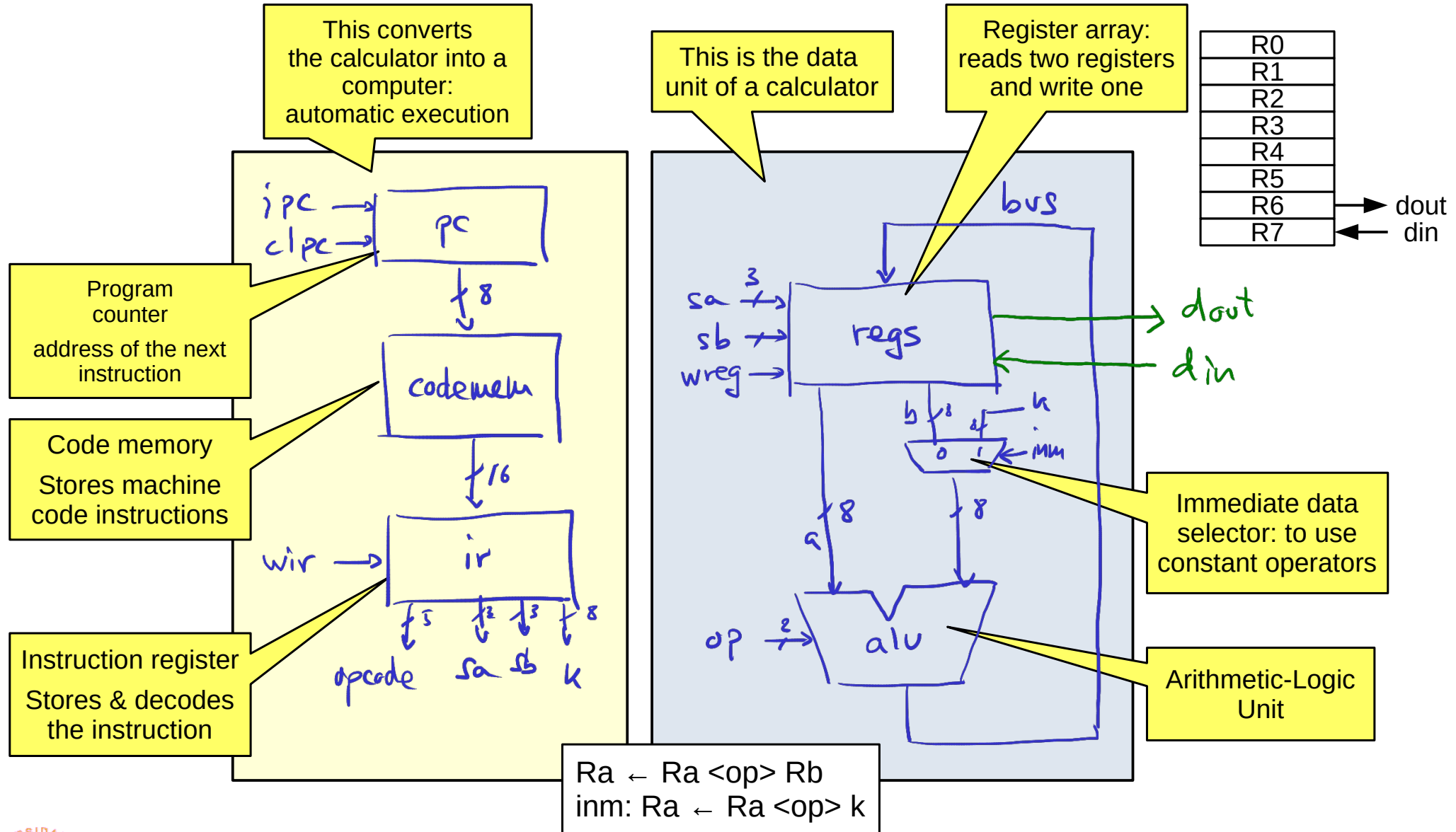

YASAC Stage 1


Data unit

data_unit

 

YASAC Stage 1

Register array

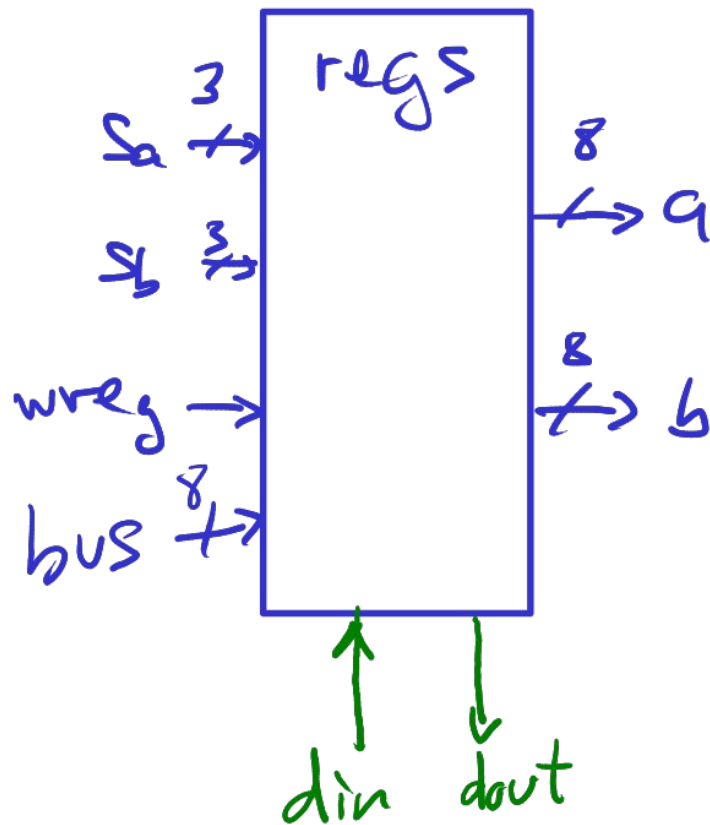

$$a = \text{regs}[sa]$$

$$b = \text{regs}[sb]$$

$$\overline{wreg} : \text{regs}[sa] \leftarrow \text{bus}$$

$$\overline{wreg} : \text{regs}[7] \leftarrow \text{din}$$


$$\text{dout} = \text{regs}[6]$$

Quick exercise

- Design the register array using combinational and sequential subsystems.
- Write a Verilog code fragment that models the register array.


YASAC Stage 1

Program counter and Instruction register

 

clpc : $pc \leftarrow \emptyset$
 ipc : $pc \leftarrow pc + 1$

clpc	ipc	pc ←
0	0	pc (INH.)
1	-	∅
0	1	pc + 1

 

wir : $ir \leftarrow ir_in$

wir	ir ←
0	ir (INH.)
1	ir_in

opcode = $ir[15:11]$

sa = $ir[10:8]$

sb = $ir[2:0]$



k = $ir[7:0]$

Quick exercise

Write a Verilog code fragment that models the registers.

YASAC Stage 1

Code memory and ALU

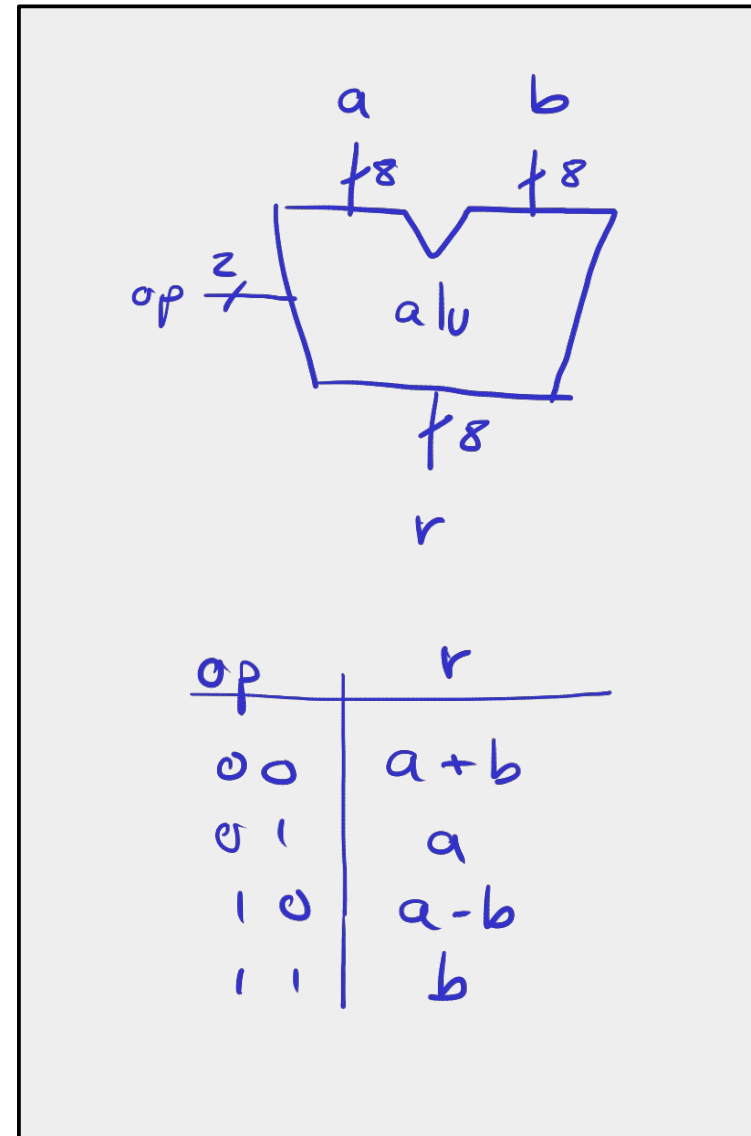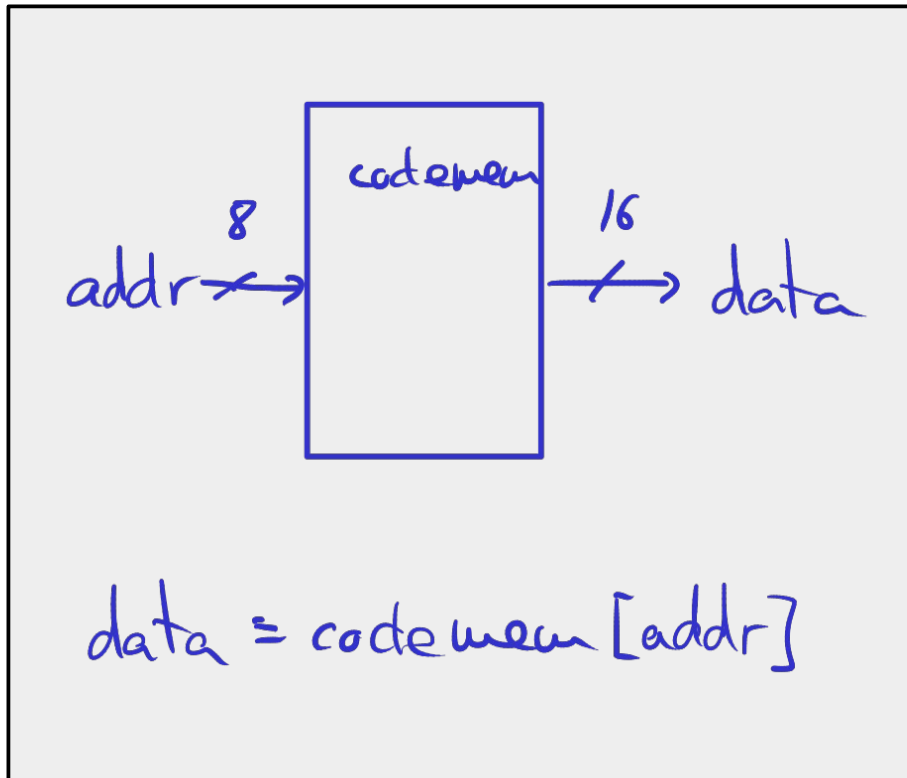


Quick exercise

Model the code memory in Verilog with a “case” statement. The memory has the contents of the sample program in a [previous slide](#).

YASAC Stage 1

Control unit

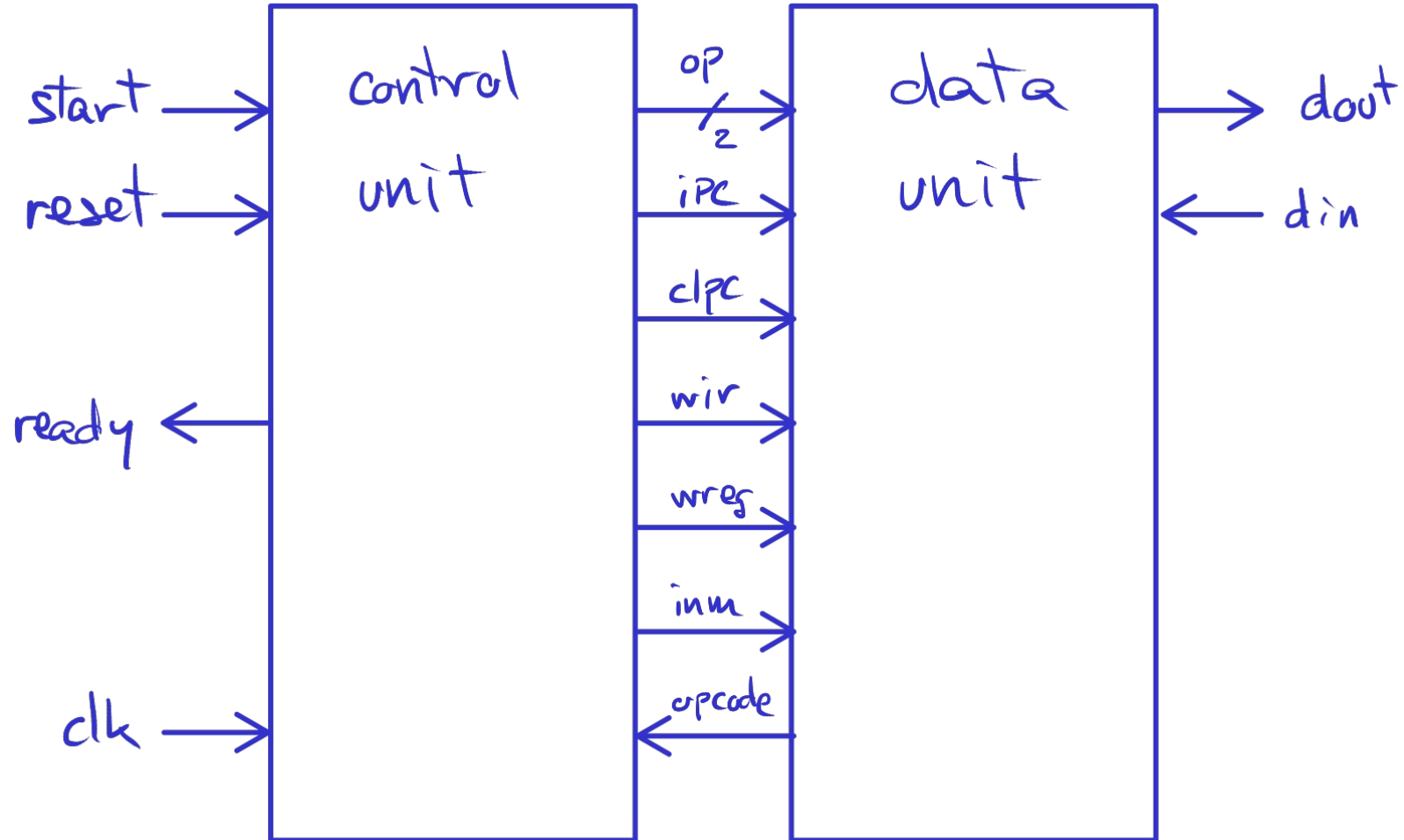

YASAC Stage 1

Control unit. Initial analysis

- The initial state waits for “start” activation. Then, the program counter is initialized:
 - $pc \leftarrow 0$ (clpc)
- For each instruction, the control unit must FETCH the instruction for memory and then EXECUTE the instruction by doing micro-operations on the data unit.
- FETCH: read the instruction code into the instruction register and increment the program counter:
 - $ir \leftarrow \text{code_mem}(pc); pc \leftarrow pc + 1$ (wir, ipc)
- EXECUTION
 - Depends on the “opcode”.
 - All the instructions in this stage can be executed in one clock cycle.
 - After executing and instruction, go back to FETCH the next one.

YASAC Stage 1


Control unit. Execution macro-operations

ADD :	$R_a \leftarrow R_a + R_b$		wreg ; op = 00
SUB :	$R_a \leftarrow R_a - R_b$		wreg ; op = 10
MOV :	$R_a \leftarrow R_b$		wreg ; op = 11
LDI :	$R_a \leftarrow k$		wreg ; imm ; op = 11
STOP :	→ Next state: READY		

YASAC Stage 1

Control unit. ASM chart

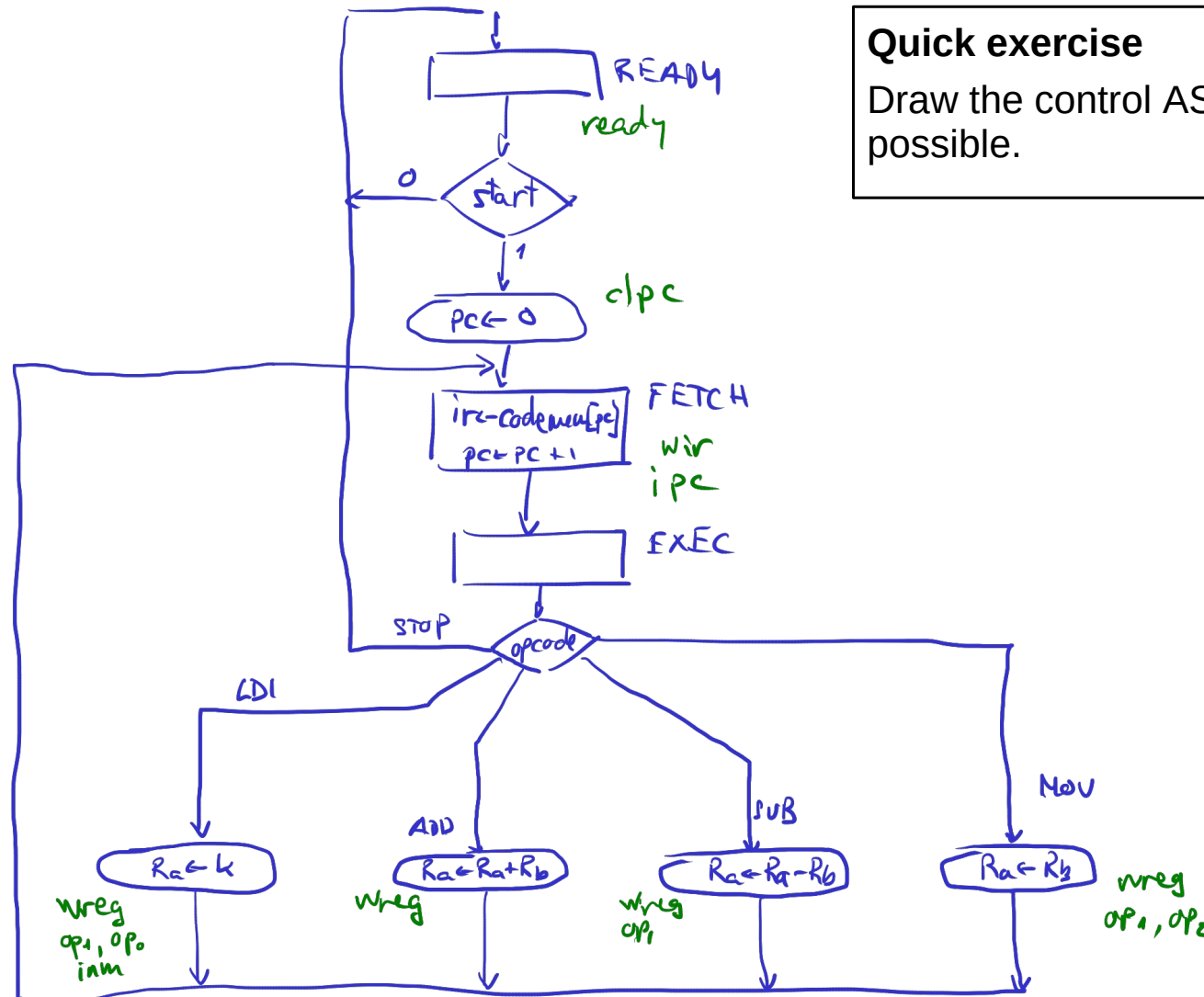Quick exercise
 Draw the control ASM chart. Simplify things if possible.



YASAC Stage 1

Control unit. States and control table


	READY	FETCH	EXEC
LDI Ra, k	ready start: clpc	wir, ipc	op=11, wreg, inm → FETCH
MOV Ra, Rb			op=11, wreg → FETCH
ADD Ra, Rb			op=00, wreg → FETCH
SUB Ra, Rb			op=10, wreg → FETCH
STOP			→ READY

The table represents the control signals to activate at every execution step depending on the instruction (opcode) to execute.

It is a convenient way to organize the information about the control unit that simplifies HDL coding.

YASAC Stage 1

Verilog coding

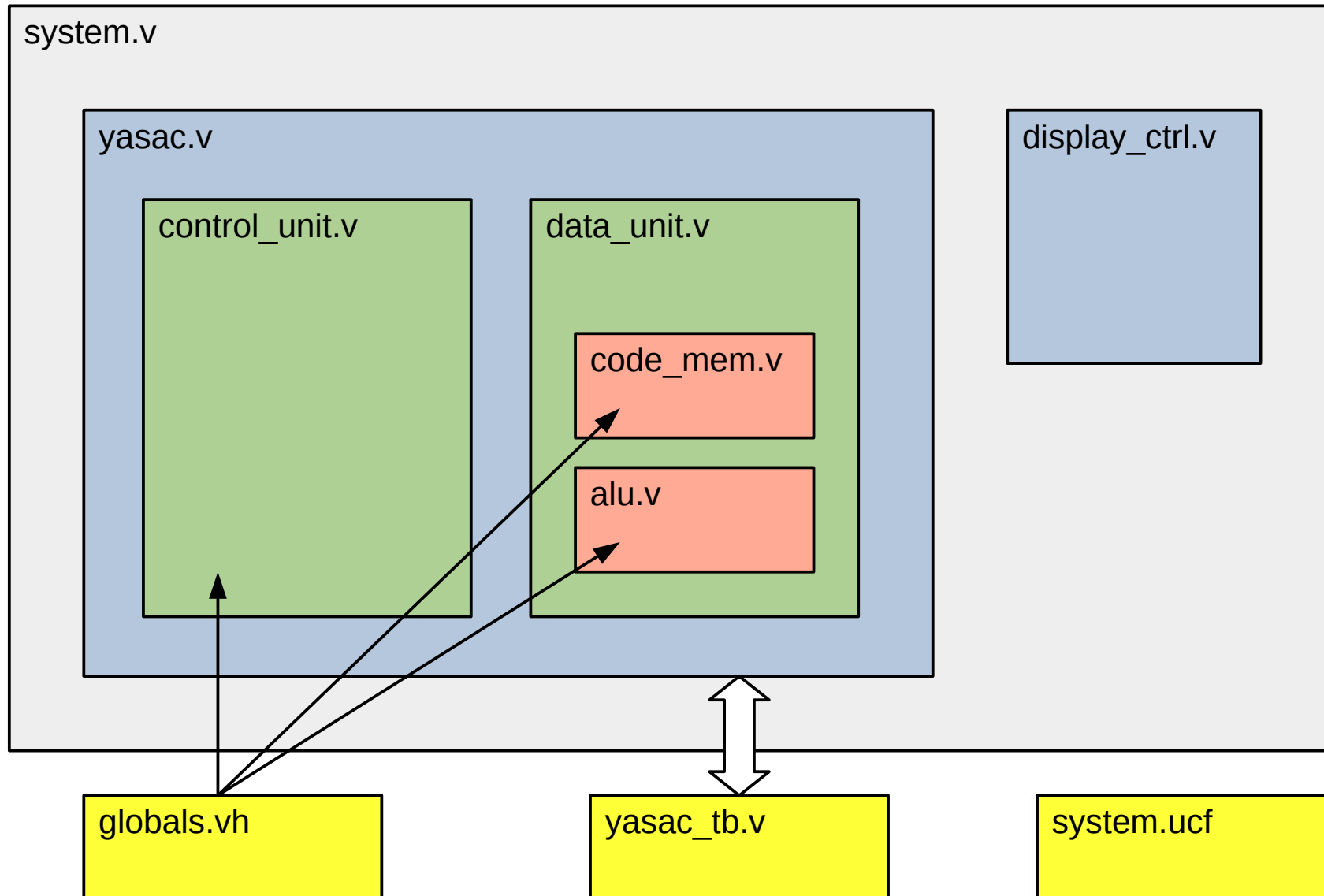

YASAC Stage 1 Verilog coding globals.vh


```
//// Assembly operation codes
`define LDI      5'd1
`define MOV     5'd2
`define ADD     5'd3
`define SUB     5'd4
`define STOP    5'd5

//// Registers
`define R0      3'd0
`define R1      3'd1
`define R2      3'd2
`define R3      3'd3
`define R4      3'd4
`define R5      3'd5
`define R6      3'd6
`define R7      3'd7

//// ALU operation codes
`define ALU_ADD  2'd0
`define ALU_TRA  2'd1
`define ALU_SUB  2'd2
`define ALU_TRB  2'd3
```

YASAC Stage 1 Verilog coding

alu.v

 

```

module alu (
    input wire [7:0] a,
    input wire [7:0] b,
    input wire [1:0] op,
    output reg [7:0] r
);

```

```

always @* begin
    case(op)
        `ALU_ADD: begin
            r = a + b;
        end
        `ALU_SUB: begin
            r = a - b;
        end
        `ALU_TRA: begin
            r = a;
        end
        `ALU_TRB: begin
            r = b;
        end
        default:
            r = 'bx;
    endcase
end
endmodule

```

YASAC Stage 1 Verilog coding code_mem.v

```
// Assembly op. codes
`define LDI      5'd1
`define MOV      5'd2
`define ADD      5'd3
`define SUB      5'd4
`define STOP     5'd5

// Registers
`define R0       3'd0
`define R1       3'd1
`define R2       3'd2
`define R3       3'd3
`define R4       3'd4
`define R5       3'd5
`define R6       3'd6
`define R7       3'd7

// ALU op. codes
`define ALU_ADD  2'd0
`define ALU_TRA  2'd1
`define ALU_SUB  2'd2
```

```
MOV R1, R7
MOV R0, R1
ADD R0, R1
LDI R2, 5
SUB R0, R2
MOV R6, R0
STOP
```

```
module code_mem (
    input wire [7:0] addr,
    output wire [15:0] data
);


    reg [15:0] code[0:255];
    integer i;

    assign data = code[addr];


    initial begin
        for (i=0; i<256; i=i+1) // Initialization
            code[i] = 16'h0000;

        // Code memory contents (program)
        code['h0] = {`MOV, `R1, 5'd0, `R7}; // format A
        code['h1] = {`MOV, `R0, 5'd0, `R1};
        code['h2] = {`ADD, `R0, 5'd0, `R1};
        code['h3] = {`LDI, `R2, 8'h05}; // format B
        code['h4] = {`SUB, `R0, 5'd0, `R2};
        code['h5] = {`MOV, `R6, 5'd0, `R0};
        code['h6] = {`STOP, 11'd0};

    end
endmodule
```

 

$data = code_mem[addr]$

 

YASAC Stage 1 Verilog coding data_unit.v

```

module data_unit (
  input wire clk,
  input wire [1:0] op,
  input wire ipc,
  input wire clpc,
  input wire wir,
  input wire wreg,
  input wire inm,
  output wire [4:0] opcode,
  input wire [7:0] din,
  output wire [7:0] dout
);

  reg [7:0] pc;
  reg [15:0] ir;
  reg [7:0] regs [0:7];

  //// Internal signals

  wire [15:0] inst;
  wire [2:0] sa, sb;
  wire [7:0] k;
  wire [7:0] rega, regb;
  wire [7:0] alu_b;
  wire [7:0] bus;
  
```

```

//// PC register
always @(posedge clk)
  if (clpc)
    pc <= 'b0;
  else if (ipc)
    pc <= pc + 1;


//// IR register
always @(posedge clk)
  if (wir)
    ir <= inst;
  assign opcode = ir[15:11];
  assign sa = ir[10:8];
  assign sb = ir[2:0];
  assign k = ir[7:0];

//// Register array
always @(posedge clk)
  if (wreg)
    regs[sa] <= bus;
  else
    regs[7] <= din;
  assign rega = regs[sa];
  assign regb = regs[sb];
  assign dout = regs[6];
  
```

```

//// Code memory
code_mem code_mem (
  .addr(pc),
  .data(inst)
);

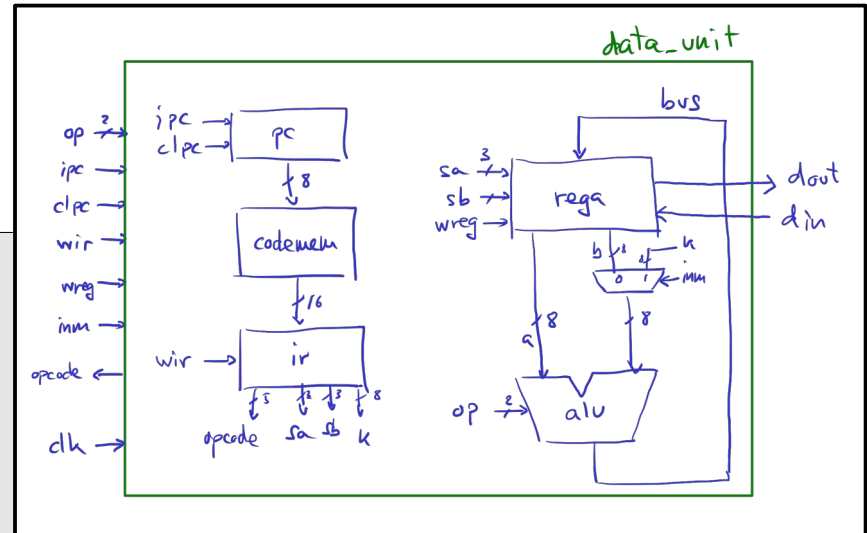//// ALU
assign alu_b = inm ? k : regb;
alu alu (
  .a(rega),
  .b(alu_b),
  .op(op),
  .r(bus)
);
endmodule
  
```



YASAC Stage 1 Verilog coding control_unit.v

```

`include "globals.vh"

module control_unit (
  // External signals
  input wire clk, // clock (rising edge)
  input wire reset, // reset (synchronous)
  input wire start, // start operation
  output reg ready, // ready output indicator

  // Data unit signals
  input wire [4:0] opcode,
  output reg [1:0] op, // ALU operation code
  output reg ipc, // PC increment
  output reg clpc, // PC clear
  output reg wir, // write IR
  output reg wreg, // write register array
  output reg inm, // use immediate value
  // FSM state output for testing
  output wire [1:0] state_out
);

// Route state signal for testing
assign state_out = state;

// State definition
localparam [1:0] READY = 0,
               FETCH = 1,
               EXEC = 2;

// State variables
reg [1:0] state, next_state;


// State change process
always @(posedge clk)
  if (reset == 1'b1)
    state <= READY;
  else
    state <= next_state;

```

```


// Next state and output process
always @* begin
  // Default output values
  ready = 1'b0; op = 'b0; ipc = 1'b0; clpc = 1'b0;
  wir = 1'b0; wreg = 1'b0; inm = 1'b0;
  next_state = 'bx;
  case (state)
    READY: begin
      ready = 1'b1;
      if (start) begin
        clpc = 1'b1;
        next_state = FETCH;
      end else begin
        next_state = READY;
      end
    end
    FETCH: begin
      wir = 1'b1;
      ipc = 1'b1;
      next_state = EXEC;
    end
    EXEC: begin
      next_state = FETCH; // except if STOP
      case(opcode)
        `LDI: begin
          op = `ALU_TRB;
          wreg = 1'b1; inm = 1'b1;
        end
        [...]
        default: // including STOP
          next_state = READY;
        endcase
      end
    end
    default: // Should not reach this point
      next_state = 'bx;
    endcase
  end
end
endmodule

```

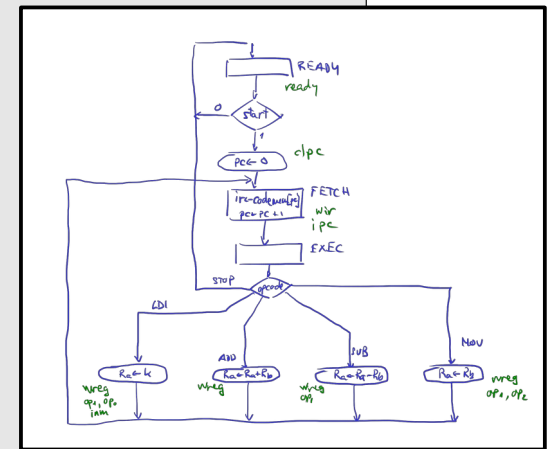

YASAC Stage 1 Verilog coding

yasac.v

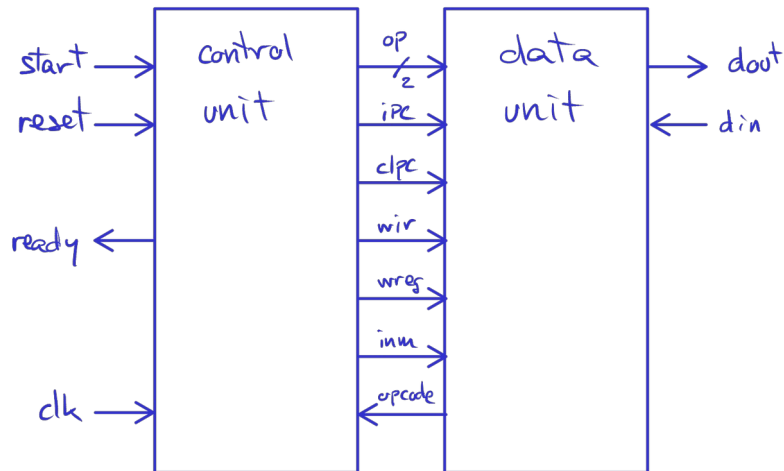

```

module yasac (
    input wire clk,
    input wire reset,
    input wire start,
    output wire ready,
    input wire [7:0] din,
    output wire [7:0] dout,
    output wire [1:0] state_out
);

    // Internal signals
    wire [4:0] opcode;
    wire [1:0] op;
    wire ipc, clpc, wir, wreg, inm;

```

```

// Control unit instance
control_unit control_unit (
    .clk(clk),
    .reset(reset),
    .start(start),
    .ready(ready),
    .opcode(opcode),
    .op(op),
    .ipc(ipc),
    .clpc(clpc),
    .wir(wir),
    .wreg(wreg),
    .inm(inm),
    .state_out(state_out)
);

// Data unit instance
data_unit data_unit (
    .clk(clk),
    .op(op),
    .ipc(ipc),
    .clpc(clpc),
    .wir(wir),
    .wreg(wreg),
    .inm(inm),
    .opcode(opcode),
    .din(din),
    .dout(dout)
);

endmodule

```

YASAC Stage 1 Verilog coding

yasac_tb.v

- Generate a clock signal.
- Reset the system.
- Activate execution (start).
- Wait for “ready” activation.
 - End if not activated in a long time
- Print “din” and “dout”.
- “dout” not as expected?
 - Open a waveform viewer.

```

module test ();
    reg clk;           // clock (rising edge)
    reg reset;        // reset (synchronous, active low)
    reg start;        // start operation
    wire ready;       // ready output indicator
    reg [7:0] din;    // external data input
    wire [7:0] dout;  // external data output

    yasac uut (
        .clk(clk),    // clock (rising edge)
        .reset(reset), // reset (synchronous, active low)
        .start(start), // start operation
        .ready(ready), // ready output indicator
        .din(din),    // external data input
        .dout(dout)   // external data output
    );

    // Clock generator (T=20ns, f=50MHz)
    always
        #10 clk = ~clk;
  
```

```

initial begin
    // output generation
    $dumpfile("yasac_tb.vcd");
    $dumplimit(100000000); // limit dump file to 10MB
    $dumpvars(0, test);
    // input signal initialization
    clk = 1'b0;
    reset = 1'b0;
    start = 1'b0;
    din = 8'd6;
    // global reset
    @(posedge clk) #1 reset = 1'b1;
    @(posedge clk) #1 reset = 1'b0;

    repeat(3) @(posedge clk) #1;

    // start program execution
    start = 1'b1;
    @(posedge clk) #1;
    start = 1'b0;
    // wait for "ready"
    wait(ready)
        $display("'ready' activation detected.");

    repeat(3) @(posedge clk) #1;
    $display("Normal simulation end.");

    // Print input and output ports (quick check results)
    $display("din: %h, dout: %h", din, dout);
    $finish;
end

// Force finish after 1000 clock cycles
initial begin
    #(20*1000);
    $display("'ready' not detected. Abnormal simulation end.");
    $display("Check the design.");
end
endmodule
  
```

YASAC Stage 1 Verilog coding system.v


```

module system (
  // External signals
  input wire clk,           // clock (rising edge)
  input wire reset,        // reset (synchronous)
  input wire start,        // start operation
  output wire ready,       // ready output
  input wire [7:0] din,    // external data input
  output wire [7:0] dout,  // external data output
  output wire [0:6] seg,   // 7-segment output
  output wire [3:0] an,    // anode output
  output wire dp,         // decimal point output
  // FSM state output for testing
  output reg [7:0] state_dec
);

// Clock divider to 1Hz
reg [24:0] prescaler;
reg clk_in;
always @(posedge clk)
  if (prescaler == 25000000-1) begin
    clk_in = ~clk_in;
    prescaler = 'b0;
  end else begin
    prescaler = prescaler + 1;
  end

// Edge detector for 'start'
reg start0=0, start1=0;
wire start_pulse;
always @(posedge clk_in) begin
  start1 <= start0;
  start0 <= start;
end
assign start_pulse = start0 & ~start1;

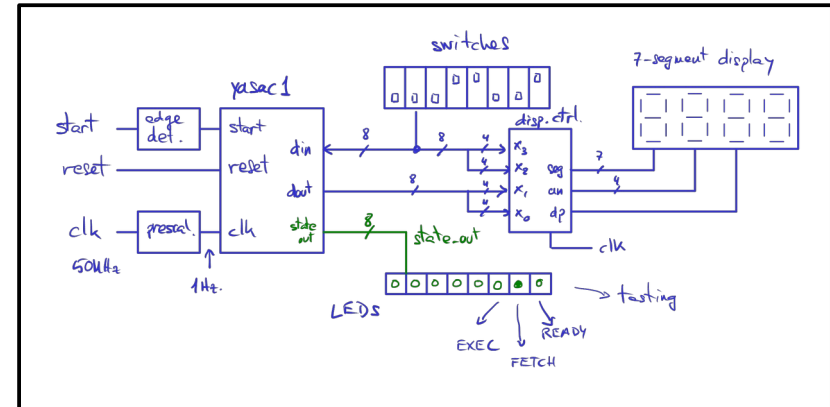// State decoder (for testing)
wire [1:0] state_out;
always @* begin
  state_dec = 'b0;
  state_dec[state_out] = 1'b1;
end
  
```



```

// Processor instance
yasac yasac (
  .clk(clk_in),           // clock (rising edge)
  .reset(reset),         // reset (synchronous)
  .start(start_pulse),   // start operation
  // .ready(ready),       // ready output indicator
  .din(din),             // external data input
  .dout(dout),           // external data output
  // state output (for testing)
  .state_out(state_out)
);

// 7-segment controller instance
display_ctrl #(
  .cdbits(18), .hex(1)
) display_ctrl (
  .ck(clk),              // system clock
  .x3(din[7:4]),         // display digits
  .x2(din[3:0]),
  .x1(dout[7:4]),
  .x0(dout[3:0]),
  .dp_in(4'b1011),     // decimal point vector
  .seg(seg),            // 7-segment output
  .an(an),              // anode output
  .dp(dp)               // decimal point output
);
endmodule
  
```


YASAC Stage 2

- Stage 1 limitations
 - No data memory (storage limited to internal registers).
 - Limited input/output (only one input and one output port).
 - (Many more...)
- Why do we need a data memory?
 - 8 registers are not enough for most applications
 - Need more room to store data (lists, conversion tables, text, etc.)
- Why do we need more input/output ports
 - An useful computer, even a simple one, needs a few peripherals:
 - serial ports,
 - generic input/output ports -GPIO-,
 - keyboard,
 - display, etc.

Data memory


- Having a data memory implies new design decisions:
 - Need new instructions to transfer data to/from memory.
 - Q1: Can we operate with the memory data directly?
 - A1: Data processing architecture.
 - Q2: How do we transfer data to/from memory?
 - Addressing modes.
- Q1: Load/Store architecture
 - Processing instructions (ADD, SUB, etc.) only work on registers.
 - Data must be loaded into registers before processing and stored back in memory afterwards.
 - Simplifies the design of the computer.
 - Typical of RISC processors.
 - We will use this approach in the YASAC
 - Other processors can process data in the memory directly (with limitations).
Eg. x86-XX.

Data memory Addressing modes

- How data is accessed.
- Addressing modes in the YASAC
 - **Immediate mode**: data is within the instruction code (eg. LDI instruction).
 - **Register mode**: data is in a register (eg. MOV instruction).
 - **Direct memory mode**: data is in memory and the address is included the instruction code (new LDS instruction).
 - **Register indirect mode**: data is in memory and the memory address is in a register (new LD instruction).
- Other addressing modes (not in the YASAC)
 - **Displacement mode**: the memory address is obtained by adding a “small” displacement value (offset) to the value of a register.
 - **Indexed mode**: the memory address is obtained by adding the value of a register to the address included in the instruction.
 - **PC-relative addressing**: the memory address is obtained by adding a “small” displacement to the value of the Program Counter (PC).

YASAC Stage 2. General specification

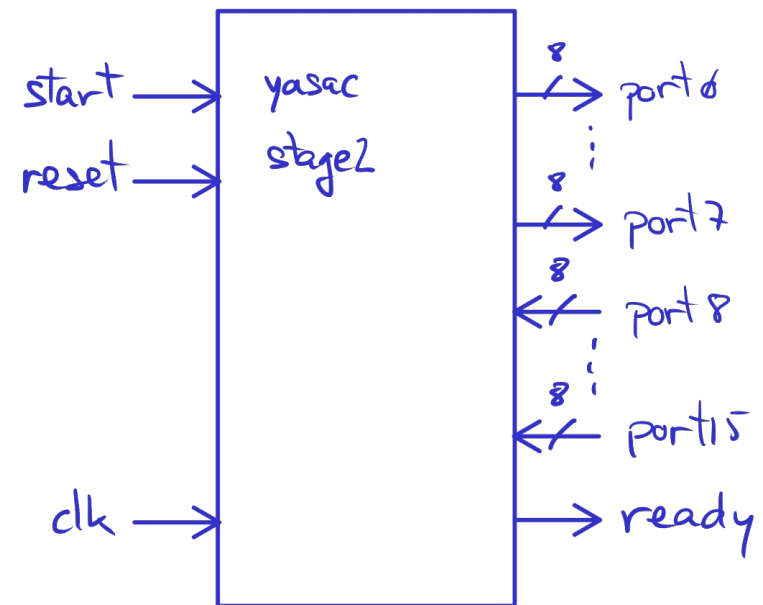- 8-bit data unit and registers
- 8 general purpose registers
- Program memory: 256x16
- Data memory: 256x8
- 8 8-bit input ports and 8 8-bit output ports
 - port0 to port7: output ports mapped to memory addresses 240 to 247 (F0 to F7).
 - port8 to port15: input ports mapped to memory addresses 248 to 255 (F8 to FF).
- 16-bit instructions



YASAC Stage 2

Needed changes

- Data memory module.
 - RAM memory.
- More input/output ports.
 - I/O ports will be mapped to memory addresses and will be implemented together with the memory module.
- Memory Address Register (MAR).
 - To hold the data memory address that is to be accessed.
- A multiplexed bus.
 - Now data can come from the ALU or the data memory.


YASAC Stage 2

Memory-mapped I/O


- From the computer's and programmer's point of view, there is only data memory.
 - There are no special instructions to access input/output ports.
- Some ranges of the data memory address space are routed to input or output ports.
- A control circuit in the data memory module decides if it has to access memory or ports depending on the address.
- Memory-mapped input/output is common in real processors.

YASAC Stage 2


Memory-mapped I/O

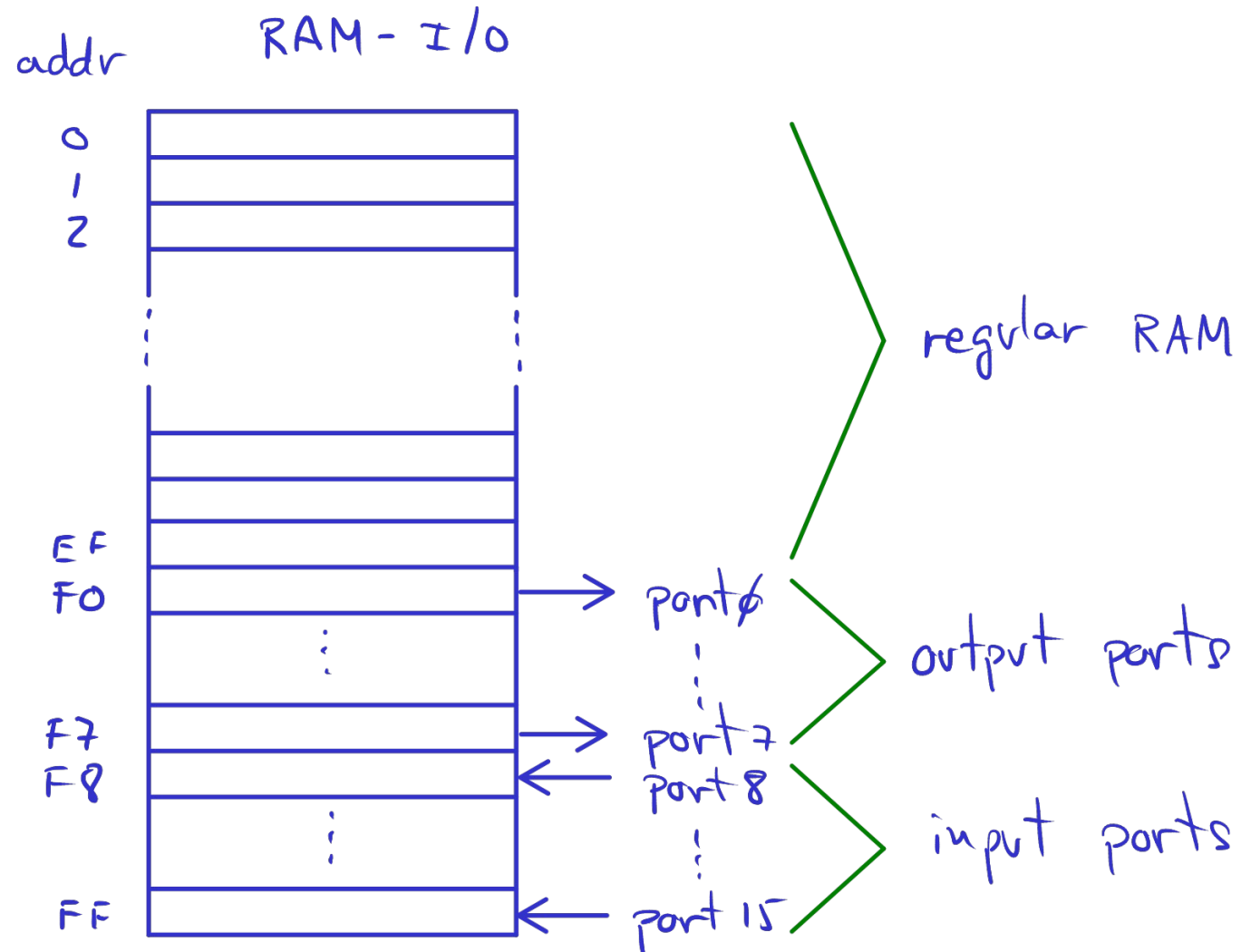

YASAC Stage 2 Board implementation

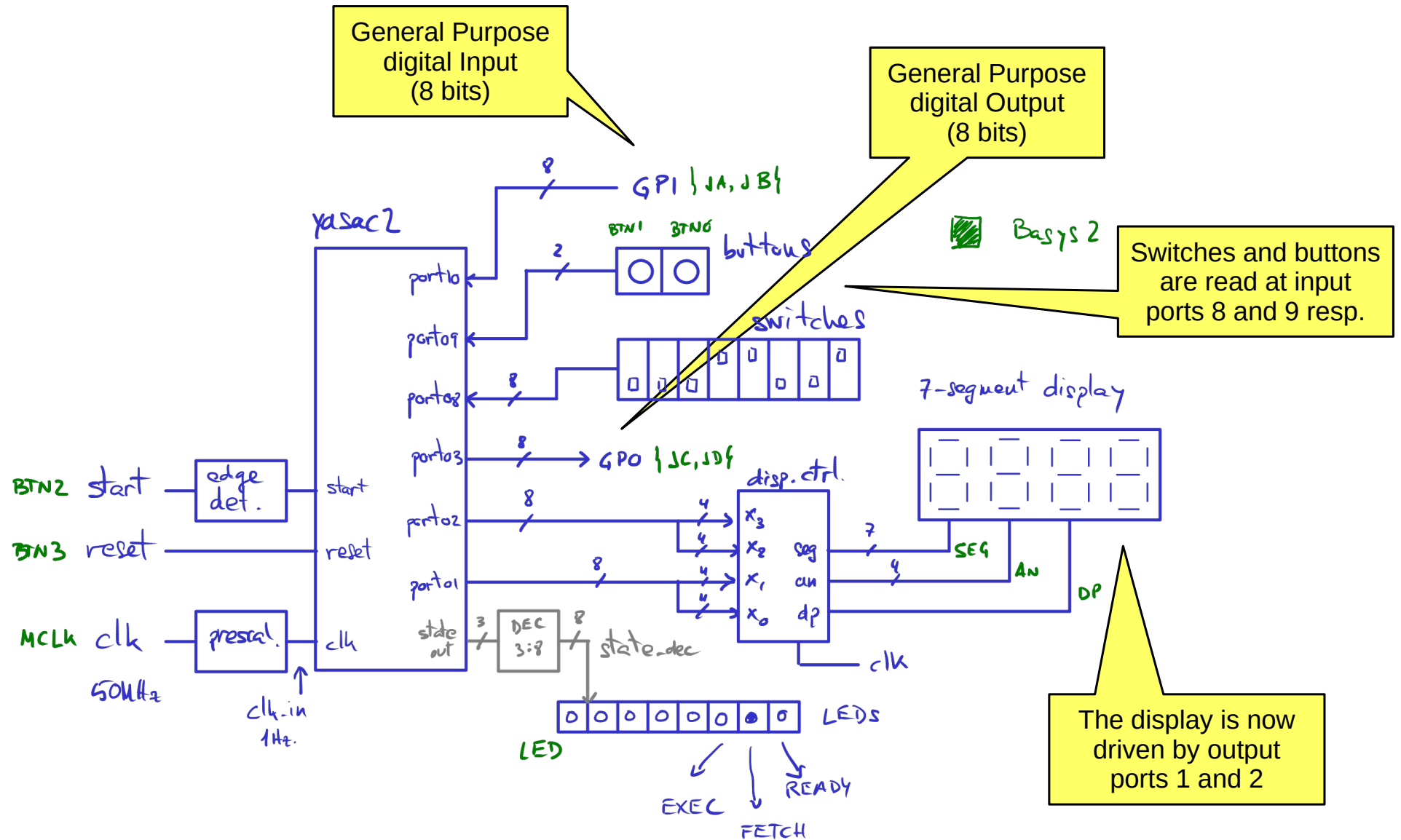


YASAC Stage 2 Board implementation

 

YASAC Stage 2 Instruction Set

Instruction format

 

Op. code	Instruction	RTL
00001	LDI Ra, k	Ra ← k
00010	MOV Ra, Rb	Ra ← Rb
00011	ADD Ra, Rb	Ra ← Ra+Rb
00100	SUB Ra, Rb	Ra ← Ra-Rb
00101	STOP	–
00110	LD Ra, Rb	Ra ← datamem(Rb)
00111	ST Rb, Ra	datamem(Rb) ← Ra
01000	LDS Ra, k	Ra ← datamem(k)
01001	STS k, Ra	datamem(k) ← Ra

YASAC Stage 2

Sample program

Reads data from port8, adds to previous value at memory address 10h, saves the result to address 10h and outputs the result to output port1.

Assembly code


```
LDI R1,0x10 ; pointer to old value
LDI R2,0xF1 ; pointer to port1
LDS R3,0xF8 ; read port8
LD R4,R1 ; read old value to R4
ADD R3,R4 ; add old and new value
STS 0x10,R3 ; store result in memory
ST R2,R3 ; output result to port1
STOP
```

Quick exercise

- Obtain the machine code in binary and hexadecimal.
- What is the output value at port01 if the initial value at memory address 0x10 is 25 and the input at port08 is 7?
- What is the value at the output port if we execute the program again?


YASAC Stage 2

Data unit

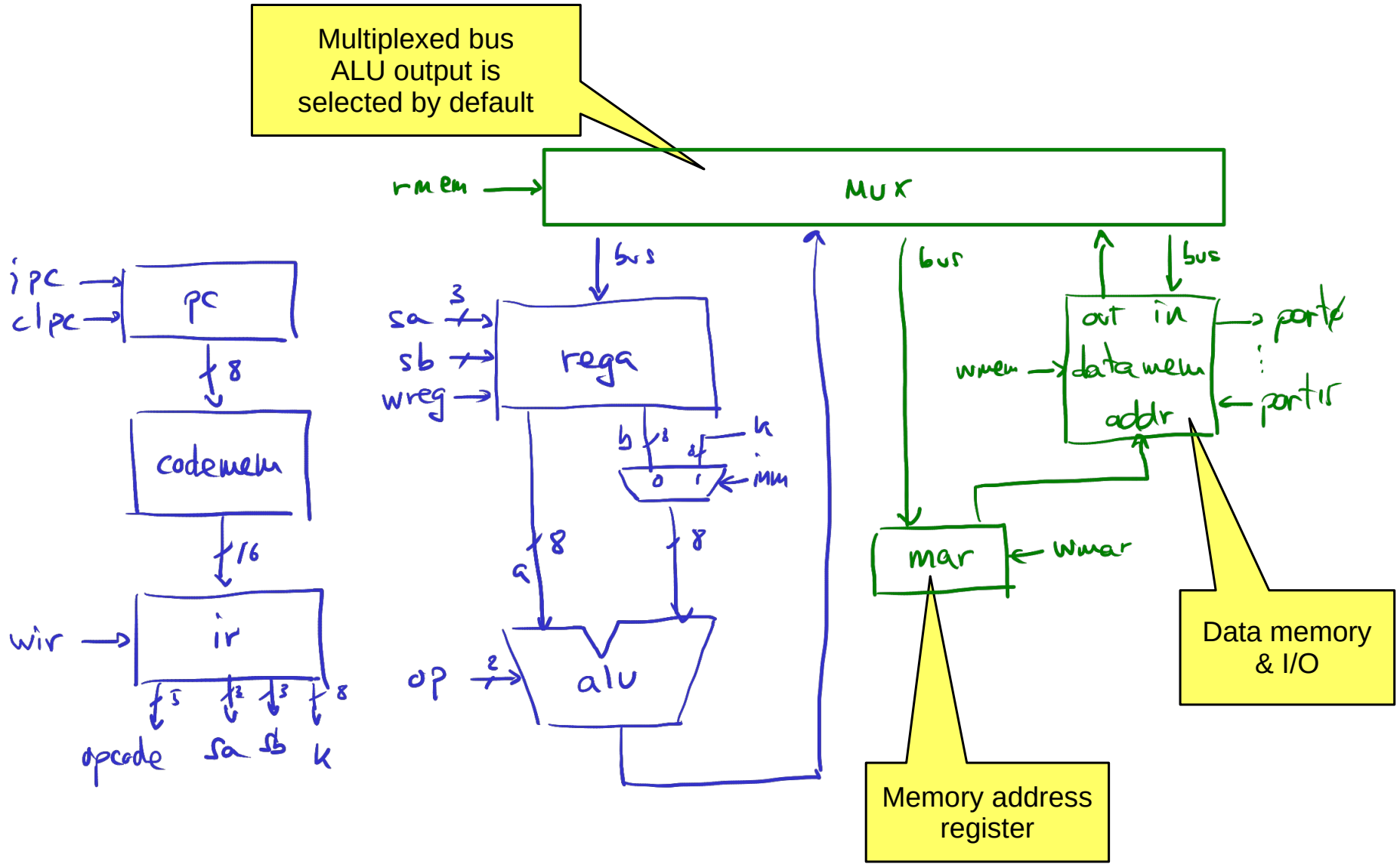

YASAC Stage 2

Data memory and I/O

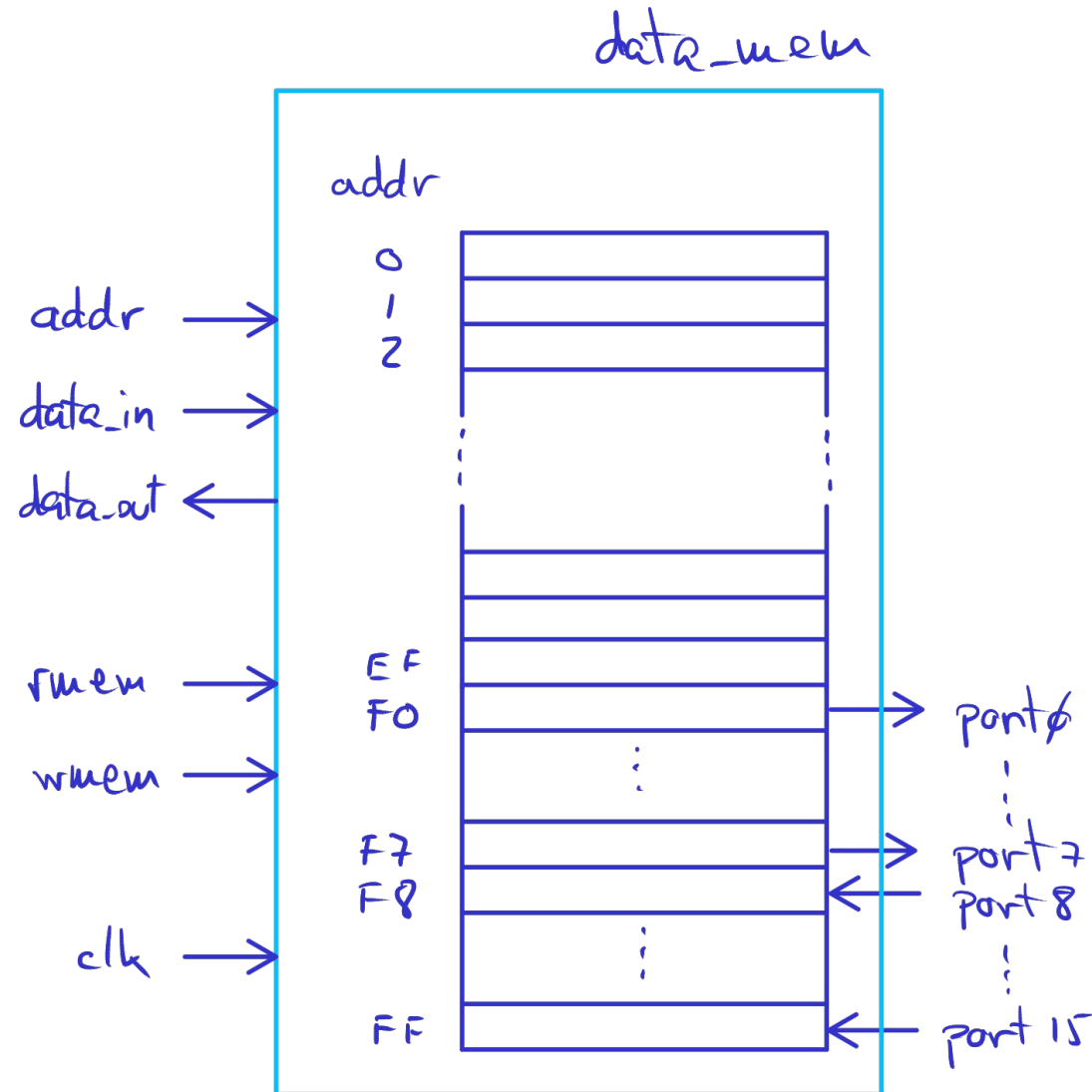

YASAC Stage 2

Control unit. Micro-operations

LD R_a, R_b

1) $mar \leftarrow rb$

$op = ALU_TRB, wmar$

2) $ra \leftarrow data_mem[mar]$

$rmem, wreg$

ST R_b, R_a

1) $mar \leftarrow rb$

$op = ALU_TRB, wmar$

2) $data_mem[mar] \leftarrow ra$

$op = ALU_TRA, wmem$

LDS R_a, k

1) $mar \leftarrow k$

$op = ALU_TRB, imm, wmar$

2) $ra \leftarrow data_mem[mar]$

$rmem, wreg$

STS k, ra

1) $mar \leftarrow k$

$op = ALU_TRB, imm, wmar$


2) $data_mem[mar] \leftarrow ra$

$op = ALU_TRA, wmem$

YASAC Stage 2 control unit State definition strategy

Different states for different instructions

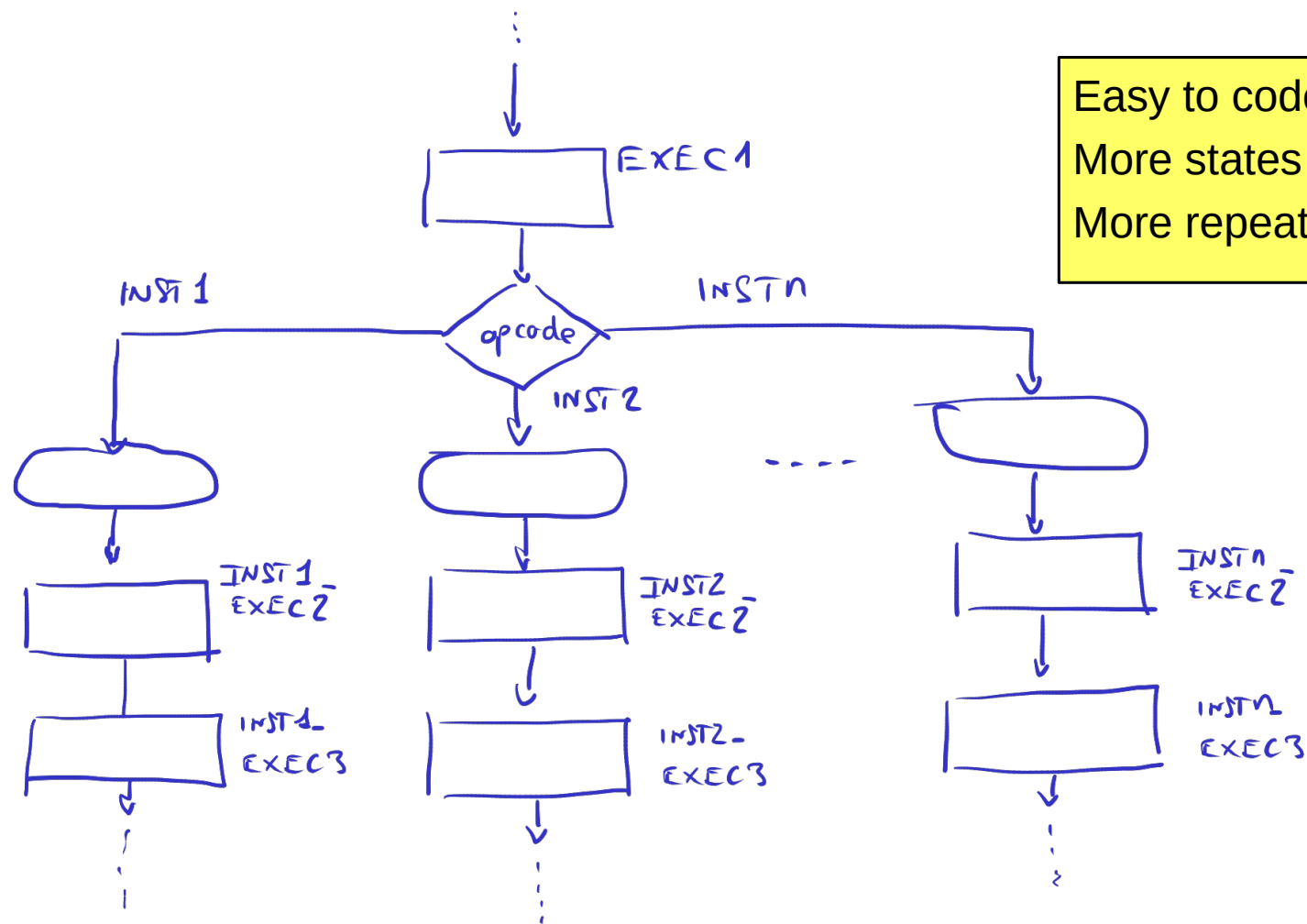
Easy to code in HDL.
More states than necessary.
More repeated code.



YASAC Stage 2 control unit

State definition strategy

Same states for all instructions

 

Saves states.
 Easier to combine similar instructions.
 Easier to separate sequential and combinational processes.
 More difficult to code?

We will use this one!

YASAC Stage 2

Control unit. States and control table

	READY	FETCH	EXEC1	EXEC2
LDI Ra, k	ready start: clpc	wir, ipc	op=11, wreg, inm → FETCH	
MOV Ra, Rb			op=11, wreg → FETCH	
ADD Ra, Rb			op=00, wreg → FETCH	
SUB Ra, Rb			op=10, wreg → FETCH	
STOP			→ READY	
LD Ra, Rb			op=11, wmar	rmem, wreg → FETCH
ST Rb, Ra			op=11, wmar	op=01, wmem → FETCH
LDS Ra, k			op=11, wmar, inm	rmem, wreg → FETCH
STS k, Ra			op=11, wmar, inm	op=01, wmem → FETCH


The table represents the control signals to activate at every execution step depending on the instruction (opcode) to execute.

With this representation, the same states are used to execute all the instructions.

It is a convenient way to organize the information about the control unit that simplifies HDL coding.


YASAC Stage 2

Control unit. ASM control chart

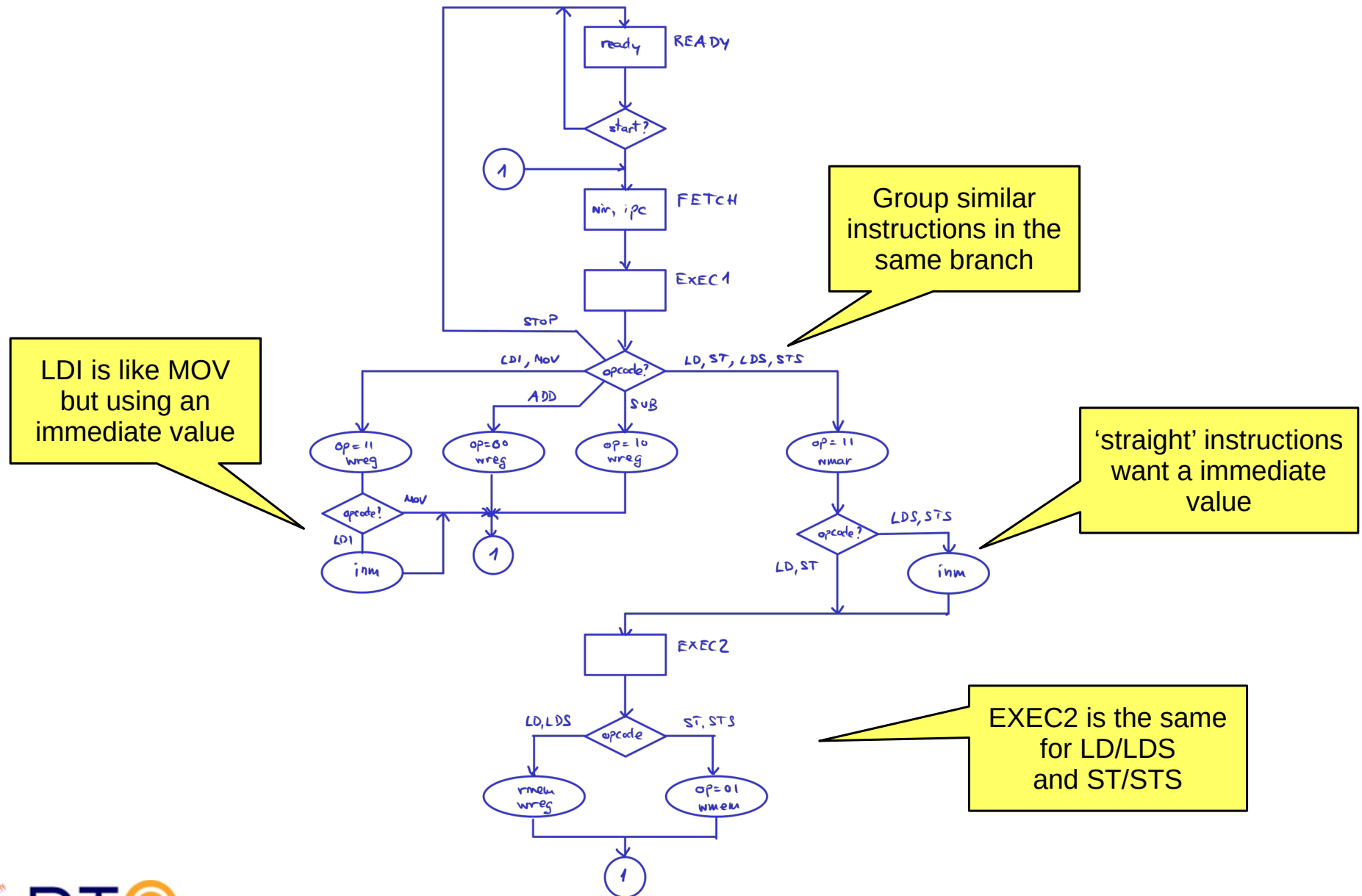

YASAC Stage 2

Verilog coding

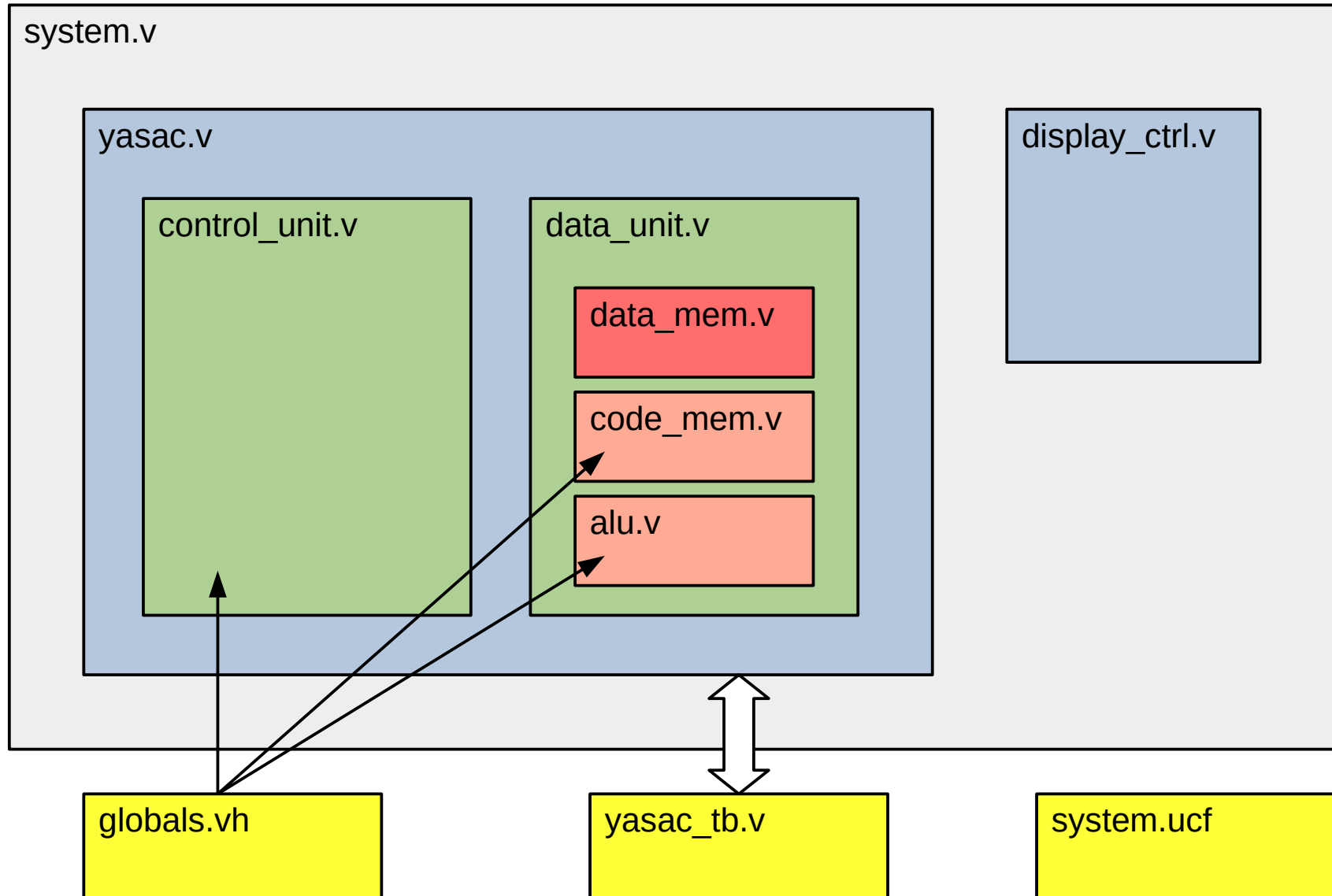

YASAC Stage 2 Verilog coding

code_mem.v

```

`include "globals.vh"

module code_mem (
    input wire [7:0] addr,          // address port
    output wire [15:0] data        // data port
);


    reg [15:0] code[0:255];
    integer i;

    assign data = code[addr];

    initial begin
        // Code memory contents (program)
        code['h0] = {`LDI, `R1, 8'h10};           // LDI R1,0x10
        code['h1] = {`LDI, `R2, 8'hf1};           // LDI R2,0xf1
        code['h2] = {`LDS, `R3, 8'hf8};           // LDS R3,0xf8 ; load from port08
        code['h3] = {`LD, `R4, 5'd0, `R1};        // LD R4,R1
        code['h4] = {`ADD, `R3, 5'd0, `R4};        // ADD R3,R4
        code['h5] = {`STS, `R3, 8'h10};           // STS 0x10,R3
        code['h6] = {`ST, `R3, 5'd0, `R2};        // ST R2,R3 ; store to port01
        code['h7] = {`STOP, 11'd0};               // STOP
    end
endmodule

```


Tests all the
new instructions

 

$data = code_mem[addr]$

YASAC Stage 2 Verilog coding

data_mem.v

 

```

module data_mem (
    input wire clk,                // clock (rising edge)
    input wire wmem,              // write data memory
    input wire [7:0] addr,        // address
    input wire [7:0] data_in,     // input data
    output wire [7:0] data_out,   // output data
    output wire [7:0] port00, port01, port02, port03, // output
    port04, port05, port06, port07, // ports
    input wire [7:0] port08, port09, port10, port11, // input
    port12, port13, port14, port15 // ports
);

```

YASAC Stage 2 Verilog coding

data_mem.v

```
// RAM write
always @(posedge clk)
    // Write only RAM and output ports
    if (wmem && addr < 8'hf0)
        mem[addr] <= data_in;

// Output port write
always @(posedge clk)
    if (wmem && addr >= 8'hf0 && addr < 8'hf8)
        case(addr[3:0])
            4'h0: port_reg00 <= data_in;
            [...]
            4'h7: port_reg07 <= data_in;
        endcase

// Output port read
assign port00 = port_reg00;
[...]
assign port07 = port_reg07;

// Input port write (from external pins)
always @(posedge clk) begin
    port_reg08 <= port08;
    [...]
    port_reg15 <= port15;
end
```


```
// Asynchronous read
always @*
    case(addr[3:0])
        4'h0: port_out = port_reg00;
        [...]
        4'h7: port_out = port_reg07;
        4'h8: port_out = port_reg08;
        [...]
        4'hf: port_out = port_reg15;
        default: port_out = 'bx;
    endcase

// Data output generation
assign data_out = (addr < 8'hf0) ?
    mem[addr] : port_out;
```

Memory and
ports reading

Memory and
ports writing

YASAC Stage 2 Verilog coding data_unit.v

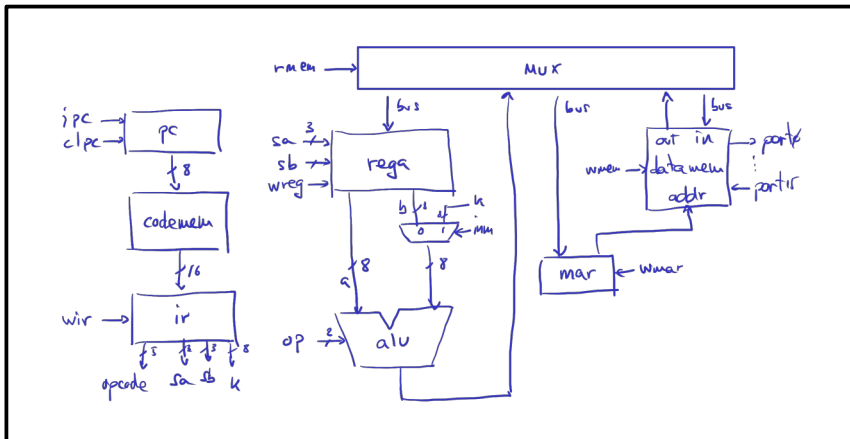

```

module data_unit (
    input wire clk,           // clock (rising edge)
    input wire [1:0] op,     // ALU operation code
    input wire ipc,         // PC increment
    input wire clpc,       // PC clear
    input wire wir,        // write IR
    input wire wreg,      // write register array
    input wire inm,      // use immediate value
    output wire [4:0] opcode, // operation code
    input wire wmem,     // write data memory
    input wire rmem,     // read data memory
    input wire wmar,     // write MAR
    output wire [7:0] port00, port01, // output
    port02, port03, // ports
    port04, port05,
    port06, port07,
    input wire [7:0] port08, port09, // input
    port10, port11, // ports
    port12, port13,
    port14, port15
);

```

```

[...]
```

```

//// Memory address register

always @(posedge clk)
    if (wmar)
        mar <= bus;

//// Data memory

data_mem data_mem (
    .clk(clk),
    .wmem(wmem),
    .addr(mar),
    .data_in(bus),
    .data_out(data_out),
    .port00(port00), .port01(port01),
    .port02(port02), .port03(port03),
    .port04(port04), .port05(port05),
    .port06(port06), .port07(port07),
    .port08(port08), .port09(port09),
    .port10(port10), .port11(port11),
    .port12(port12), .port13(port13),
    .port14(port14), .port15(port15)
);
[...]
```

YASAC Stage 2 Verilog coding control_unit.v


```
// Next state process
always @* begin
  // Default next state
  next_state = 'bx;
  case (state)
  READY:
    if (start)
      next_state = FETCH;
    else
      next_state = READY;
  FETCH:
    next_state = EXEC1;
  EXEC1:
    case (opcode)
    `LDI, `MOV, `ADD, `SUB:
      next_state = FETCH;
    `LD, `ST, `LDS, `STS:
      next_state = EXEC2;
    default: // Shou
      next_state =
    endcase
  EXEC2:
    next_state =
  default: // Shou
    next_state =
  endcase
end
```

```
// Output process
always @* begin
  // Default output
  ready = 1'b0; op =
  ipc = 1'b0; clpc =
  wir = 1'b0; wreg =
  inm = 1'b0; wmem =
  rmem = 1'b0; wmar

  case (state)
  READY: begin
    ready = 1'b1;
    if (start)
      clpc = 1'b1;
    end
  FETCH: begin
    wir = 1'b1;
    ipc = 1'b1;
  end
  end
```

```
EXEC1:
  case (opcode)
  `LDI: begin
    op = `ALU_TRB;
    wreg = 1'b1; inm = 1'b1;
  end
  `ADD: begin
    op = `ALU_ADD;
    wreg = 1'b1;
  end
  `SUB: begin
    op = `ALU_SUB;
    wreg = 1'b1;
  end
  `MOV: begin
    op = `ALU_TRB;
    wreg = 1'b1;
  end
  `LD, `ST, `LDS, `STS: begin
    op = `ALU_TRB;
    wmar = 1'b1;
    if (opcode==`LDS || opcode==`STS)
      inm = 1'b1;
  end
  endcase

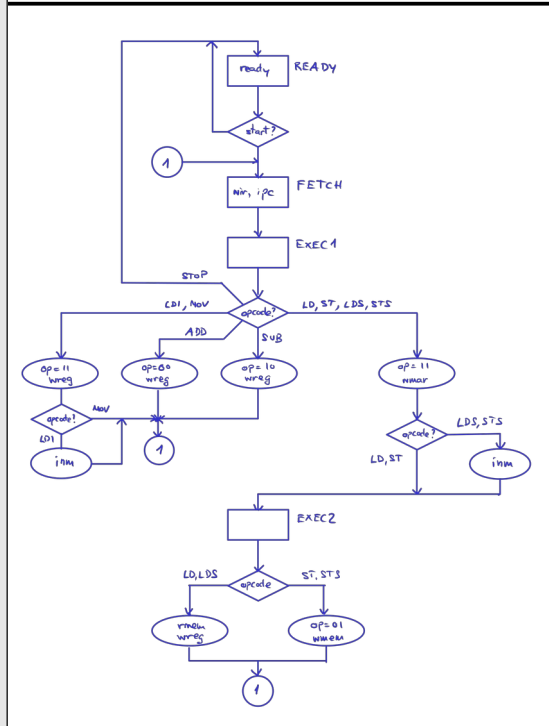EXEC2:
  case (opcode)
  `LD, `LDS: begin
    rmem = 1'b1;
    wreg = 1'b1;
  end
  `ST, `STS: begin
    op = `ALU_TRA;
    wmem = 1'b1;
  end
  endcase
end
```



Separate processes for next state and output calculation.
One thing at a time is easier!

YASAC Stage 2 Verilog coding

yasac.v

```

module yasac (
  input wire clk,           // clock (rising edge)
  input wire reset,        // reset (synchronous, active-high)
  input wire start,        // start operation
  output wire ready,       // ready output indicator
  output wire [7:0] port00, port01, port02, port03, // output ports
  port04, port05, port06, port07,
  input wire [7:0] port08, port09, port10, port11, // input ports
  port12, port13, port14, port15,
  output wire [1:0] state_out // FSM state output for testing
);

```

```

// Internal signals
wire [4:0] opcode;
wire [1:0] op;
wire ipc, clpc, wir, wreg

```

```

// Control unit instance
control_unit control_unit (
  .clk(clk),           // clock (rising edge)
  .reset(reset),      // reset (synchronous, active-low)
  .start(start),      // start operation
  .ready(ready),
  .opcode(opcode),
  .op(op),
  .ipc(ipc),
  .clpc(clpc),
  .wir(wir),
  .wreg(wreg),
  .inm(inm),
  .wmem(wmem),
  .rmem(rmem),
  .wmar(wmar),
  .state_out(state_out)
);

```

```

// Data unit instance
data_unit data_unit (
  .clk(clk),           // clock (rising edge)
  .op(op),             // ALU operation code
  .ipc(ipc),           // PC increment
  .clpc(clpc),        // PC clear
  .wir(wir),          // write IR
  .wreg(wreg),        // write register array
  .inm(inm),          // use immediate value
  .opcode(opcode),    // operation code of current instruction
  .wmem(wmem),        // write data memory
  .rmem(rmem),        // read data memory
  .wmar(wmar),        // write memory address register
  .port00(port00), .port01(port01), // output ports
  .port02(port02), .port03(port03),
  .port04(port04), .port05(port05),
  .port06(port06), .port07(port07),
  .port08(port08), .port09(port09), // input ports
  .port10(port10), .port11(port11),
  .port12(port12), .port13(port13),
  .port14(port14), .port15(port15)
);
endmodule

```

YASAC Stage 2 Verilog coding

yasac_tb.v

```

module test ();

    reg clk;           // clock (rising edge)
    reg reset;        // reset (synchronous)
    reg start;        // start operation
    wire ready;       // ready output indicator
    // output ports
    wire [7:0] port00, port01, port02, port03,
              port04, port05, port06, port07;
    // input ports
    reg [7:0] port08, port09, port10, port11,
             port12, port13, port14, port15;

    yasac uut (
        .clk(clk),           // clock (rising edge)
        .reset(reset),      // reset (synchronous)
        .start(start),      // start operation
        .ready(ready),      // ready output indicator
        .port00(port00), .port01(port01),
        .port02(port02), .port03(port03),
        .port04(port04), .port05(port05),
        .port06(port06), .port07(port07),
        .port08(port08), .port09(port09),
        .port10(port10), .port11(port11),
        .port12(port12), .port13(port13),
        .port14(port14), .port15(port15)
    );

    // Clock generator (T=20ns, f=50MHz)
    always
        #10 clk = ~clk;

```

```

initial begin
    // output generation
    $dumpfile("yasac_tb.vcd");
    $dumpvars(0, test);
    //$dumpvars(0, uut.data_unit.data_mem.mem['hf1]);

    // input signal initialization
    clk = 1'b0;
    reset = 1'b0;
    start = 1'b0;
    port08 = 8'd5;

    // global reset
    @(posedge clk) #1 reset = 1'b1;
    @(posedge clk) #1 reset = 1'b0;

    repeat(3) @(posedge clk) #1;

    // start program execution
    start = 1'b1;
    @(posedge clk) #1;
    start = 1'b0;
    // wait for "ready"
    wait(ready)
        $display("'ready' activation detected.");


    repeat(3) @(posedge clk) #1;
    $display("Normal simulation end.");

    // Check input and output ports
    $display("port08 (input): %h, port01 (output): %h",
            port08, port01);

    // port01 (output) should be equal to port08 (input)
    if (port01 == port08) begin
        $display("Test bench result: PASS.");
        $finish;
    end else begin
        $display("Test bench result: FAIL.");
        $finish;
    end
end

```

YASAC Stage 2 Verilog coding system.v

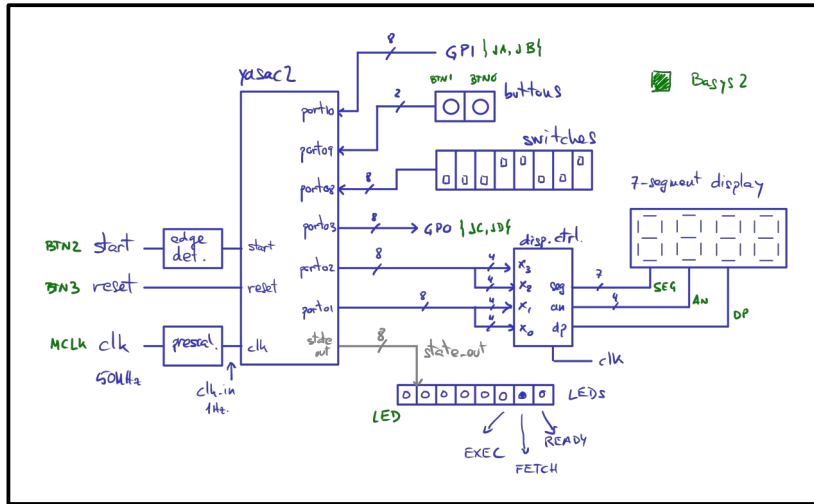

```
// Processor instance
yasac yasac (
    .clk(clk_in),
    .reset(reset),
    .start(start_pulse),
    // .ready(ready), // disabled for debugging
    // .port00(port00), // disabled for debugging
    .port01(port01),
    .port02(port02),
    .port03(port03), // ports 4 to 7 not used
    .port08(port08),
    .port09(port09),
    .port10(port10),
    .port11(8'h00), // not used
    .port12(8'h00),
    .port13(8'h00),
    .port14(8'h00),
    .port15(8'h00),
    .state_out(state_out) // state output
);
```

```
// 7-segment controller instance
display_ctrl #(.cdbits(18), .hex(1)) display_ctrl (
    .ck(clk), // system clock
    .x3(port02[7:4]), // display digits
    .x2(port02[3:0]),
    .x1(port01[7:4]),
    .x0(port01[3:0]),
    .dp_in(4'b1011), // decimal point vector
    .seg(seg), // 7-segment output
    .an(an), // anode output
    .dp(dp) // decimal point output
);
```

```
module system (
    // External signals
    input wire clk, // clock (rising edge)
    input wire reset, // reset (synchronous,
    input wire start, // start operation
    output wire ready, // ready output indicator
    // output wire [7:0] port00, // 8xLED (disabled for
    output wire [7:0] port03, // generic digital output
    input wire [7:0] port08, // 8xSwitches
    input wire [7:0] port09, // 4xButtons
    input wire [7:0] port10, // generic digital input
    output wire [0:6] seg, // 7-segment output
    output wire [3:0] an, // anode output
    output wire dp, // decimal point output
    output reg [7:0] state_dec // FSM state output for
);
[...]
```

YASAC Stage 3

- Stage 2 limitations
 - YASAC Stage 2 programs cannot alter the sequence of instructions (branching). Cannot take decisions!
 - (A few more...)
- Why do we need (conditional) branching instructions?
 - Take decisions in our program.
 - Implement (any) algorithm.
 - Conditional branching makes a true computer.

With these modifications, YASAC will become a Turing-complete computer: it can implement any algorithm (except for memory limitations).


YASAC Stage 3

Needed changes

- New instruction format
 - To encode new branch instructions.
- Program counter:
 - Connect to the bus to allow PC writing (branch instructions).
- ALU:
 - Needs to generate the status output of the last performed operation.
 - CF: carry flag. Set when carry (add) or borrow (sub).
 - ZF: zero flag. Set when result is zero.
 - NF: negative flag. Set when result is negative (in Two's complement).
 - VF: overflow flag. Set when overflow.
 - SF: sign flag ($S=N^{\wedge}V$). Set to 1 when $A-B$ is negative, even if there is overflow.
- Status register:
 - New register to store ALU's status output.
- Control unit:
 - Implement new instructions

YASAC Stage 3


Instruction format

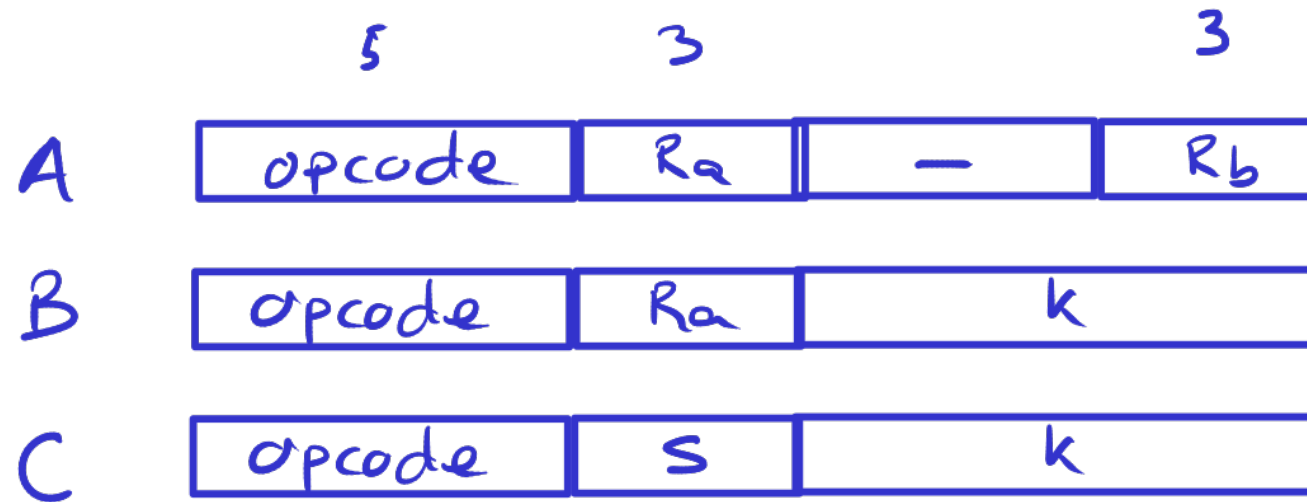

Status bit and branch condition selector. Works as an extension to the operation code.

YASAC Stage 3

Status register

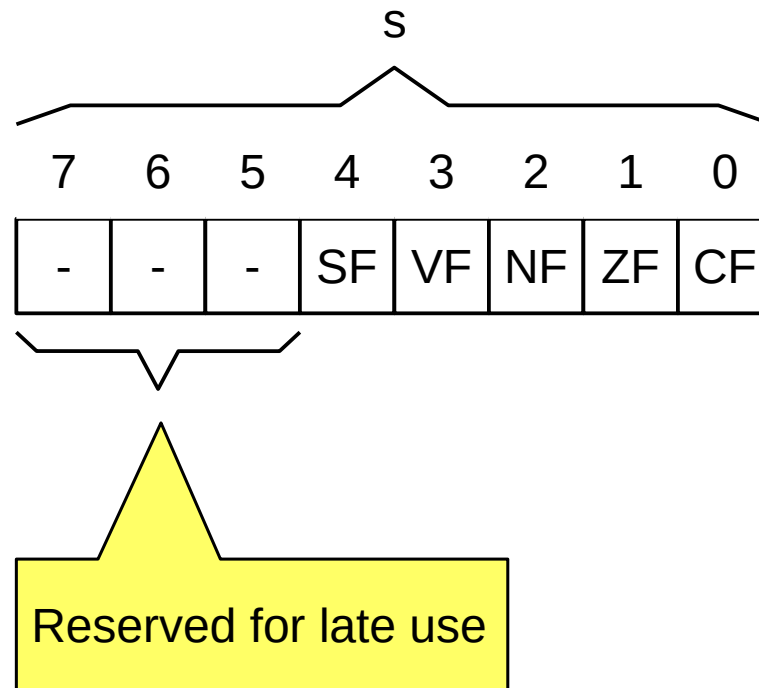

Status register flags

- CF: Carry Flag
- ZF: Zero Flag
- NF: Negative Flag
- VF: oVerflow Flag
- SF: Sign Flag

YASAC Stage 3

Branch instructions

- **JMP** k
 - **JuMP** to instruction at memory address k.
 - It is like a MOV instruction for the program counter.
- **BRBS** s, k
 - **BR**anch to instruction at memory address k if **Bit** s in the status register is **Set**.
- **BRBC** s, k
 - **BR**anch to instruction at memory address k if **Bit** s in the status register is **Cleared**.

```
JMP 0xA2          ; Using a numeric address
JMP LOOP          ; Using a label (translated by the assembler)

BRBS 0, NEXT      ; Branch if carry set
BRBS ZF, CONT     ; Branch if zero (using a constant ZF=1)

BRBC VF, NO_OV   ; Branch if no overflow
BRBC SF, PLUS    ; Branch if the sign of the result is positive
```


YASAC Stage 3

Instruction set

Op. code	Instruction	RTL	SVNZC
00001	LDI Ra, k	$Ra \leftarrow k$	-----
00010	MOV Ra, Rb	$Ra \leftarrow Rb$	-----
00011	ADD Ra, Rb	$Ra \leftarrow Ra + Rb$	*****
00100	SUB Ra, Rb	$Ra \leftarrow Ra - Rb$	*****
00101	STOP	–	-----
00110	LD Ra, Rb	$Ra \leftarrow \text{datamem}(Rb)$	-----
00111	ST Rb, Ra	$\text{datamem}(Rb) \leftarrow Rb$	-----
01000	LDS Ra, k	$Ra \leftarrow \text{datamem}(k)$	-----
01001	STS k, Ra	$\text{datamem}(k) \leftarrow Ra$	-----
01010	JMP k	$PC \leftarrow k$	-----
01011	BRBS s, k	$\text{sreg}[s]: PC \leftarrow k$	-----
01100	BRBC s, k	$\text{sreg}[s]==0: PC \leftarrow k$	-----

Now we need to specify how the status register is updated

YASAC Stage 3

Branch pseudo instructions

Instruction	Pseudo-instructions	Description
BRBS 0, k	BRCS k BRLO k	Branch if carry (Carry Set) Branch if A<B after unsigned A-B (LOWer)
BRBS 1, k	BRZS k BREQ k	Branch if the result is zero (Zero Set) Branch if A=B after A-B (EQual)
BRBS 2, k	BRMI k	Branch if the sign is Minus
BRBS 3, k	BRVS k	Branch if overflow (oVerflow Set)
BRBS 4, k	BRLT k	Branch A<B after signed A-B (Less Than)
BRBC 0, k	BRCC k BRSH k	Branch if no carry (Carry Cleared) Branch if A≥B after uns. A-B (Same or Higher)
BRBC 1, k	BRZC k BRNE k	Branch if the result is not zero (Zero Cleared) Branch if A≠B after A-B (Not Equal)
BRBC 2, k	BRPL k	Branch if the sign is PLus
BRBC 3, k	BRVC k	Branch if not overflow (oVerflow Cleared)
BRBC 4, k	BRGE k	Branch A≥B after signed A-B (Greater or Equal)

- Easier to remember.
- Automatically translated by the assembler.

YASAC Stage 3

Sample program

Assembly code


```
LDI R0, 120
LDS R1, 40
STS 0xf1, R0
STS 0xf2, R1
ADD R0, R1
STS 0xf1, R0
BRVS OK
STOP
OK:  JMP CONT
     STOP
CONT: LDI R3, 0xff
     STS 0xf2, R3
     STOP
```

Quick exercise


- What is the output at ports 01 and 02 if the program runs correctly?
- What is the real instruction for "BRVS OK"?

Change these to try other numbers and instructions

YASAC Stage 3 Data unit

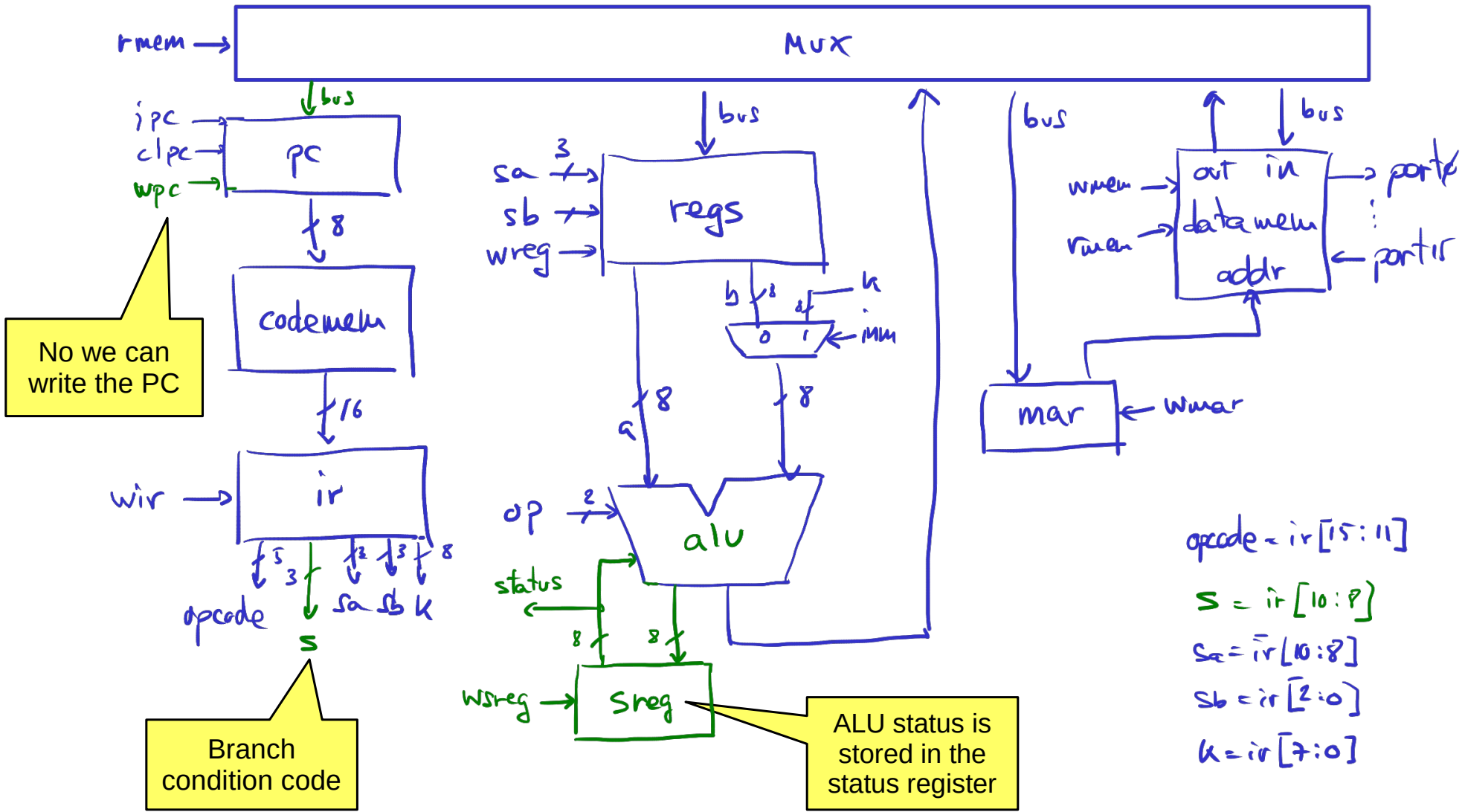

YASAC Stage 3 Updated ALU

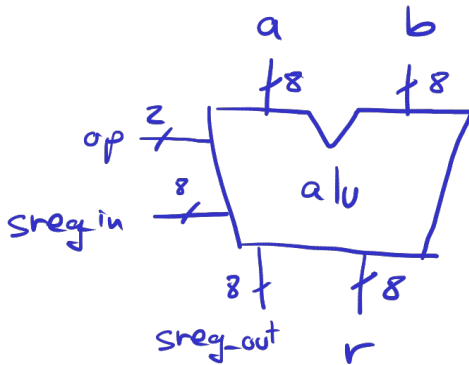

OP sym.	OP	alu_out	sreg_out S V N Z C
ALU-ADD	0 0	a+b	* * * * *
ALU-TRA	0 1	a	- - - - -
ALU-SUB	1 0	a-b	* * * * *
ALU-TRB	1 1	b	- - - - -

sreg_in = { -, -, -, S_i, V_i, N_i, Z_i, C_i }

sreg_out = { -, -, -, S_o, V_o, N_o, Z_o, C_o }

ADD

$$C_0 = a_7 b_7 + b_7 \bar{r}_7 + a_7 \bar{r}_7$$

$$Z_0 = \overline{\text{OR}(r)}$$

$$N_0 = r(7)$$

$$V_0 = a_7 b_7 \bar{r}_7 + \bar{a}_7 \bar{b}_7 r_7$$

$$S_0 = V_0 \oplus N_0$$

SUB

$$C_0 = \bar{a}_7 b_7 + b_7 r_7 + \bar{a}_7 r_7$$

$$Z_0 = \overline{\text{OR}(r)}$$

$$N_0 = r(7)$$


$$V_0 = a_7 \bar{b}_7 \bar{r}_7 + \bar{a}_7 b_7 r_7$$

$$S_0 = V_0 \oplus N_0$$

$$S_0 = \begin{cases} N_0 & \text{if } V_0 = 0, \\ \bar{N}_0 & \text{if } V_0 = 1 \end{cases}$$

YASAC Stage 3

Updated/new data unit blocks

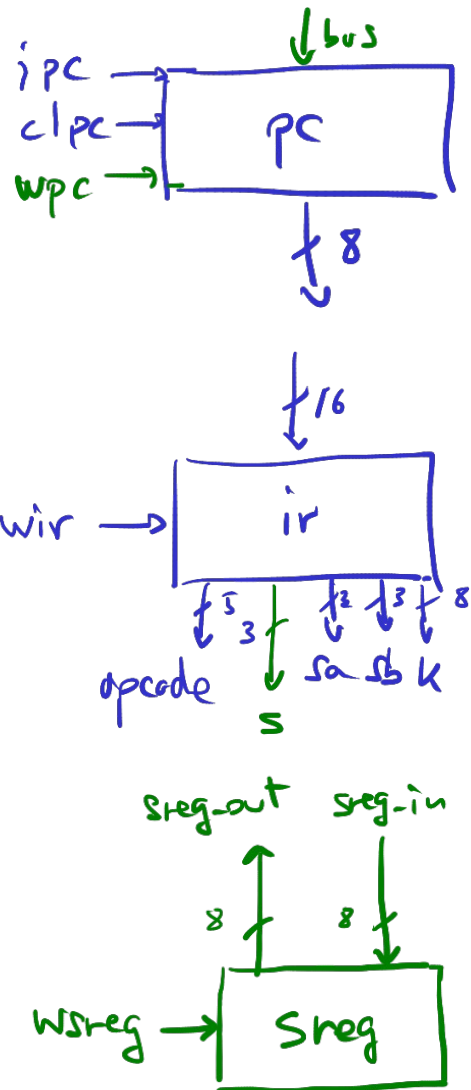

$iPC: PC \leftarrow (PC + 1) \bmod 256$

$clPC: PC \leftarrow 0$

$wPC: PC \leftarrow bus$

$S = ir [10:8]$

$wsreg: sreg \leftarrow sreg_in$

YASAC Stage 3

Control unit. Micro-operations

Updated arithmetic operations

ADD R_a, R_b 1) $R_a \leftarrow R_a + R_b$; $sreg \leftarrow sreg_out$ $op = ALU_ADD, wreg, wsreg$

SUB R_a, R_b 1) $R_a \leftarrow R_a - R_b$; $sreg \leftarrow sreg_out$ $op = ALU_SUB, wreg, wsreg$

New jump instructions

JMP k 1) $pc \leftarrow k$ $imm, op = ALU_TRB, wpc$

BRBS s, k 1) $status[s] : pc \leftarrow k$ $status[s] : (imm, op = ALU_TRB, wpc)$

BRBC s, k 1) $\overline{status[s]} : pc \leftarrow k$ $\overline{status[s]} : (imm, op = ALU_TRB, wpc)$

All new instructions are executed in a single clock cycle.

YASAC Stage 3

Control unit. States and control table

	READY	FETCH	EXEC1	EXEC2
LDI Ra, k	ready start: clpc	wir, ipc	op=11, wreg, inm → FETCH	
MOV Ra, Rb			op=11, wreg, → FETCH	
ADD Ra, Rb			op=00, wreg, wsreg → FETCH	
SUB Ra, Rb			op=10, wreg, wsreg → FETCH	
STOP			→ READY	
LD Ra, Rb			op=11, wmar	rmem, wreg → FETCH
ST Rb, Ra			op=11, wmar	op=01, wmem → FETCH
LDS Ra, k			op=11, wmar, inm	rmem, wreg → FETCH
STS k, Ra			op=11, wmar, inm	op=01, wmem → FETCH
JMP k			inm, op=11, wpc	
BRBS s, k			status[s]: inm, op=11, wpc → FETCH	
BRBC s, k			~status[s]: inm, op=11, wpc → FETCH	

With this table we can update the Verilog code (do not need to draw an ASM chart).

YASAC Stage 3

Verilog coding. Try it yourself!

- Update the data unit modules that have changed:
 - ALU (alu.v)
 - PC, IR (data_unit.v)
- Design the new elements
 - Status register (data_unit.v)
- Update the control unit with the new instructions
- Update the input/output interface of the control and data units and update its interconnection (yasac.v).
- Write a simple program that uses branch instructions.
- Simulate:
 - Resolve syntax and compiler problems.
 - Check result.
 - If not correct, debug with Gtkwave.

YASAC Stage 4

- Stage 3 limitations
 - The instruction set is poor: no logic or bit manipulation instructions.
 - (A few more...)
- Why logic instructions?
 - Bit manipulation (through masks).
 - Very useful to read/write individual input/output bits.
- Why shifting instructions?
 - Bit manipulation: bit counting, parity, etc.
 - Arithmetic: multiply/divide by 2.
 - Serial communications.
- What about updating the status register?
 - Useful to clean previous states.

With these modifications, the YASAC ISA is fairly complete and makes writing assembly programs much easier.


YASAC Stage 4

Overall needed changes

- ALU:
 - Implement logic operations.
 - Implement shift operations.
- Status register:
 - New inputs to allow register updates.
- Control unit:
 - Implement new instructions.

YASAC Stage 4

Instruction format

 

Now also used as status register bit selector.

YASAC Stage 4

Instruction set

Op. code	Instruction	RTL	SVNZC
00001	LDI Ra, k	$Ra \leftarrow k$	-----
00010	MOV Ra, Rb	$Ra \leftarrow Rb$	-----
00011	ADD Ra, Rb	$Ra \leftarrow Ra + Rb$	*****
00100	SUB Ra, Rb	$Ra \leftarrow Ra - Rb$	*****
00101	STOP	–	-----
00110	LD Ra, Rb	$Ra \leftarrow \text{datamem}(Rb)$	-----
00111	ST Rb, Ra	$\text{datamem}(Rb) \leftarrow Ra$	-----
01000	LDS Ra, k	$Ra \leftarrow \text{datamem}(k)$	-----
01001	STS k, Ra	$\text{datamem}(k) \leftarrow Ra$	-----
01010	JMP k	$PC \leftarrow k$	-----
01011	BRBS s, k	$\text{status}[s]: PC \leftarrow k$	-----
01100	BRBC s, k	$\sim\text{status}[s]: PC \leftarrow k$	-----
01101	AND Ra, Rb	$Ra \leftarrow Ra \& Rb$	*****
01110	OR Ra, Rb	$Ra \leftarrow Ra Rb$	*****
01111	EOR Ra, Rb	$Ra \leftarrow Ra \wedge Rb$	*****
10000	ROR Ra	$Ra \leftarrow \text{SHR}(Ra, C)$	*****
10001	ROL Ra	$Ra \leftarrow \text{SHL}(Ra, C)$	*****
10010	BCLR s	$\text{sreg}[s] \leftarrow 0$	*****
10011	BSET s	$\text{sreg}[s] \leftarrow 1$	*****

YASAC Stage 4

BCLR and BSET pseudo instructions

Instruction	Pseudo-instructions	Description
BCLR 0	CLC	CLear Carry bit
BCLR 1	CLZ	CLear Zero bit
BCLR 2	CLN	CLear Negative bit
BCLR 3	CLV	CLear oVerflow bit
BCLR 4	CLS	CLear Sign bit
BSET 0	SEC	SEt Carry bit
BSET 1	SEZ	SEt Zero bit
BSET 2	SEN	SEt Negative bit
BSET 3	SEV	SEt oVerflow bit
BSET 4	SES	SEt Sign bit

YASAC Stage 4

Sample program

```

; input:  port08 = 0x5a (01011010)
; output: port01 = 0xa2
;         port02 = 0x8a
;
ldi r0, 0          ; r0 = 0
sub r0, r0         ; C=N=V=S=0, Z=1
lds r0, 0xf8       ; 0 01011010 (0 5a)
rol r0             ; 0 10110100 (0 b4)
rol r0             ; 1 01101000 (1 68)
rol r0             ; 0 11010001 (0 c1)
rol r0             ; 1 10100010 (1 a2)
sts 0xf1, r0       ; port01 = a2
clc                ; 0 10100010 (0 a2)
ror r0             ; 0 01010001 (0 51)
clc                ; 0 01010001 (0 51)
ror r0             ; 1 00101000 (1 28)
clc                ; 0 00101000 (0 28)
ror r0             ; 0 00010100 (0 14)
sec                ; 1 00010100 (1 14)
ror r0             ; 0 10001010 (0 8a)
sts 0xf2, r0       ; port02 = 8a
stop               ;)

```

Quick exercise


- What is the output at ports 01 and 02 if port08 = 11010011 initially?
- What are the real instruction for “CLC” and “SEC”?

C, R0


We do not have simple shift instructions but:

- CLC + ROR → SHR
- CLC + ROL → SHL

YASAC Stage 4 Data unit

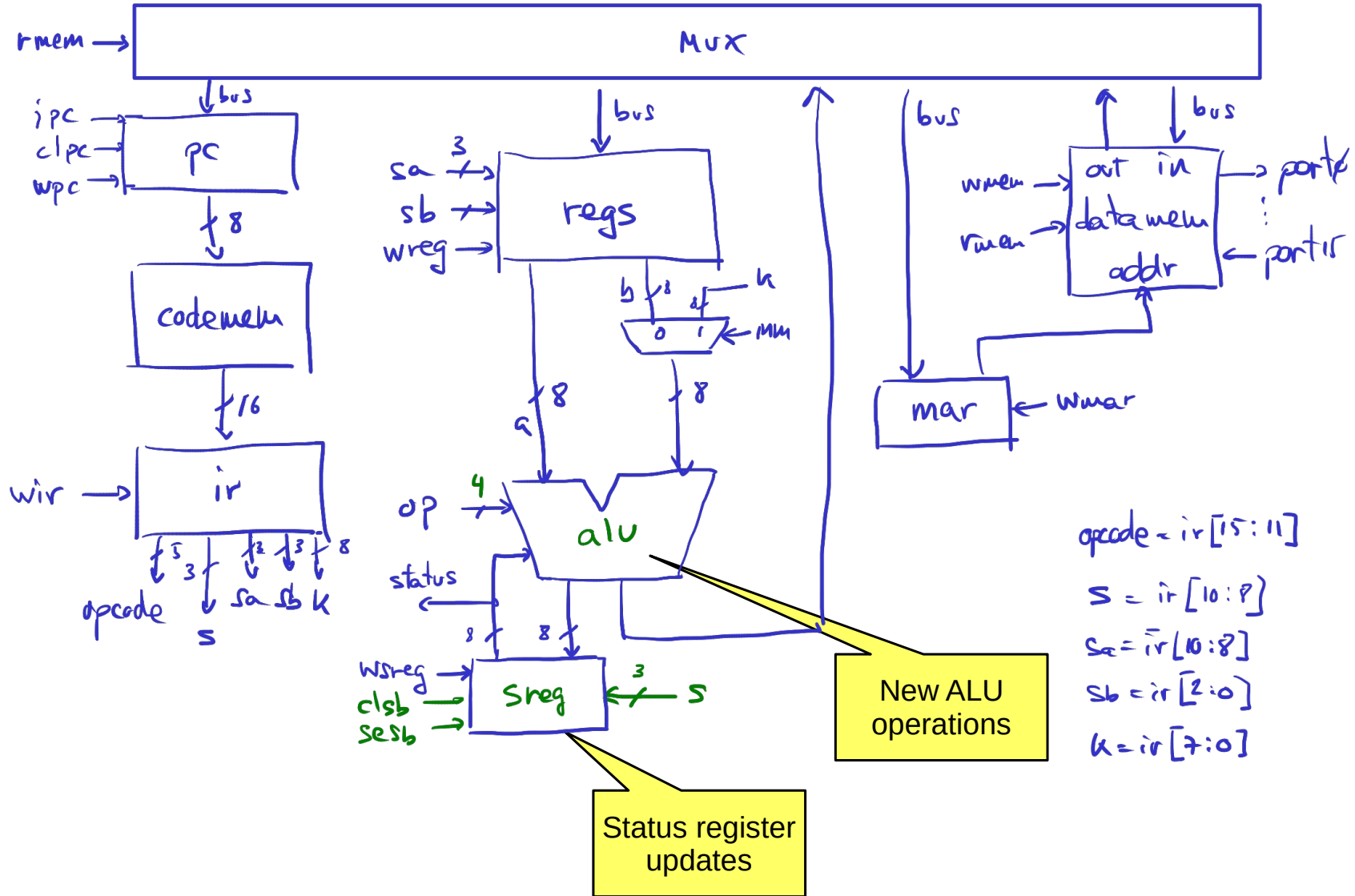

YASAC Stage 4 Updated ALU

 

OP sym.	OP	r	Sreg SVNZC
ALU_ADD	0000	a+b	*****
ALU_TRA	0001	a	-----
ALU_SUB	0010	a-b	*****
ALU_TRB	0011	b	-----
ALU_NEG	0100	-a	*****
ALU_AND	0101	AND(a,b)	****-
ALU_OR	0110	OR(a,b)	****-
ALU_EOR	0111	EOR(a,b)	* ** *-
ALU_ROR	1000	SHR(a, c _i)	*****
ALU_ROL	1001	SHL(a, c _i)	*****

NEG

$$C_0 = \overline{OR(a)}$$

$$Z_0 = \overline{OR(r)}$$

$$N_0 = r(7)$$

$$V_0 = a_7 r_7 + \overline{a_7} \overline{r_7}$$

$$S_0 = V_0 \oplus N_0$$

AND, OR, EOR

$$C_0 = C_i$$

$$Z_0 = \overline{OR(r)}$$

$$N_0 = r(7)$$


$$V_0 = 0$$

$$S_0 = V_0 \oplus N_0$$

ROR	ROL
$C_0 = a_0$	$C_0 = a_7$
$Z = \overline{OR(r)}$	$Z = \overline{OR(r)}$
$N = r(7)$	$N = r(7)$
$V_0 = C_{in} \oplus a_0$	$V_0 = a_7 \oplus a_6$
$S_0 = V_0 \oplus N_0$	$S_0 = V_0 \oplus N_0$

YASAC Stage 4

Updated/new data unit blocks

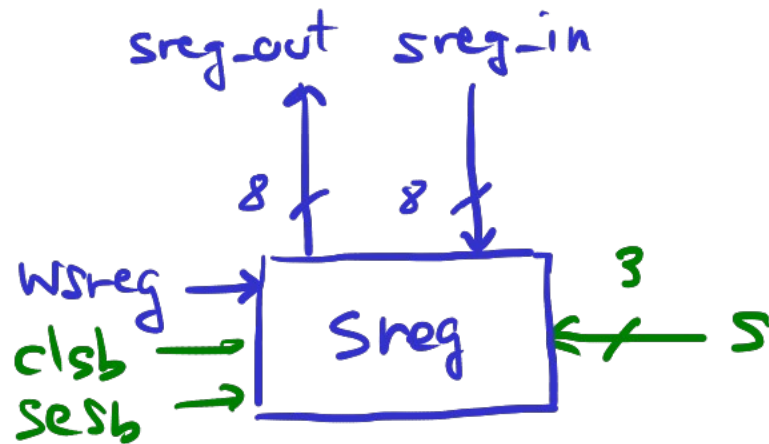

wsreg : $sreg \leftarrow sreg_in$

clsb : $sreg[s] \leftarrow 0$

sesb : $sreg[s] \leftarrow 1$

YASAC Stage 4

Control unit. Micro-operations

Logic instructions

AND R_a, R_b 1) $R_a \leftarrow R_a \& R_b$; $sreg \leftarrow sreg_out$ ($op = ALU_AND, wreg, wsreg$)

OR R_a, R_b 1) $R_a \leftarrow R_a | R_b$; $sreg \leftarrow sreg_out$ ($op = ALU_OR, wreg, wsreg$)

EOR R_a, R_b 1) $R_a \leftarrow R_a \wedge R_b$; $sreg \leftarrow sreg_out$ ($op = ALU_EOR, wreg, wsreg$)

Shifting (rotating) instructions

ROR R_a 1) $R_a \leftarrow SHR(R_a, c)$; $sreg \leftarrow sreg_out$ ($op = ALU_ROR, wreg, wsreg$)

ROL R_a 1) $R_a \leftarrow SHL(R_a, c)$; $sreg \leftarrow sreg_out$ ($op = ALU_ROL, wreg, wsreg$)

Status update instructions

BCLR s 1) $sreg[s] \leftarrow 0$ $clsb$

BSET s 1) $sreg[s] \leftarrow 1$ $sesb$

All new instructions are executed in a single clock cycle.

YASAC Stage 4

Control unit. States and control table

	READY	FETCH	EXEC1	EXEC2
LDI Ra, k	ready start: clpc	wir, ipc	op=0011, wreg, inm → FETCH	
MOV Ra, Rb			op=0011, wreg, → FETCH	
ADD Ra, Rb			op=0000, wreg, wsreg → FETCH	
SUB Ra, Rb			op=0010, wreg, wsreg → FETCH	
STOP			→ READY	
LD Ra, Rb			op=0011, wmar	rmem, wreg → FETCH
ST Rb, Ra			op=0011, wmar	op=0001, wmem → FETCH
LDS Ra, k			op=0011, wmar, inm	rmem, wreg → FETCH
STS k, Ra			op=0011, wmar, inm	op=0001, wmem → FETCH
JMP k			inm, op=0011, wpc	
BRBS s, k			status[s]: inm, op=0011, wpc → FETCH	
BRBC s, k			~status[s]: inm, op=0011, wpc → FETCH	

Old instructions only update the width of the ALU's operation code.

YASAC Stage 4

Control unit. States and control table

	READY	FETCH	EXEC1
AND Ra, Rb	ready start: clpc	wir, ipc	op=0101, wreg, wsreg → FETCH
OR Ra, Rb			op=0110, wreg, wsreg → FETCH
EOR Ra, Rb			op=0111, wreg, wsreg → FETCH
ROR Ra			op=1000, wreg, wsreg → FETCH
ROL Ra			op=1001, wreg, wsreg → FETCH
BCLR s			clsb → FETCH
BSET s			sesb → FETCH

With this table we can update the Verilog code (do not need to draw an ASM chart).

YASAC Stage 4

Verilog coding. Try it yourself!

- Update the data unit modules that have changed:
 - ALU (alu.v)
 - Status register
- Update the control unit with the new instructions
- Update the input/output interface of the control and data units and update its interconnection (yasac.v).
- Write a simple program that uses the new instructions.
 - Or use the example in a previous slide.
- Simulate:
 - Resolve syntax and compiler problems.
 - Check result.
 - If not correct, debug with Gtkwave.

YASAC Stage 5

- Stage 4 limitations
 - No subroutine support and no stack.
 - (A few more...)
- Why subroutines?
 - Repetitive tasks.
 - Code re-usability.
 - Recursion.
- Why a stack?
 - It is a convenient way to store data needed to implement subroutines.
 - It is also useful to save register contents to memory and recall it later.
 - Greatly simplifies the job of programs that implement higher-level languages (compilers):
 - Parameter passing.
 - Local data (to a function or method).

With these modifications, the YASAC ISA is ready to implement complex programs in assembly, like programs to support higher-level languages: parsers, assemblers, compilers, etc.

Stacks

- A type of Last-In, First-Out memory (LIFO).
- Two operations:
 - PUSH: stores data in the stack.
 - POP: retrieves the last data pushed to the stack, not previously popped.
- Implementation in computers
 - Use RAM memory.
 - Start at a stack's base memory address.
 - Use a stack pointer register to store the current stack's top address.
 - Make the stack to grow downwards to maximize memory usage.
 - Be careful not to overrun your program's code or data by growing the stack too much.
 - Do not worry, modern processors have mechanisms to handle it.


YASAC Stage 5

Needed changes

- Stack pointer register.
- Program counter read operation.
 - Needed to save it onto the stack when CALL.
- Control unit:
 - Implement new instructions.

YASAC Stage 5

Instruction format (same as stage 4)

 

YASAC Stage 5

Instruction set

Op. code	Instruction	RTL	SVNZC
00001	LDI Ra, k	$Ra \leftarrow k$	-----
00010	MOV Ra, Rb	$Ra \leftarrow Rb$	-----
00011	ADD Ra, Rb	$Ra \leftarrow Ra + Rb$	*****
00100	SUB Ra, Rb	$Ra \leftarrow Ra - Rb$	*****
00101	STOP	–	-----
00110	LD Ra, Rb	$Ra \leftarrow \text{datamem}(Rb)$	-----
00111	ST Rb, Ra	$\text{datamem}(Rb) \leftarrow Rb$	-----
01000	LDS Ra, k	$Ra \leftarrow \text{datamem}(k)$	-----
01001	STS k, Ra	$\text{datamem}(k) \leftarrow Ra$	-----
01010	JMP k	$PC \leftarrow k$	-----
01011	BRBS s, k	$\text{status}[s]: PC \leftarrow k$	-----
01100	BRBC s, k	$\sim\text{status}[s]: PC \leftarrow k$	-----
01101	AND Ra, Rb	$Ra \leftarrow Ra \& Rb$	*****
01110	OR Ra, Rb	$Ra \leftarrow Ra Rb$	*****
01111	EOR Ra, Rb	$Ra \leftarrow Ra \wedge Rb$	*****
10000	ROR Ra	$Ra \leftarrow \text{SHR}(Ra, C)$	*****
10001	ROL Ra	$Ra \leftarrow \text{SHL}(Ra, C)$	*****
10010	BCLR s	$\text{sreg}[s] \leftarrow 0$	*****
10011	BSET s	$\text{sreg}[s] \leftarrow 1$	*****
10100	PUSH Ra	$\text{datamem}[sp] \leftarrow Ra; sp \leftarrow sp - 1$	-----
10101	POP Ra	$Ra \leftarrow \text{datamem}[sp+1]; sp \leftarrow sp + 1$	-----
10110	CALL k	$\text{datamem}[sp] \leftarrow pc; pc \leftarrow k; sp \leftarrow sp - 1$	-----
10111	RET	$pc \leftarrow \text{datamem}[sp+1]; sp \leftarrow sp + 1$	-----

YASAC Stage 5

Sample program


```
; input:  port08 = 0x5a (01011010)
; output: port01 = ?
;         port02 = ?
;
;         lds r0, 0xf8      ; r0 = port08
;         ldi r1, 0xff
;         push r0
;         pop r1
;         call send
;         stop
;         stop
;         stop
;         stop
send:     sts 0xf1, r1
;         sts 0xf2, r0
;         ret
;         stop
```

Quick exercise

- What is the expected output at port01 and port02?
- How many instruction in the sample code are never executed?


YASAC Stage 5

Data unit

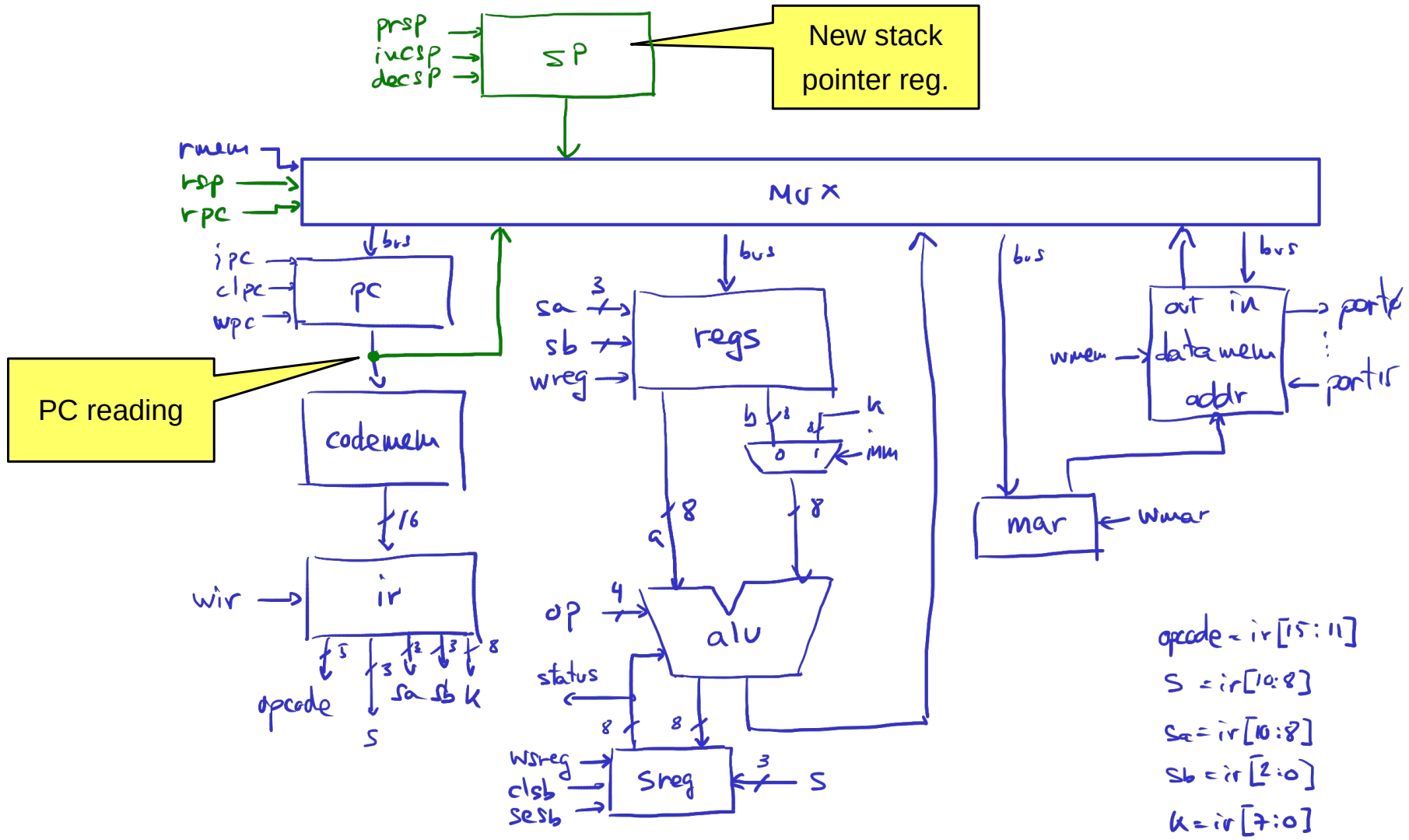

YASAC Stage 5

New stack pointer register

 

prsp: $SP \leftarrow \text{STACK_BASE}$

decsp: $sp \leftarrow sp - 1$

incsp: $sp \leftarrow sp + 1$

$\text{STACK_BASE} = 0x\text{EF}$

YASAC Stage 5

Control unit. Micro-operations

PUSH R_a $data_mem(sp) \leftarrow R_a ; sp \leftarrow sp - 1$

1) $mar \leftarrow sp ; sp \leftarrow sp - 1$ $r_{sp}, w_{mar}, dec_{sp}$

2) $data_mem(mar) \leftarrow R_a$ $op = ALU_TRA, w_{mem}$

POP R_a $R_a \leftarrow data_mem(sp+1) ; sp \leftarrow sp + 1$

1) $sp \leftarrow sp + 1$ inc_{sp}

2) $mar \leftarrow sp$ r_{sp}, w_{mar}

3) $R_a = data_mem(mar)$ r_{mem}, w_{reg}

YASAC Stage 5

Control unit. Micro-operations

CALL k $data_mem(sp) \leftarrow pc ; pc \leftarrow k ; sp \leftarrow sp - 1$

- | | | |
|----|--|----------------------------------|
| 1) | $mar \leftarrow sp ; sp \leftarrow sp - 1$ | $r_{sp}, w_{mar}, dec_{sp}$ |
| 2) | $data_mem(mar) \leftarrow pc$ | r_{pc}, w_{mem} |
| 3) | $pc \leftarrow k$ | $i_{mem}, op = ALU_TRB, w_{pc}$ |

RET $pc \leftarrow data_mem(sp + 1) ; sp \leftarrow sp + 1$

- | | | |
|----|--------------------------------|-------------------|
| 1) | $sp \leftarrow sp + 1$ | inc_{sp} |
| 2) | $mar \leftarrow sp$ | r_{sp}, w_{mar} |
| 3) | $pc \leftarrow data_mem(mar)$ | r_{mem}, w_{pc} |

YASAC Stage 5

Control unit. States and control table

Instruction	EXEC1	EXEC2
LDI Ra, k	op=0011, wreg, inm	
MOV Ra, Rb	op=0011, wreg	
ADD Ra, Rb	op=0000, wreg, wsreg	
SUB Ra, Rb	op=0010, wreg, wsreg	
STOP		
LD Ra, Rb	op=0011, wmar	rmem, wreg
ST Rb, Ra	op=0011, wmar	op=0001, wmem
LDS Ra, k	op=0011, wmar, inm	rmem, wreg
STS k, Ra	op=0011, wmar, inm	op=0001, wmem
JMP k	inm, op=0011, wpc	
BRBS s, k	status[s]: inm, op=0011, wpc	
BRBC s, k	~status[s]: inm, op=0011, wpc	

NOTE:

- READY and FETCH states have been omitted.
- All instructions go back to FETCH except STOP that returns to READY.

YASAC Stage 5

Control unit. States and control table

	EXEC1	EXEC2	EXEC3
AND Ra, Rb	op=0101, wreg, wsreg		
OR Ra, Rb	op=0110, wreg, wsreg		
EOR Ra, Rb	op=0111, wreg, wsreg		
ROR Ra	op=1000, wreg, wsreg		
ROL Ra	op=1001, wreg, wsreg		
BCLR s	clsb		
BSET s	sesb		
PUSH Ra	rsp, wmar, decsp	op=ALU_TRA, wmem	
POP Ra	incsp	rsp, wmar	rmem, wreg
CALL k	rsp, wmar, decsp	rpc, wmem	inm, op=ALU_TRB, wpc
RET	incsp	rsp, wmar	rmem, wpc

NOTE:

- EXEC1 is the same for (PUSH, CALL) and (POP, RET).
- EXEC2 is the same for (POP, RET).

YASAC Stage 5

Verilog coding. Try it yourself!

- Update the data unit:
 - Add stack pointer register.
 - Add PC out.
- Update the control unit with the new instructions.
- Update the input/output interface of the control and data units and update its interconnection (yasac.v).
- Write a simple program that uses the new instructions.
 - Or use the example in a previous slide.
- Simulate:
 - Resolve syntax and compiler problems.
 - Check result.
 - If not correct, debug with Gtkwave.

What's next?

Stage 6. Interrupts

- Interrupt lines are activated by external devices.
- The computer executes an interrupt service routine every time an external interrupt is activated.
 - Service routines are very similar to subroutines.
- Interrupts may be disabled.
- Greatly simplifies input/output programming:
 - No need to poll input ports in a loop, the external device will activate an interrupt when new data is available.
- Greatly simplifies common tasks:
 - A timer can activate an interrupt at regular intervals to update the time, check a keyboard, update output ports, etc.
- The basis for multitasking:
 - Periodic interrupts can be used to execute a task scheduler that will switch from one task to another.

What's next?

Stage 7. Bootloading

- Currently, the program is fixed and can only be changed by re-programming the FPGA chip.
- Bootloading: ability of the computer to load programs from the outside world.
- Two strategies:
 - Programming interface:
 - The control unit has a “programming” mode that reads data from the outside world and writes to the program memory.
 - Needs additional hardware, an external programmer device and external programming software.
 - Software bootloader and serial port:
 - The initial program in the computer will load a new program from the outside world by using some peripheral (e.g. a serial port).
 - Needs a hardware peripheral (serial port controller), instructions to load and store data from/to program memory (LDPM, STPM) and external programming software.

What's next?

System improvements

- Pulse-Width Modulation (PWM) output:
 - Light control, motor and servo control, etc.
- Serial communications: RS-232, SPI, I2C
 - Many peripherals use these: sensors, LCD screens, keyboards, etc.
- Timer (specially if we implement interrupts)
 - Measure time, do things at regular intervals, etc.

What's next?

Toolchain

- **Toolchain**
 - Software tool used for software or hardware development.
- **Basic toolchain:**
 - **Assembler:** converts assembly code into machine code.
 - **Programmer/uploader:** uploads machine code to the computer using a programming interface or bootloader.
- **Other typical toolchain programs:**
 - **C language compiler:** entry point to high-level programming.
 - **Linker:** combines machine code fragments, library functions, etc.
 - **Debugger:** executes programs in a controlled way in order to find errors (bugs).
 - **Object file (machine code) inspection:** disassembly, etc.

We'll see more on this in the next unit with a real computer.