 


Apartado 1

Carta ASM de la U. control:



Código Verilog

```

module unidcd_control(input reset, clk, S, P, output Wa, Wc, Rb, FIN)
parameter S0 = 2'b00, S1 = 2'b01, SF = 2'b10;
reg [1:0] estado_actual, proximo_estado;
always @(posedge clk, posedge reset)
    if (reset == 1)
        estado_actual <= S0;
    else
        estado_actual <= proximo_estado;
    
```

```
always @ (xs, P, estado_actual)
```

```
begin
```

```
{fin, wa, wc, rb} = 0;
```

```
proximo_estado = S0;
```

```
case (estado_actual)
```

```
S0:
```

```
if (xs == 1)
```

```
proximo_estado = S1;
```

```
S1:
```

```
begin
```

```
proximo_estado = SF;
```

```
wa = 1;
```

```
rb = 1;
```

```
if (P)
```

```
wc = 1;
```

```
end
```


```
SF:
```

```
fin = 1;
```


```
end case
```

```
end
```

```
endmodule
```

 


# Diagrama de ondas

 

# Apartado 2


1928 11/10

## Esquema del sistema digital

 


## Descripción a nivel RT

### CONT 1

 


$cl_1$	$up_1$	CONT1 ←	OUT =	$Cy_1$
0	0	CONT1	[CONT1]	1 si
0	1	CONT1 + 1	"	[CONT1] = 255
1	0	0	"	
1	1	proh.	proh	

### CONT 2

 

$cl_2$	$up_2$	CONT2 ←	$Cy_2$
0	0	CONT2	1 si
0	1	CONT2 + 1	[CONT2] = 7
1	0	0	
1	1	proh	

### REG

 

$w$	$shr$	REG ←	$z =$
0	0	REG	REG[0]
0	1	SHR(REG, -)	"
1	0	IN	"
1	1	proh	"

Carta ASM

